

Chapter 1

Introduction to CMOS Circuit Design

Jin-Fu Li

Advanced Reliable Systems (ARES) Lab.
Department of Electrical Engineering
National Central University
Jhongli, Taiwan


Outline

- Introduction
- MOS Transistor Switches
- CMOS Logic
- Circuit and System Representation

Binary Counter


Present state		Next state	
a	b	A	B
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

$$A = a'b + ab'$$
$$B = a'b' + ab'$$

 

Source: Prof. V. D. Agrawal

1-bit Multiplier

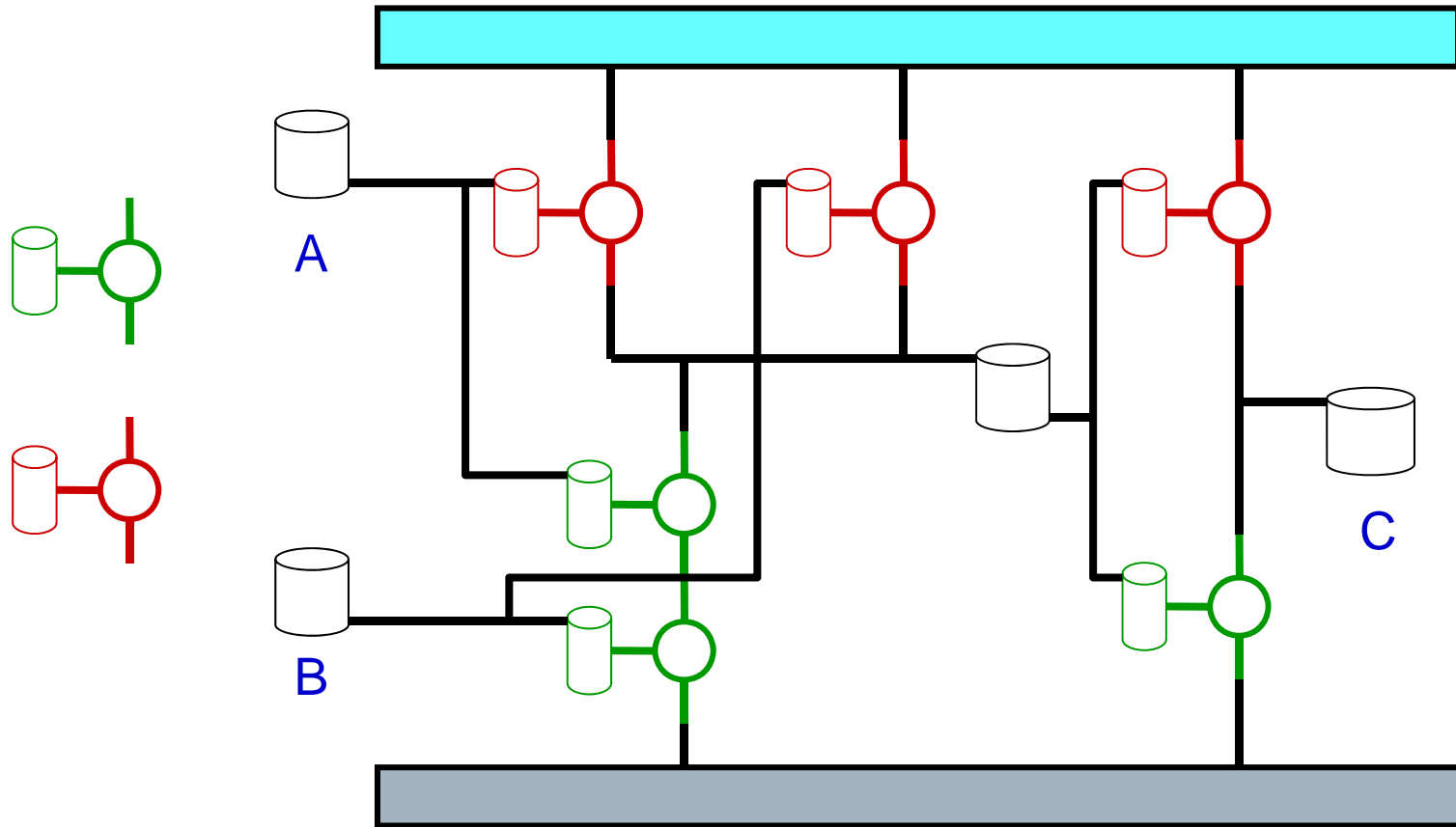


$$C = A \times B$$

Switch: MOSFET

- MOSFETs are basic electronic devices used to direct and control logic signals in IC design
 - MOSFET: Metal-Oxide-Semiconductor Field-Effect Transistor
 - N-type MOS (NMOS) and P-type MOS (PMOS)
 - Voltage-controlled switches
- A MOSFET has four terminals: gate, source, drain, and substrate (body)
- Complementary MOS (CMOS)
 - Using two types of MOSFETs to create logic networks
 - NMOS & PMOS


P-N Junctions

 - A junction between p-type and n-type semiconductor forms a diode.
- Current flows only in one direction




anode

cathode

 


NMOS Transistor

 - Four terminals: gate, source, drain, body
- Gate-oxide-body stack looks like a capacitor
 - Gate and body are conductors
 - SiO_2 (oxide) is a very good insulator
 - Called metal-oxide-semiconductor (MOS) capacitor
 - Even though gate is no longer made of metal




NMOS Operations

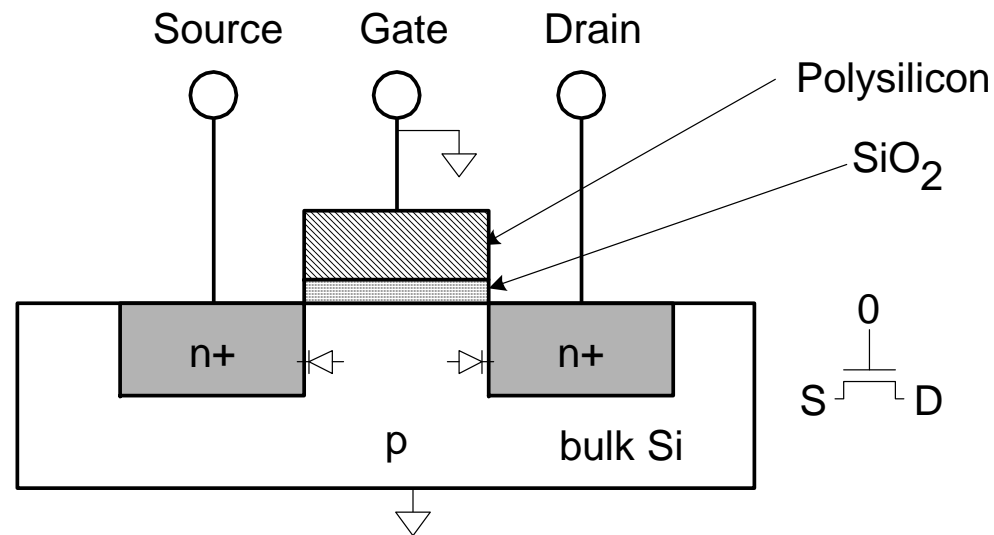- Body is commonly tied to ground (0 V)
- When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body diodes are OFF
 - No current flows, transistor is OFF




NMOS Operations (Cont.)

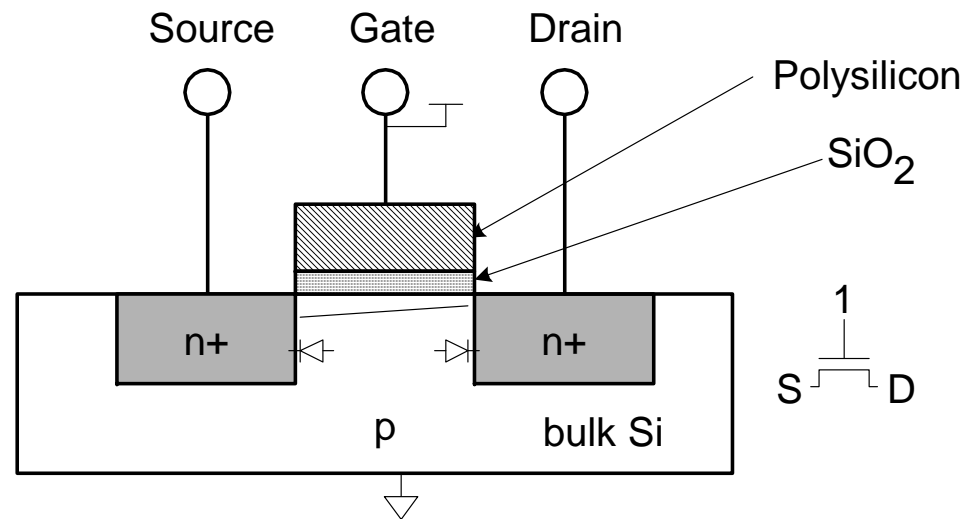- When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



PMOS Operations

 
- Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior




Threshold Voltage

- Every MOS transistor has a characterizing parameter called the **threshold voltage** V_T
- The specific value of V_T is established during the manufacturing process
- Threshold voltage of an NMOS and a PMOS

NMOS

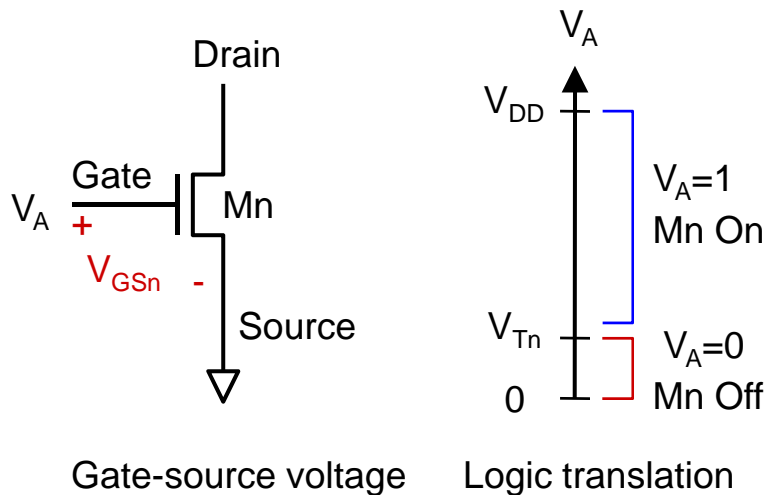

PMOS


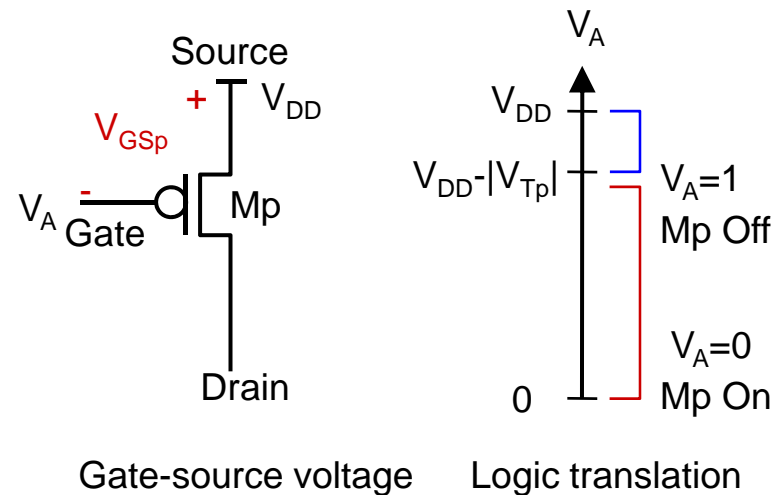


MOS Transistor is Like a Tap...




Source: Prof. Banerjee, ECE, UCSB

MOSFET & FinFET

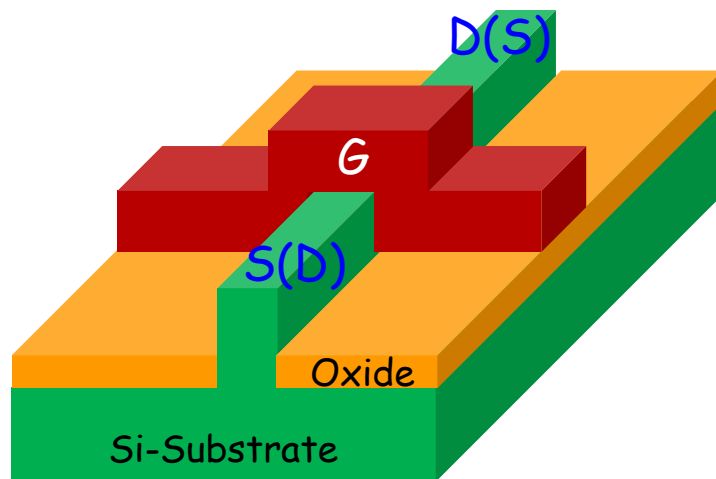 


Bulk FinFET

 



SOI FinFET

IG & SG FinFETs

 
- According to the gate structure, FinFET can be classified as
 - Independent-Gate (IG) FinFET
 - Short-Gate (SG) FinFET



IG FinFET

  


SG FinFET

 


MOS Switches

□ NMOS symbol and characteristics

 


□ PMOS symbol and characteristics

 


CMOS Switch

- A complementary CMOS switch
 - Transmission gate

Symbols

 



Characteristics

 

CMOS Logic-Inverter


□ The NOT or INVERT function is often considered the simplest Boolean operation

■ $F(x) = \text{NOT}(x) = x'$

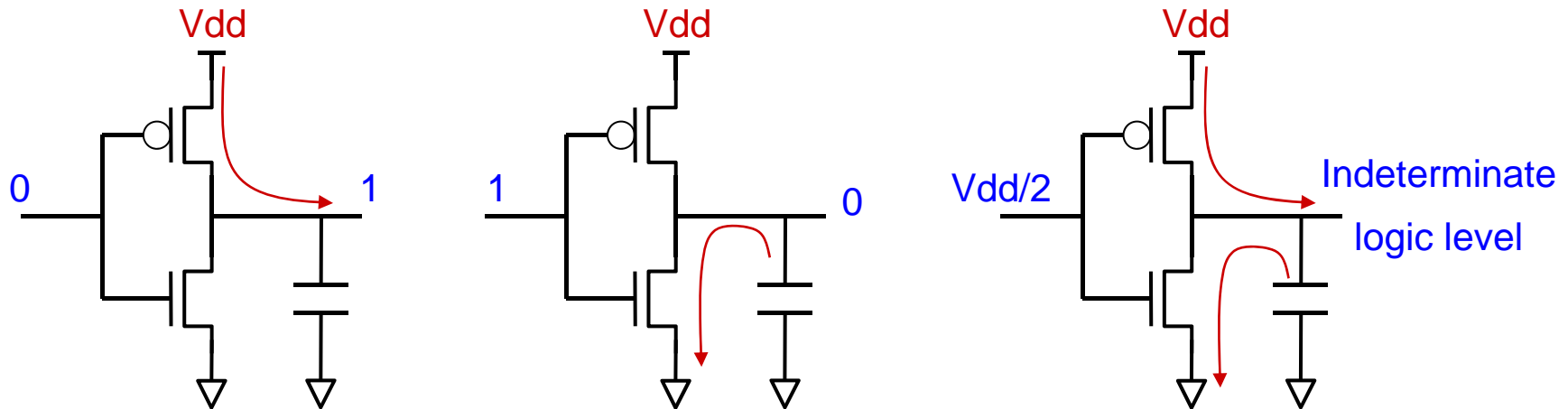 


Combinational Logic

Serial structure

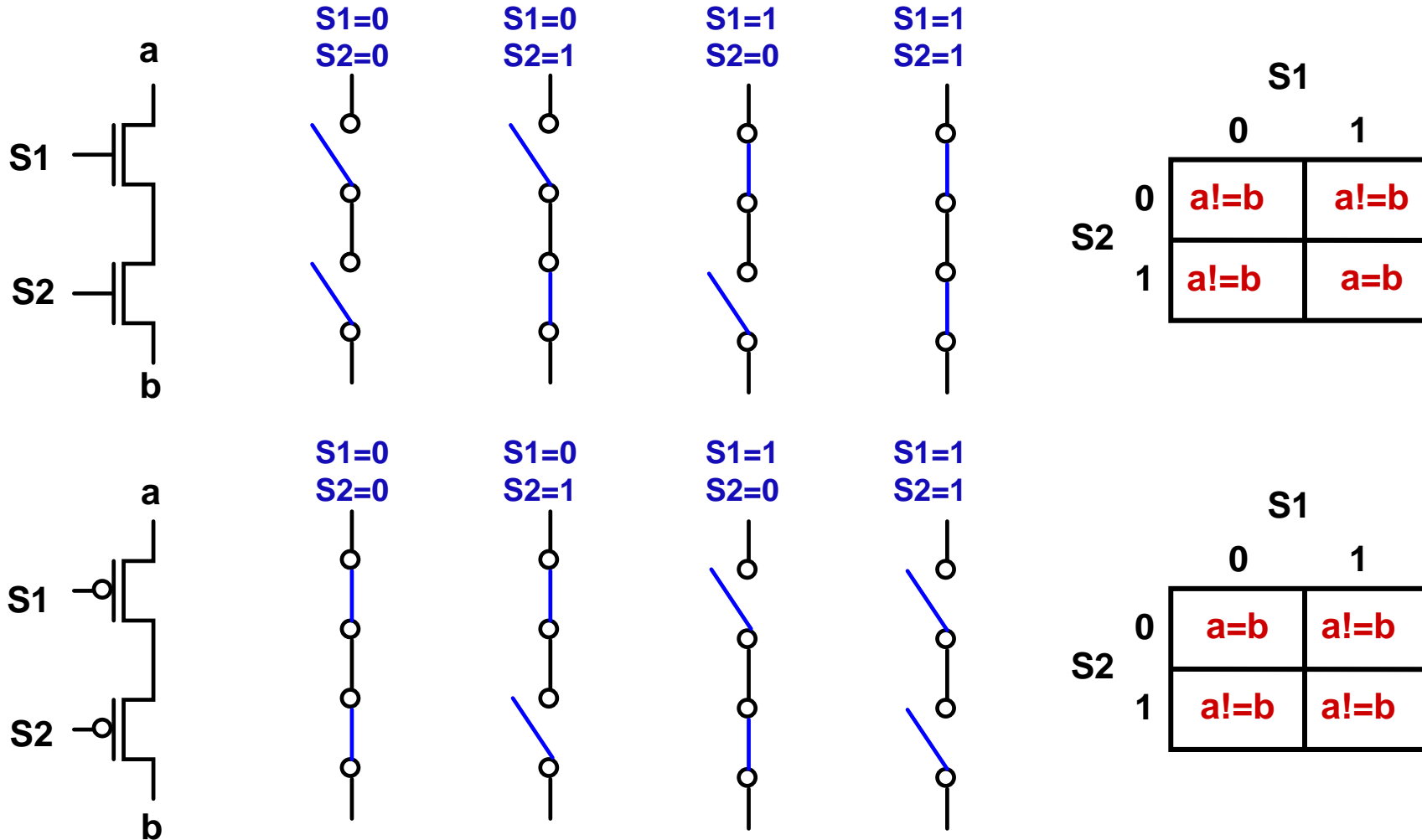


Combinational Logic


□ Parallel structure

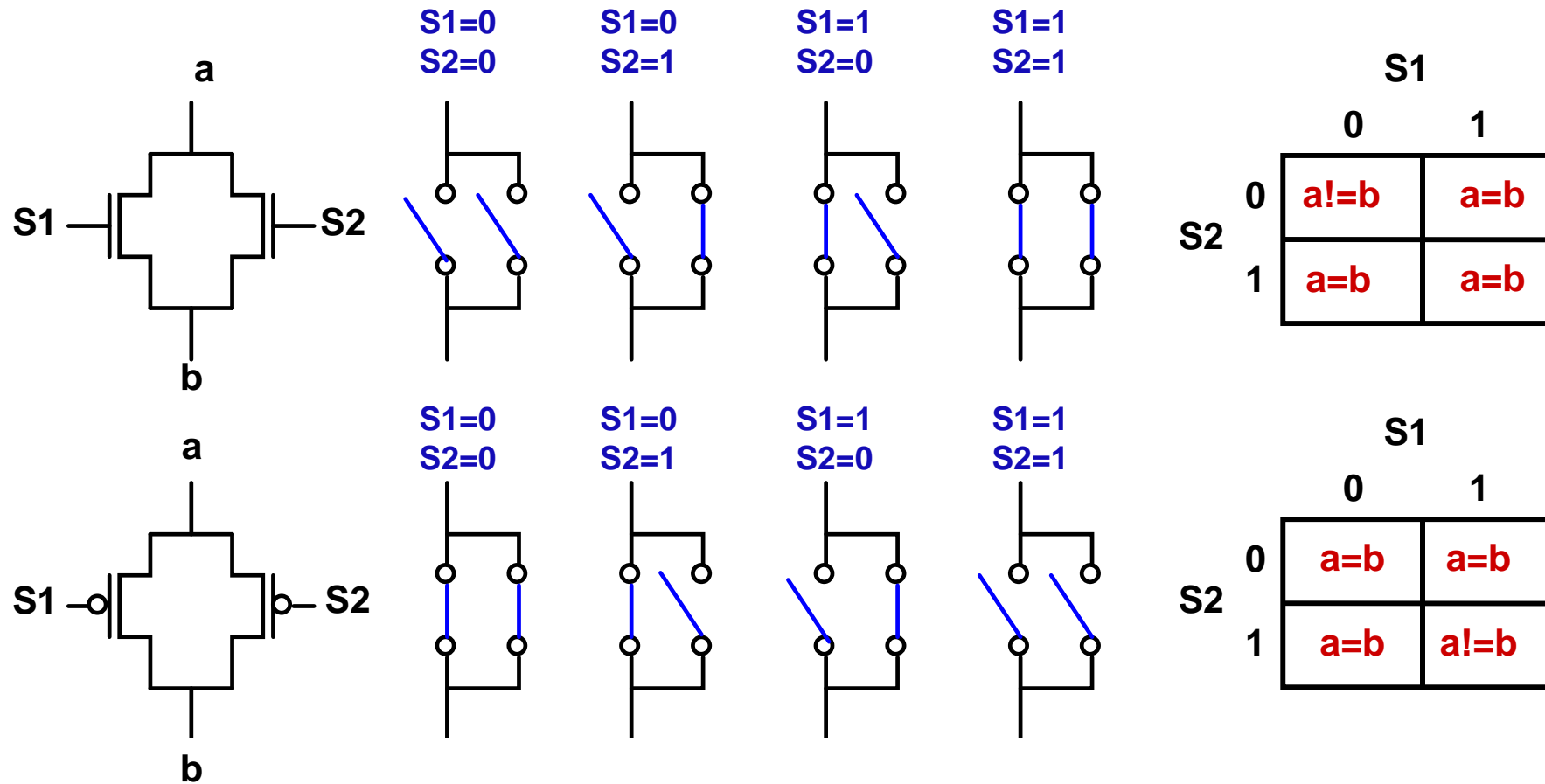

NAND Gate


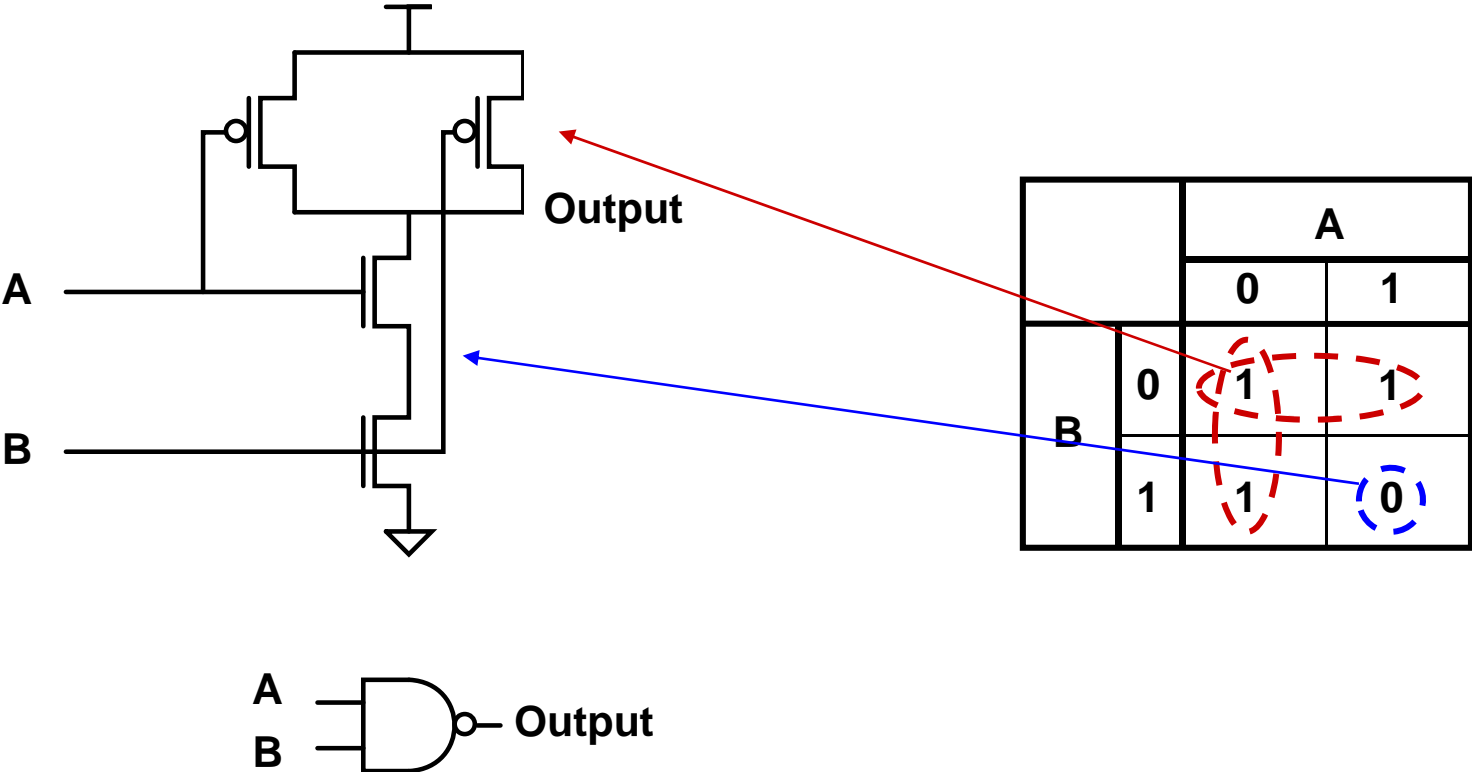


NOR Gate

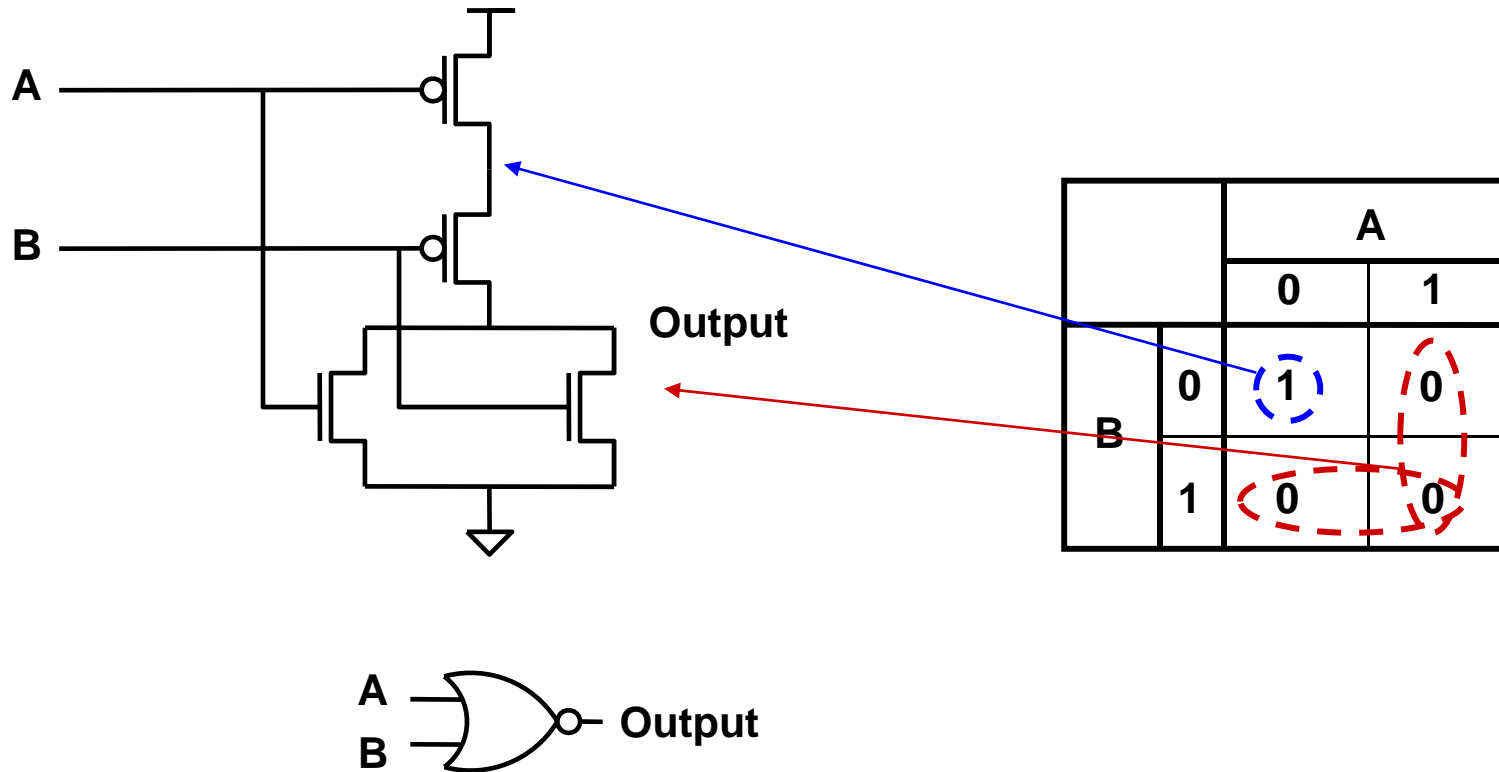


Compound Gate

□ $F = \overline{((AB) + (CD))}$

  

Structured Logic Design

 - CMOS logic gates are intrinsically **inverting**
 - The output always produces a NOT operation acting on the input variables
- For example, the inverter shown below illustrates this property



Structured Logic Design

- The inverting nature of CMOS logic circuits allows us to construct logic circuits for AOI and OAI expressions using a structured approach
- AOI logic function
 - Implements the operations in the order **AND then OR then NOT**
 - E.g., $g(a, b, c, d) = \overline{a.b + c.d}$
- OAI logic function
 - Implements the operations in the order **OR then AND then NOT**
 - E.g., $g(a, b, c, d) = \overline{(a + b) \cdot (c + d)}$

Structured Logic Design

- Behaviors of nMOS and pMOS groups
 - Parallel-connected nMOS
 - OR-NOT operations
 - Parallel-connected pMOS
 - AND-NOT operations
 - Series-connected nMOS
 - AND-NOT operations
 - Series-connected pMOS
 - OR-NOT operations
- Consequently, wired groups of nMOS and pMOS are logical **duals** of another

Dual Property

- If an NMOS group yields a function of the form

$$g = \overline{a \cdot (b + c)}$$

then an identically wired PMOS array gives the dual function


$$G = \overline{a + (b \cdot c)}$$

where the AND and OR operations have been interchanged

- This is an interesting property of NMOS-PMOS logic that can be exploited in some CMOS designs


An Example of Structured Design

□ $X = \overline{a + b \cdot (c + d)}$

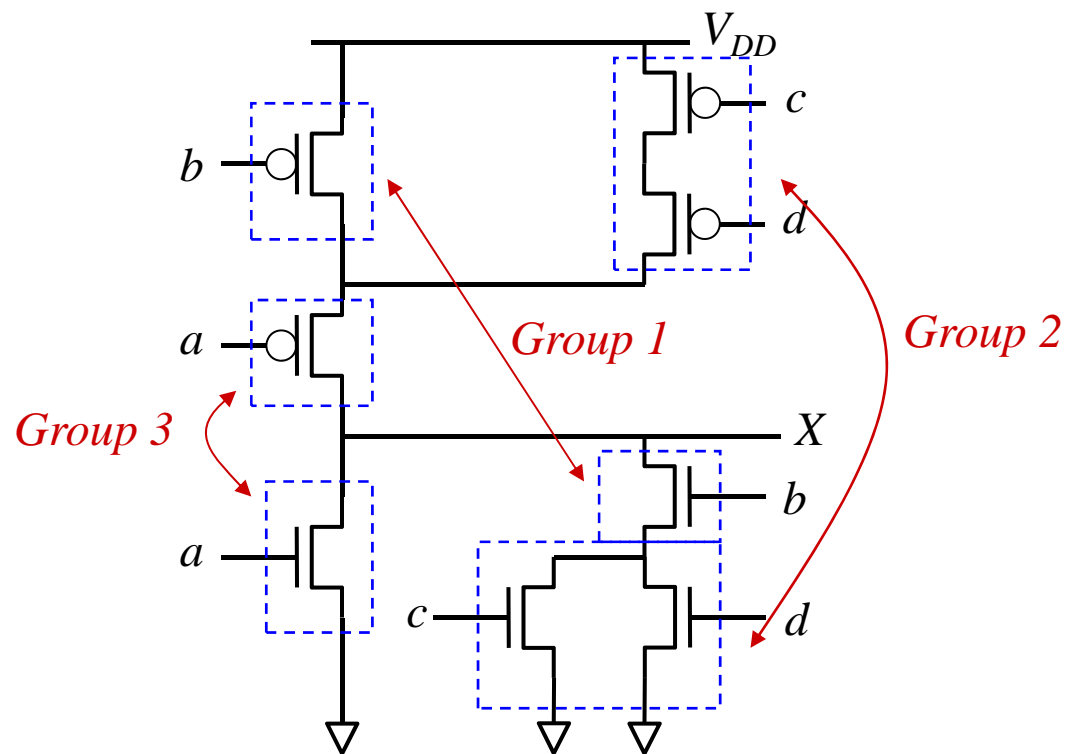


An Example of XOR Gate

 - Boolean equation of the two input XOR gate
 - $a \oplus b = \bar{a} \cdot b + a \cdot \bar{b}$, this is not in AOI form
 - But, $\overline{a \oplus b} = a \cdot b + \bar{a} \cdot \bar{b}$, this is in AOI form
 - Therefore, $a \oplus b = \overline{\overline{a \oplus b}} = \overline{a \cdot b + \bar{a} \cdot \bar{b}}$




XOR Gate

 

XNOR Gate


Multiplexer

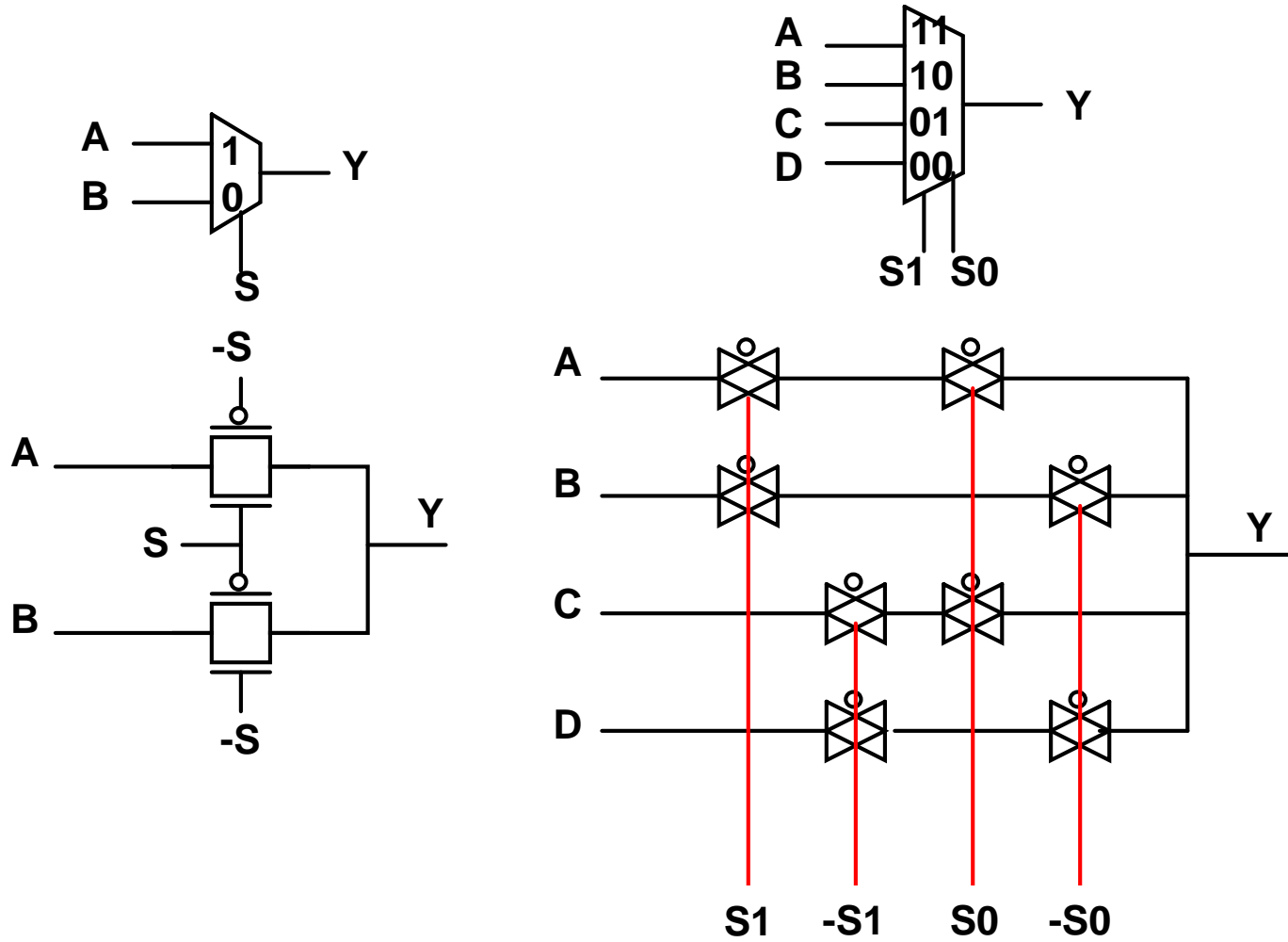

Static CMOS Summary

- In static circuits at every point in time (except when switching), the output is connected to either V_{dd} or Gnd through a low resistance path
 - Fan-in of n (or n inputs) requires $2n$ (n N-type and n P-type) devices
- Non-ratioed logic: gates operate independent of PMOS or NMOS sizes
- No path ever exists between V_{dd} and Gnd : low static power
- Fully-restored logic (NMOS passes "0" only and PMOS passes "1" only)
- Gates must be inverting

Design Flow for a VLSI Chip

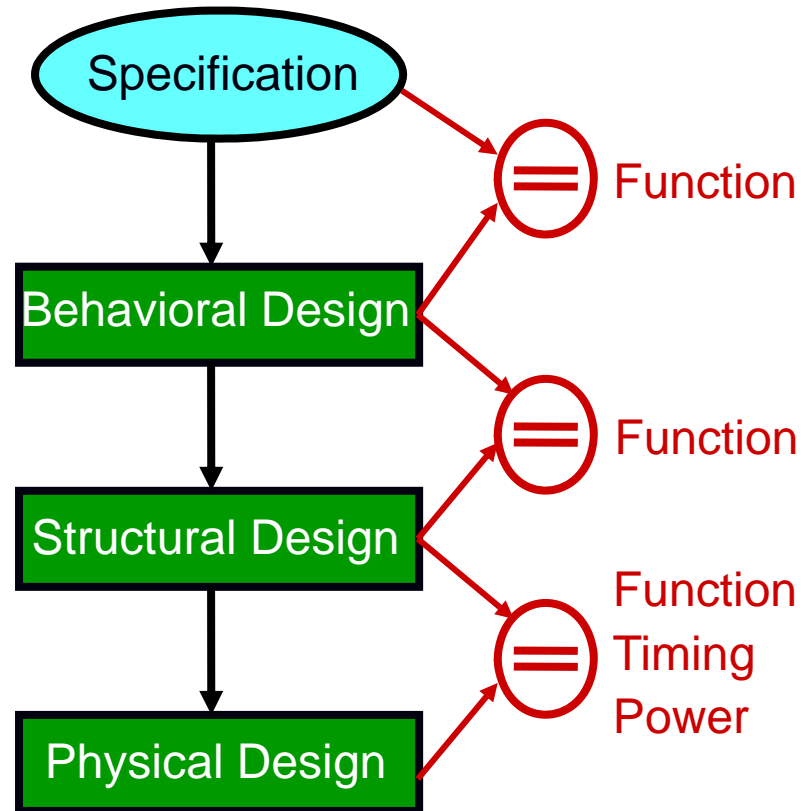

Circuit and System Representations

□ Behavioral representation

- Functional, high level
- For documentation, simulation, verification

□ Structural representation

- System level - CPU, RAM, I/O
- Functional level - ALU, Multiplier, Adder
- Gate level - AND, OR, XOR
- Circuit level - Transistors, R, L, C
- For design & simulation

□ Physical representation

- For fabrication

Behavior Representation

□ A one-bit full adder (Verilog)

```
module fadder(sum,cout,a,b,ci);
```

```
output sum, cout;
```

```
input a, b, ci;
```

```
reg sum, cout;
```


```
always @(a or b or ci) begin
```

```
    sum = a^b^ci;
```

```
    cout = (a&b)|(b&ci)|(ci&a);
```

```
end
```


```
endmodule
```

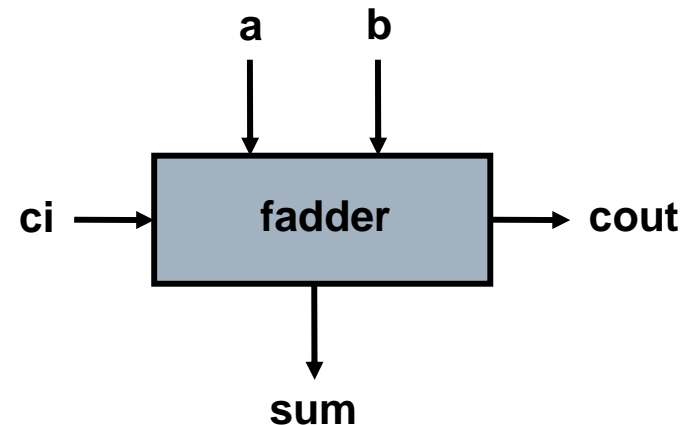

Structure Representation

□ A four-bit full adder (Verilog)
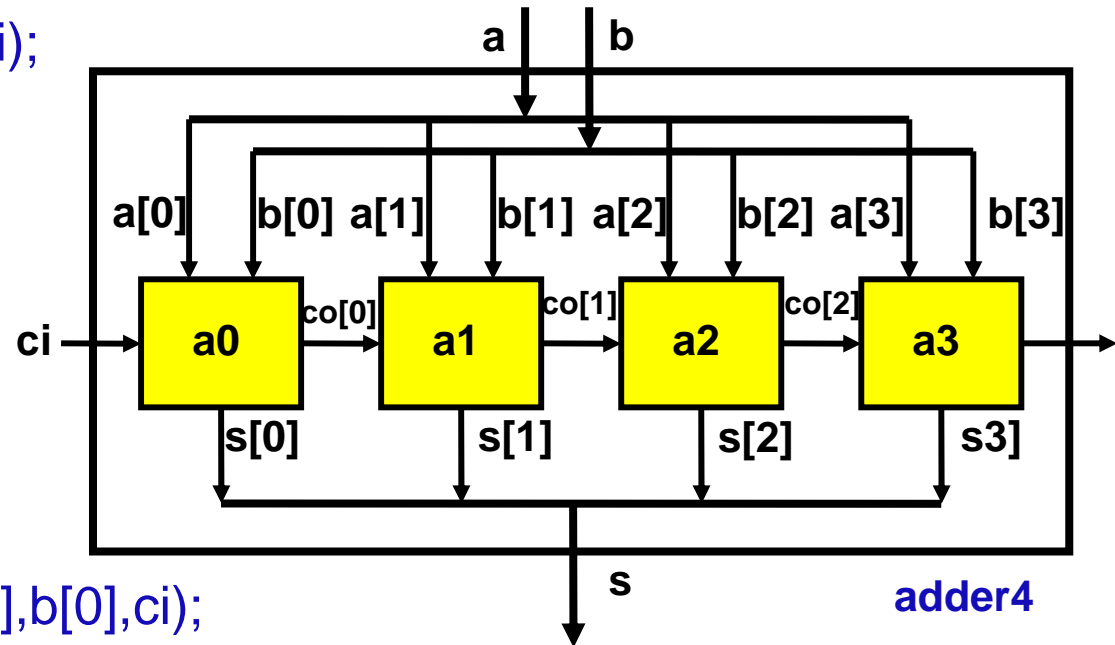
```
module adder4(s,c4,a,b,ci);
output[3:0] sum;
output c4;
input[3:0] a, b;
input ci;
reg[3:0] s;
reg c4;
wire[2:0] co;
    fadder a0(s[0],co[0],a[0],b[0],ci);
    fadder a1(s[1],co[1],a[1],b[1],co[0]);
    fadder a2(s[2],co[2],a[2],b[2],co[1]);
    fadder a3(s[3],c4,a[3],b[3],co[2]);
endmodule
```



Physical Representation

- Layout of a 4-bit NAND gate

