



## Chapter 3

---

# Gate-Level Minimization

3-1



## Outline

---

- Karnaugh Map Method
- NAND and NOR Implementations
- Other Two-Level Implementations
- Exclusive-OR Function
- Hardware Description Language

3-2

## Why Logic Minimization ?

- Minimize the number of gates used
  - Reduce gate count = reduce cost
- Minimize total delay (critical path delay)
  - Reduce delay = improve performance
- Satisfy design constraints
  - Maximum fanins and fanouts, ...
- Remove undesired circuit behavior
  - Hazard, race, ...

3-3


## The Map Method

- The map method is also known as the **Karnaugh map** or **K-map**
- Provide a straightforward procedure for minimizing Boolean functions
- The simplified expressions are always in one of the two standard forms:
  - Sum of Products (SOP)
  - Product of Sums (POS)


3-4
 
## Two-Variable Map (1/2)

- Two-variable function has **four** minterms
  - Four squares in the map for those minterms
- The corresponding minterm of each square is determined by the bit status shown outside




(a)

 


(b)

3-5

## Two-Variable Map (2/2)

 

(a)  $xy$

 


(b)  $x + y$

$$\begin{aligned}
 x + y &= x(y+y') + y(x+x') \\
 &= xy (m_3) + xy' (m_2) + x'y (m_1) \\
 &= m_1 + m_2 + m_3
 \end{aligned}$$

3-6

## Three-Variable Map (1/2)

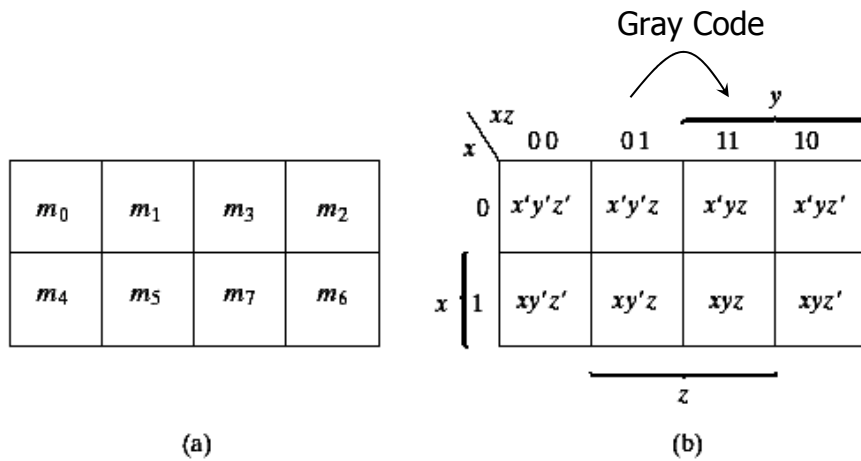


3-7
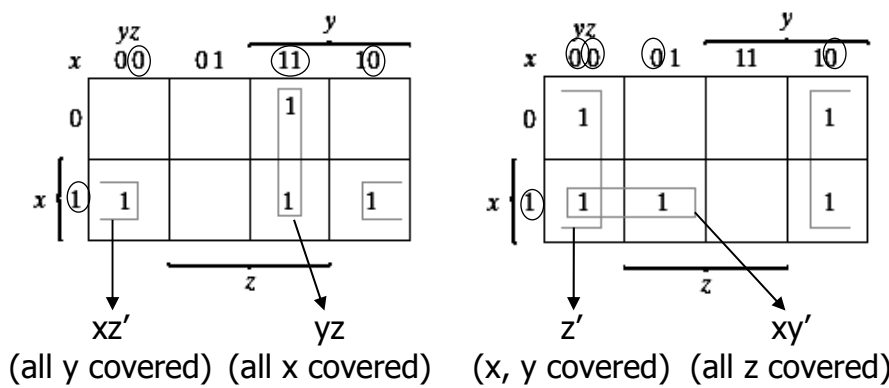
## Three-Variable Map (2/2)

$$F(x, y, z) = \sum(3,4,6,7) = yz + xz'$$

$$F(x, y, z) = \sum(0,2,4,5,6) = z' + xy'$$




3-8

## Four-Variable Map (1/2)

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$

(a)

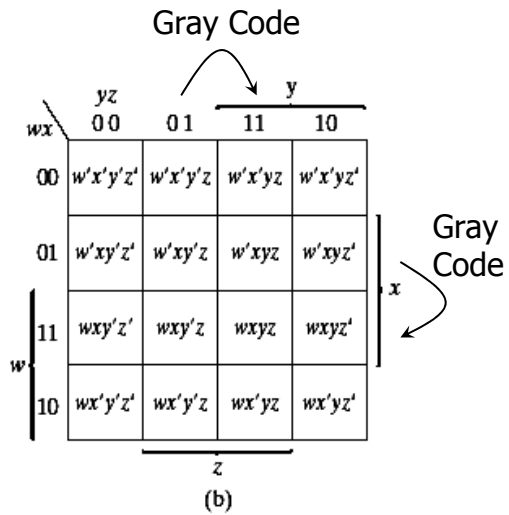


(b)

3-9

## Four-Variable Map (2/2)


$$F = A'B'C' + B'CD' + A'BCD' + AB'C' = \sum(0,1,2,6,8,9,10)$$

$$= B'D' + B'C' + A'CD'$$

 

3-10

## Five-Variable Map (1/2)

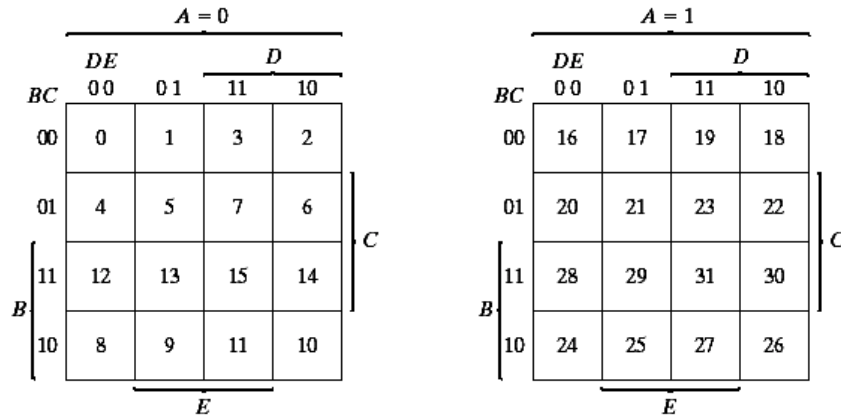


\* Maps with six or more variables need too many squares and are impractical to use.

3-11

## Five-Variable Map (2/2)

$$F(A,B,C,D,E) = (0,2,4,6,9,13,21,23,25,29,31)$$


$$= A'B'E' + BD'E + ACE$$

 

3-12
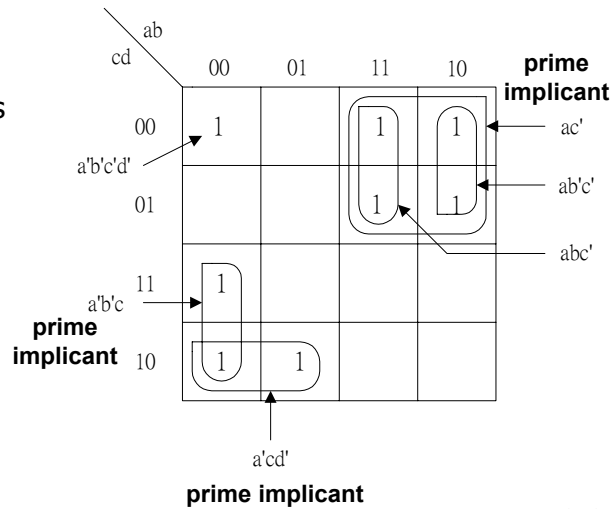
## Prime Implicants


- **Implicant (cube) :**  
A group of minterms that form a cube
- **Prime implicant :**  
Combine maximum possible number of adjacent squares in the map



3-13
 
## Essential Prime Implicants

- If a minterm is covered by only one prime implicant, that prime implicant is **essential** and must be included




Note: 1's in red color are covered by only one prime implicant. All other 1's are covered by at least two prime implicants


3-14
 
## Systematic Simplification

- Identify all prime implicants on the k-map
- Select all essential prime implicants
- Select a minimum subset of the remaining prime implicants that cover all 1's
- Ex:  $F(A, B, C, D) = \sum(0,2,3,5,7,8,9,10,11,13,15)$



 (a) Essential prime implicants  $BD$  and  $B'D'$



(b) Prime implicants  $CD$ ,  $B'C$ ,  $AD$ , and  $AB'$


$$F = BD + B'D'$$

$$+ \begin{cases} CD + AD \\ CD + AB' \\ B'C + AD \\ B'C + AB' \end{cases}$$

3-15
 
## Product of Sums Simplification

- The complement of a function is represented in the map by the squares not marked by 1's
  - Choose 1  $\rightarrow$  sum of products (minterms)
  - Choose 0  $\rightarrow$  product of sums (Maxterms)



$$F(A, B, C, D) = \sum(0,1,2,5,8,9,10)$$

$$= B'D' + B'C + A'C'D$$

$$= (A' + B')(C' + D')(B' + D)$$


3-16



## Two Gate Implementations


- Sometimes product-of-sums representations may have smaller implementations

7 literals, 4 gates

 

$$(a) F = B'D' + B'C' + A'C'D$$

6 literals, 4 gates

 


$$(b) F = (A' + B')(C' + D')(B + D)$$

Fig. 3-15 Gate Implementation of the Function of Example 3-8

3-17
 
## Don't Care Conditions

- X = don't care (can be 0 or 1)
- Don't cares can be included to form a larger cube, but not necessary to be completely covered
- Ex:  $F(w, x, y, z) = \sum(1,3,7,11,15)$   $d(w, x, y, z) = \sum(0,2,5)$



3-18


## Outline

- Karnaugh Map Method
- **NAND and NOR Implementations**
- Other Two-Level Implementations
- Exclusive-OR Function
- Hardware Description Language

3-19
 
## NAND and NOR Implementation


- Digital circuits are frequently constructed with **NAND** or **NOR** gates rather than with AND and OR gate
  - NAND and NOR gates are much easier to fabricate
- NAND or NOR gates are both universal gates
  - Any digital system can be implemented with only NAND gates or NOR gates



3-20
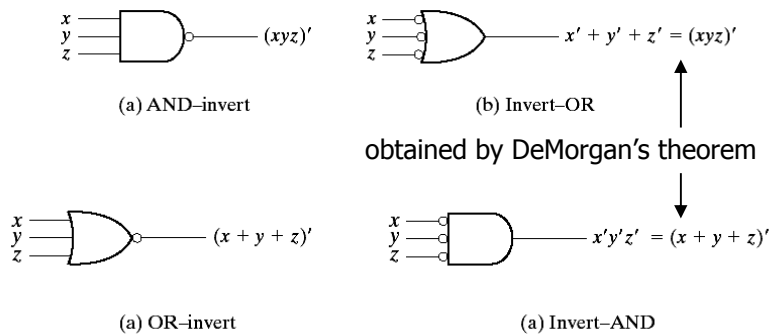
## Alternative Graphic Symbols


- To facilitate the conversion to NAND or NOR logic, it is convenient to define alternative graphic symbols
  - “Bubble” means complement



3-21
 
## Two-Level Implementation (NAND)

- It's easy to implement a Boolean function with only NAND gates if converted from a **sum of products** form
- Ex:  $F = AB + CD = ((AB)')(CD)'$






3-22

## Example 3-10

$$F(x, y, z) = \sum(1, 2, 3, 4, 5, 7)$$

Procedures:

   
1. Simplify the function in sum of products
2. Draw NAND gates for the first level
3. Draw a single AND-invert or invert-OR in the second level
4. Add an inverter at the first level for the term with a single literal



3-23
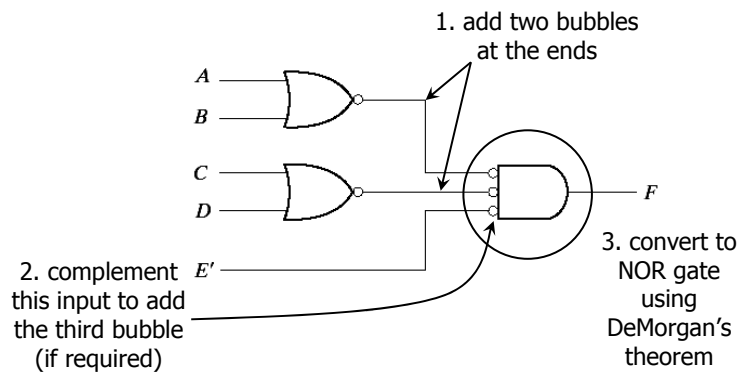
## Two-Level Implementation (NOR)

- It's easy to implement a Boolean function with only NOR gates if converted from a **product of sums** form
- Ex:  $F = (A+B)(C+D)E$




3-24

# Multilevel NAND Circuits


$$F = A(CD + B) + BC'$$

■ Procedures:

 1. Convert all AND gates to NAND gates with AND-invert symbols
2. Convert all OR gates to NAND gates with invert-OR symbols
3. Check all bubbles and insert an inverter for the bubble that are not compensated by another bubble



(a) AND-OR gates

 


(a) NAND gates

3-25


# Multilevel NOR Circuits

- For NOR gates, AND → invert-AND, OR → OR-invert
- Other procedures are the same as those for NAND

$$F = (AB' + A'B)(C + D')$$

 

(a) AND-OR gates

 

(b) NAND gates

 


Fig. 3-27 Implementing  $F = (AB' + A'B)(C + D')$  with NOR Gates

3-26


## Outline

- Karnaugh Map Method
- NAND and NOR Implementations
- Other Two-Level Implementations
- Exclusive-OR Function
- Hardware Description Language

3-27

 
## Wired Logic

- Wired logic: direct wire connection that results in a specific logic function
  - Wired-AND
  - Wired-OR
- Some NAND and NOR implementations (not all) have such a property



(a) Wired-AND in open-collector TTL NAND gates.

(AND-OR-INVERT)

 


(b) Wired-OR in ECL gates

(OR-AND-INVERT)

3-28
 
## Nondegenerate Forms


- There are 16 possible combinations of two-level forms
  - Eight of these combinations will degenerate to a single operation
- The other eight **nondegenerate** forms produce an implementation in SOP or POS



3-29
 
## AND-OR-INVERT Implementation


- NAND-AND and AND-NOR are equivalent and both perform the AND-OR-INVERT (**AOI**) function
- Require sum-of-products form in nature
  - When starting from product-of-sums form, complement it using DeMorgan's theorem to obtain sum-of-products form
- Ex:  $F = (AB + CD + E)'$




3-30
 
## OR-AND-INVERT Implementation


- OR-NAND and NOR-OR are equivalent and both perform the OR-AND-INVERT (**OAI**) function
- Require product-of-sums form in nature
  - When starting from sum-of-products form, complement it using DeMorgan's theorem to obtain product-of-sums form
- Ex:  $F = [(A+B)(C+D)E]'$



(a) OR-NAND

 

(b) OR-NAND

 

(c) NOR-OR

3-31

## Implement with Two-Level Forms

**Table 3-3**  
Implementation with Other Two-Level Forms

Equivalent Nondegenerate Form		Implements the Function	Simplify $F'$ in	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum of products by combining 0's in the map	$F$
OR-NAND	NOR-OR	OR-AND-INVERT	Product of sums by combining 1's in the map and then complementing	$F$

\*Form (b) requires an inverter for a single literal term.

3-32



## Example 3-11

- $F = x'y'z' + xyz'$   
 (choose 1 in K-map)  
 $= (x'y + xy' + z)'$   
 (choose 0 in K-map)


	yz		y	
	00	01	11	10
x				
0	1	0	0	0
1	0	0	0	1
	z			

$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$


(a) Map simplification in sum of products.

**choose 0**

 

AND-NOR  
NAND-AND  
(b)  $F = (x'y + xy' + z)'$

**choose 1**

 

OR-NAND  
NOR-OR  
(c)  $F = [(x + y + z)(x' + y' + z)]'$

3-33

## Outline

- Karnaugh Map Method
- NAND and NOR Implementations
- Other Two-Level Implementations
- **Exclusive-OR Function**
- Hardware Description Language


3-34

## Exclusive-OR (XOR) Function


- XOR is often denoted by the symbol  $\oplus$
- Logic operation of XOR
  - $X \oplus Y = XY' + X'Y$
  - Equal to 1 if **only x** is equal to 1 or if **only y** is equal to 1, but not when both are equal to 1
- Its complement, exclusive-NOR (XNOR), is often denoted by the symbol  $\odot$
- Logic operation
  - $X \odot Y = XY + X'Y'$
  - It is equal to 1 if **both x and y** are equal to 1 or if both are equal to 0
- Seldom used in general Boolean functions
  - Particularly useful in arithmetic operations and error detection and correction circuits

3-35

## Exclusive-OR Implementations

 

(a) With AND-OR-NOT gates

 


(b) With NAND gates

3-36


## Odd Function

- The multiple-variable XOR operation is defined as an **odd function**
  - TRUE when no. of "1" in inputs is odd

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

(a) 3-input odd function

 


(a) Odd function  
 $F = A \oplus B \oplus C$

3-37


## Even Function

- The multiple-variable XNOR operation is defined as an **even function**
  - TRUE when no. of "1" in inputs is even

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 

(b) 3-input even function

 

(a) Even function  
 $F = (A \oplus B \oplus C)'$

3-38

## Four-Variable XOR Function

 


Fig. 3-35 Map for a Four-variable Exclusive-OR Function

3-39

## Parity Generation and Checking

- An extra **parity** bit is often added and checked at the receiving end for error
- The circuit that generates the parity bit in the transmitter is called a **parity generator**
- The circuit that checks the parity in the receiver is called a **parity checker**
- Exclusive-OR functions are very useful to construct such circuits


3-40

# Parity Generator

- For even parity:
  - The total number of “1” (including P) is even
  - The number of “1” at inputs is odd
  - Generated with an **XOR** gate (odd function)
  - $P = x \oplus y \oplus z$  (for 3-bit message)
- Similarly, odd parity can be generated with an XNOR gate

**Table 3-4**  
Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

(a) 3-bit even parity generator


3-41

# Parity Checker

- For even parity, the total number of “1” in the message is even
  - An error occurs when the received number of “1” is odd
- An XOR gate (odd function) can detect such an error
  - Has n+1 inputs

**Table 3-5**  
Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check
x	y	z	P	C
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 

(a) 4-bit even parity checker

3-42

## Outline

- Karnaugh Map Method
- NAND and NOR Implementations
- Other Two-Level Implementations
- Exclusive-OR Function
- Hardware Description Language

3-43

## Hardware Description Language

- Have high-level language constructs to describe the functionality and connectivity of the circuit
- Can describe a design at some levels of abstraction
  - Behavioral, RTL, Gate-level, Switch
- Can describe functionality as well as timing
- Can model the concurrent actions in real hardware
- Can be used to document the complete system design tasks
  - testing, simulation ... related activities
- Comprehensive and easy to learn
- Two popular languages: Verilog & VHDL
  - Will be taught in another course

3-44

## Why Use an HDL ?

- Hard to design directly for complex systems
- Formal description using HDL
  - Verify the specification through simulation or verification
  - Easy to change
  - Enable automatic synthesis
- Allow architectural tradeoffs with short turnaround
- Reduce time for design capture
- Encourage focus on functionality
- Shorten the design verification loop

\*HDL = Hardware Description Language

3-45