

Chapter 4

Combinational Logic

4-1

Outline

- **Combinational Circuits**
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers

4-2

Combinational v.s Sequential Circuits

- Logic circuits may be **combinational** or **sequential**
- Combinational circuits:
 - Consist of **logic gates** only
 - Outputs are determined from the present values of inputs
 - Operations can be specified by a set of Boolean functions
- Sequential circuits:
 - Consist of **logic gates** and **storage elements**
 - Outputs are a function of the inputs and the state of the storage elements
 - Depend not only on present inputs, but also on past values
 - Circuit behavior must be specified by a time sequence of inputs and internal states

4-3

Combinational Circuit (1/2)

- A combinational circuit consists of
 - Input variables
 - Logic gates
 - Output variables

 


Fig. 4-1 Block Diagram of Combinational Circuit

4-4

Combinational Circuit (2/2)

- Each input and output variable is a binary signal
 - Represent logic 1 and logic 0
- There are 2^n possible binary input combinations for n input variable
- Only one possible output value for each possible input combination
- Can be specified with a truth table
- Can also be described by m Boolean functions, one for each output variable
 - Each output function is expressed in terms of n input variables

4-5

Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers

4-6

Analysis Procedure


- Analysis: determine the function that the circuit implements
 - Often start with a given logic diagram
- The analysis can be performed by
 - Manually finding Boolean functions
 - Manually finding truth table
 - Using a computer simulation program
- First step: make sure that circuit is combinational
 - Without feedback paths or memory elements
- Second step: obtain the output Boolean functions or the truth table

4-7

Output Boolean Functions (1/3)

Step 1:

 - Label all gate outputs that are a function of input variables
- Determine Boolean functions for each gate output




$$\begin{aligned} F_2 &= AB + AC + BC \\ T_1 &= A + B + C \\ T_2 &= ABC \end{aligned}$$

4-8

Output Boolean Functions (2/3)

Step 2:

 - Label the gates that are a function of input variables and previously labeled gates
- Find the Boolean function for these gates



4-9

Output Boolean Functions (3/3)

Step 3:

- Obtain the output Boolean function in term of input variables
 - By repeated substitution of previously defined functions

$$\begin{aligned}
 F_1 &= T_3 + T_2 = F_2' T_1 + ABC \\
 &= (AB + AC + BC)' (A + B + C) + ABC \\
 &= (A' + B')(A' + C')(B' + C') (A + B + C) + ABC \\
 &= (A' + B' C')(AB' + AC' + BC' + B' C) + ABC \\
 &= A' BC' + A' B' C + AB' C' + ABC
 \end{aligned}$$

4-10

Truth Table

- To obtain the truth table from the logic diagram:
 1. Determine the number of input variables

For n inputs:

 - 2^n possible combinations
 - List the binary numbers from 0 to 2^n-1 in a table
 2. Label the outputs of selected gates
 3. Obtain the truth table for the outputs of those gates that are a function of the input variables only
 4. Obtain the truth table for those gates that are a function of previously defined variables at step 3
 - Repeatedly until all outputs are determined

4-11

Truth Table for Fig. 4-2

A	B	C	F ₂	F ₂	T ₁	T ₂	T ₃	F ₁
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

4-12

Design Procedure

- Design procedure:
 - Input: the specification of the problem
 - Output: the logic circuit diagram (or Boolean functions)
- Step 1: determine the required number of inputs and outputs from the specification
- Step 2: derive the truth table that defines the required relationship between inputs and outputs
- Step 3: obtain the simplified Boolean function for each output as a function of the input variables
- Step 4: draw the logic diagram and verify the correctness of the design

4-13

Code Conversion Example


- Convert from BCD code to Excess-3 code
- The 6 input combinations not listed are don't cares
- These values have no meaning in BCD
- We can arbitrary assign them to 1 or 0

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

4-14


Maps for Code Converter (1/2)

 - The six don't care minterms (10~15) are marked with X



4-15

Maps for Code Converter (2/2)

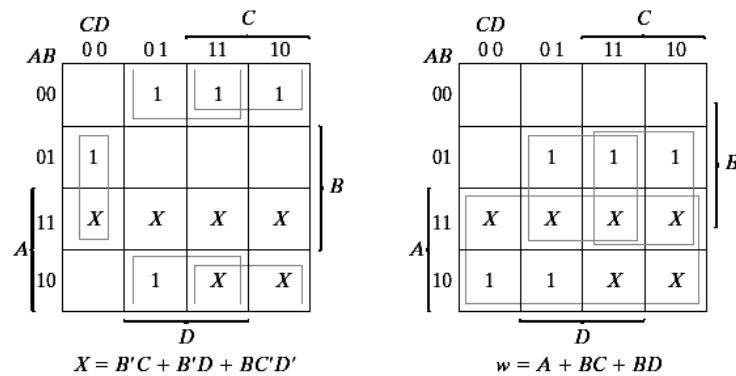

4-16


Logic Diagram for the Converter

- There are various possibilities for a logic diagram that implements a circuit
- A two-level logic diagram may be obtained directly from the Boolean expressions derived by the maps
- The expressions may be manipulated algebraically to use common gates for two or more outputs
 - Reduce the number of gates used

$$\begin{aligned}
 z &= D' \\
 y &= CD + C' D' = CD + (C + D)' \\
 x &= B'C + B'D + BC' D' = B' (C + D) + BC' D' \\
 &= B' (C + D) + B(C + D)' \\
 w &= A + BC + BD = A + B(C + D)
 \end{aligned}$$

4-17

Logic Diagram for the Converter

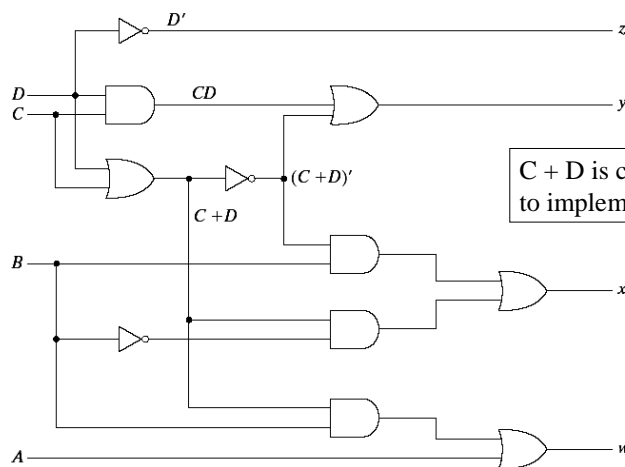

4-18



Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers

4-19



Adder

- The most basic arithmetic operation is the addition of two binary digits
 - When both augend and addend bits are equal to 1, the binary sum consists of two digits ($1 + 1 = 10$)
 - The higher significant bit of this result is called a **carry**
- A combination circuit that performs the addition of two bits is **half adder**
- An adder performs the addition of 2 significant bits and a previous carry is called a **full adder**

4-20

Half Adder

- Half adder
 - Inputs: x and y
 - Outputs: S (for sum) and C (for carry)


x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = x'y + xy'$$


$$C = xy$$

4-21

Implementation of a Half Adder

 

(a) $S = xy' + x'y$
 $C = xy$

 


(b) $S = x \oplus y$
 $C = xy$

4-22


Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 x, y: the two significant bits to be added
z: the carry from the previous position



$$S = x'y'z + x'yz' + xy'z' + xyz$$

 


$$C = xy + xz + yz$$


$$= xy + xy'z + x'yz$$

4-23

Implementation of a Full Adder

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 


$$C = xy + xz + yz$$

4-24

Implementation of a Full Adder

 - A full adder can be implemented with two half adders and an OR gate




$$\begin{aligned}
 S &= z \oplus (x \oplus y) \\
 &= z'(xy' + x'y) + z(xy' + x'y)' \\
 &= z'(xy' + x'y) + z(xy + x'y') \\
 &= xy'z' + x'yz' + xyz + x'y'z
 \end{aligned}$$

$$\begin{aligned}
 C &= z(xy' + x'y) + xy \\
 &= xy'z + x'yz + xy \\
 &= xy'z + x'yz + xyz + xyz' \\
 &= xz + yz + xy
 \end{aligned}$$

4-25

Binary Adder

 - A binary adder produces the arithmetic sum of two binary numbers
- Can be constructed with full adders connected in cascade
 - The output carry from each full adder is connected to input carry of the next full adder in the chain
 - n-bit binary **ripple carry adder** is connected by n FAs



4-26

4-bit Adder Example

- Consider two binary number $A = 1011$ and $B = 0011$

Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

4-27


Carry Propagation

- As in a combinational circuit, the signal must propagate through the gates before the correct output sum is available in the output terminals
- The total propagation time is equal to the propagation delay of a typical gate times the number of levels in the circuit
- The longest propagation delay in an adder is the time that carry propagate through the full adders
- Each bit of the sum output depends on the value of the input carry
 - The value of S_i will be in final value only after the input carry C_i has been propagated

4-28

Full Adder with P and G

 - The full adder can be redrawn with two internal signals P (propagation) and G (generation)
- The signal from input carry C_i to output carry C_{i+1} propagates through an AND and a OR gate (2 gate levels)
 - For n-bit adder, there are $2n$ gate levels for the carry to propagate from input to output




4-29

Carry Propagation

- The **carry propagation time** is a limiting factor on the speed with which two numbers are added
- All other arithmetic operations are implemented by successive additions
 - The time consumed during the addition is very critical
- To reduce the carry propagation delay
 - Employ faster gates with reduced delays
 - Increase the equipment complexity
- Several techniques for reducing the carry propagation time in a parallel adder
 - The most widely used technique employs the principle of **carry lookahead**

4-30

Carry Propagation & Generation

 

carry propagate : $P_i = A_i \oplus B_i$


carry generate : $G_i = A_i B_i$

$S_i = P_i \oplus C_i$

$C_{i+1} = G_i + P_i C_i$

4-31

Carry Lookahead Generator

 

$C_0 = \text{input carry}$

$C_1 = G_0 + P_0 C_0$

$C_2 = G_1 + P_1 C_1$

$= G_1 + P_1(G_0 + P_0 C_0)$


$= G_1 + P_1 G_0 + P_1 P_0 C_0$

$C_3 = G_2 + P_2 C_2$

$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

4-32

Carry Lookahead Adder

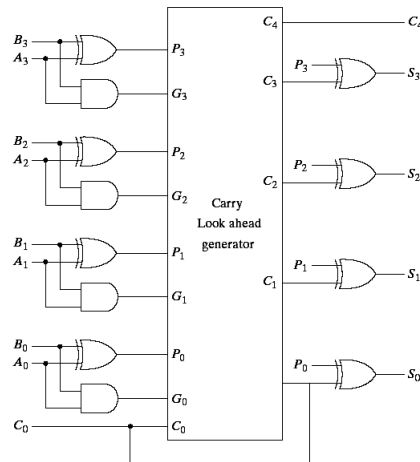

- All output carries are generated after a delay through two levels of gates
- Output S1 to S3 can have equal propagation delay times

4-33

Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- **Other Arithmetic Circuits**
- Decoders and Encoders
- Multiplexers

4-34

Binary Subtractor


- $A - B$ can be done by taking the 2's complement of B and adding it to A ---> $A - B = A + (-B)$
 - 2's complement can be obtained by taking the 1's complement and adding on to the least significant pair of bits
 - $A - B = A + (B' + 1)$
- The circuit for subtraction $A - B$ consists of an adder with inverter placed between each data input B and the corresponding input of the full adder
- The input carry C_0 must be equal to 1

4-35

4-bit Adder-Subtractor

- $M=0$ (Adder)
 - Input of FA is A and B ($B \oplus 0 = B$), and C_0 is 0
- $M=1$ (Subtractor)
 - Input of FA is A and B' ($B \oplus 1 = B'$), and C_0 is 1

x	y	$x \oplus y$	
0	0	0	y
0	1	1	
1	0	1	y'
1	1	0	

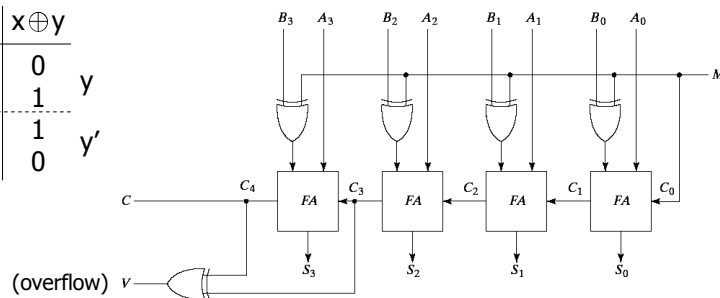

4-36

Overflow

- An overflow occurs when two number of n digits each are added and the sum occupies $n+1$ digits
- When two unsigned numbers are added, an overflow is detected from the end carry out of the most significant position
- When two signed numbers are added, the sign bit is treated as part of the number and the end carry does not indicate an overflow
 - Extra overflow detection circuits are required
- An overflow can only occur when two numbers added are **both positive** or **both negative**

4-37

Overflow Example

The two carry bits are different !!


Carries : 0	1		Carries : 1	0
+70	0	1000110	-70	1 0111010
+80	0	1010000	-80	1 0110000
-----	-----		-----	-----
+150	1	0010110 (-106)	-150	0 1101010 (+106)
(010010110)			(101101010)	

Overflow

4-38

Overflow Detection

 
- An overflow condition can be detected by observing the carry into the sign bit position and the carry out of the sign bit position
 - If these two carries are not equal, and overflow has occurred
 - If the output V is equal to 1, an overflow is detected



4-39

Adder-Subtractor Circuit

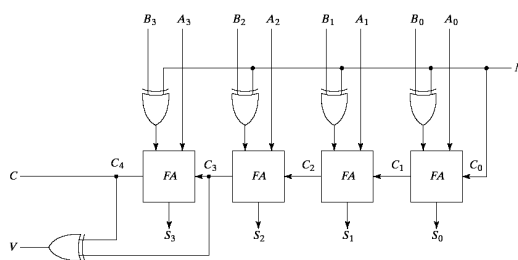- Unsigned
 - C bit detects a **carry** after addition or a **borrow** after subtraction
- Signed
 - V bit detects an overflow
 - 0: no overflow; 1: overflow



4-40

Decimal Adder

- A decimal adder requires a minimum of 9 inputs and 5 outputs
 - 1 digit requires 4-bit
 - Input: 2 digits + 1-bit carry
 - Output: 1 digit + 1-bit carry
- BCD adder
 - Perform the addition of two decimal digits in BCD, together with an input carry from a previous stage
 - The output sum cannot be greater than 19 (9+9+1)

4-41

Derivation of BCD Adder

Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
.....				
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

4-42

BCD Adder


- When the binary sum is equal to or less than 1001_b
 - BCD Sum = Binary Sum
 - $C = 0$
- When the binary sum is greater than 1001_b
 - BCD Sum = Binary Sum + 0110_b
 - $C = 1$

	Z_8Z_4			
Z_2Z_1	00	01	11	10
00			1	
01			1	
11			1	1
10			1	1

$$C = K + Z_8Z_4 + Z_8Z_2$$


4-43

Block Diagram of a BCD Adder

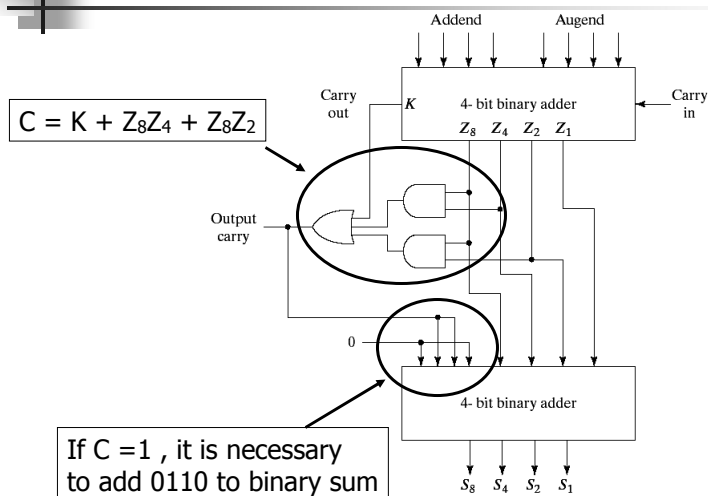


4-44

Binary Multiplier

 


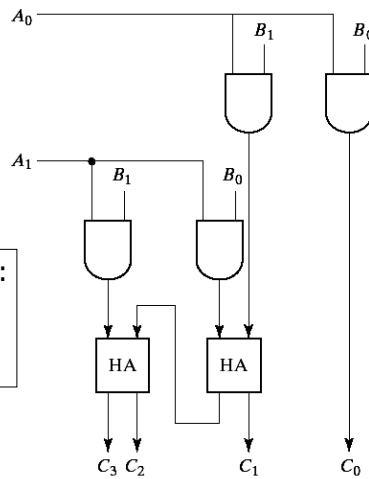For a $J \times K$ bits multiplier, we need:
 $(J \times K)$ AND gates
 $(J - 1)$ K-bit adders
to produce a product of $J+K$ bits



4-45

4-Bit By 3-Bit Binary Multiplier

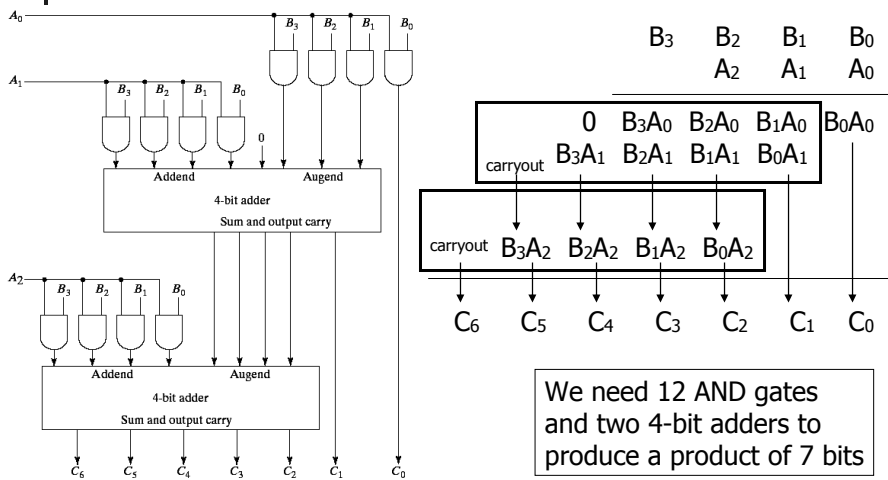

We need 12 AND gates
and two 4-bit adders
to produce a product of 7 bits

4-46

Magnitude Comparator

- Equal (A = B)

- $A_3=B_3$ and $A_2=B_2$ and $A_1=B_1$ and $A_0=B_0$

$$X_i = A_i B_i + A_i' B_i' \text{ for } i = 0, 1, 2, 3$$

$X_i = 1$ means
A_i and B_i are equal !!

- $(A=B) = X_3 X_2 X_1 X_0$

- Greater (A > B) or Less (A < B)


- Comparison start from the MSB
 - If the two digits are equal, compare the next lower digits
 - Continues until a pair of unequal digits is reached
 - A is 1 and B is 0 => A > B
 - A is 0 and B is 1 => A < B

$$(A > B) = A_3 B_3' + X_3 A_2 B_2' + X_3 X_2 A_1 B_1' + X_3 X_2 X_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + X_3 A_2' B_2 + X_3 X_2 A_1' B_1 + X_3 X_2 X_1 A_0' B_0$$

4-47

4-Bit Magnitude Comparator

 

4-48



Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- **Decoders and Encoders**
- Multiplexers

4-49



Decoder


- A circuit that converts binary information from n input lines to a maximum of 2^n unique output lines
 - May have fewer than 2^n outputs
- A n -to- m -line decoder ($m \leq 2^n$):
 - Generate the m minterms of n input variables
- For each possible input combination, there is only one output that is equal to 1
 - The output whose value is equal to 1 represents the minterm equivalent of the binary number presently available in the input lines

4-50

3-to-8-Line Decoder

- The 3 inputs are decoded into 8 outputs
- Each represent one of the minterms of the inputs variables


Inputs			Outputs							
x	y	z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 

4-51

2-to-4-Line Decoder with Enable

 - Some decoders are constructed with NAND gates
 - Generate minterms in their complement form
- An **enable** input can be added to control the operation
 - E=1: disabled
 - None of the outputs are equal to 0




E	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

4-52

Demultiplexer

 - A circuit that receives information from a single line and directs it to one of 2^n possible output lines
- A decoder with enable input can function as a demultiplexer
 - Often referred to as a **decoder/demultiplexer**



4-53

Construct Larger Decoders

- Decoders with enable inputs can be connected together to form a larger decoder
- The enable input is used as the most significant bit of the selection signal
 - $w=0$: the top decoder is enabled
 - $w=1$: the bottom one is enabled
- In general, enable inputs are a convenient feature for standard components to expand their numbers of inputs and outputs


 


Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders

4-54

Combinational Logic Implementation

 - A decoder provides the 2^n minterms of n input variables
 - Can be used to form any combinational circuits with extra OR gates (sum of minterms)
- A function having a list of k minterms can be expressed in its complemented form F' with $2^n - k$ minterms
 - If $k > 2^n/2$, F' will have fewer minterms (fewer OR gates)
 - NOR gates are used instead for implementing F'



$$S(x,y,z) = \Sigma(1,2,4,7)$$

$$C(x,y,z) = \Sigma(3,5,6,7)$$

4-55

Encoder

- A circuit that performs the inverse operation of a decoder
 - Have 2^n (or fewer) input lines and n output lines
 - The output lines generate the binary code of the input positions
- Only one input can be active at any given time
- An extra output may be required to distinguish the cases that $D_0 = 1$ and all inputs are 0

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

4-56

Priority Encoder



- An encoder circuit that includes the priority function
- If two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence
- In the following truth table:
 - $D_3 > D_2 > D_1 > D_0$
 - The X's in output columns represent don't-care conditions
 - The X's in input columns are useful for representing a truth table in condensed form

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1


V = 0 :
no valid inputs

4-57

Implement a Priority Encoder

  

 $x = D_2 + D_3$
 $y = D_3 + D_1D'_2$
 $V = D_0 + D_1 + D_2 + D_3$



4-58


Outline

- Combinational Circuits
- Analysis and Design Procedures
- Binary Adders
- Other Arithmetic Circuits
- Decoders and Encoders
- Multiplexers


4-59

Multiplexer

 - A circuit that selects binary information from one of many input lines and directs it to a single output lines
 - Have 2^n input lines and n selection lines
 - Act like an electronic switch (also called a **data selector**)
- For the following 2-to-1-line multiplexer:
 - $S=0 \rightarrow Y = I_0$; $S=1 \rightarrow Y = I_1$



(a) Logic diagram

 


(b) Block diagram

4-60

4-to-1-Line Multiplexer

 - The combinations of S_0 and S_1 control each AND gates
- Part of the multiplexer resembles a decoder
- To construct a multiplexer:
 - Start with an n -to- 2^n decoder
 - Add 2^n input lines, one to each AND gate
 - The outputs of the AND gates are applied to a single OR gate




s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

4-61

Quadruple 2-to-1-Line Multiplexer

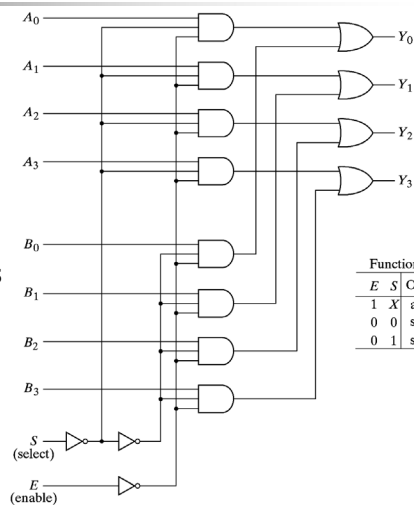- Multiplexers can be combined with **common selection inputs** to provide multiple-bit selection logic
- Quadruple 2-to-1-line multiplexer:
 - Four 2-to-1-line multiplexers
 - Each capable of selecting one bit of the 2 4-bit inputs
 - E: enable input
E=1: disable the circuit (all outputs are 0)



Function table		
E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B

4-62


Boolean Function Implementation

- A multiplexer is essentially a decoder with an external OR gate
 - Can be used to implement Boolean functions without extra logic
- To implement a Boolean function of n variables:
 - Use a multiplexer with $n - 1$ selection inputs
 - The first $n - 1$ variables are connected to the selection inputs
 - The remaining variable is used for the data inputs

$$F(x,y,z) = \Sigma(1,2,6,7)$$

x	y	z	F
0	0	0	0
0	0	1	1 $F = z$
0	1	0	1 $F = z'$
0	1	1	0
1	0	0	0 $F = 0$
1	0	1	0
1	1	0	1 $F = 1$
1	1	1	1 $F = 1$

(a) Truth table

 

(b) Multiplexer implementation


4-63

Implementing a 4-Input Function

$$F(A,B,C,D) = \Sigma(1,3,4,11,12,13,14,15)$$

logic 0: connected to ground
logic 1: connected to Vdd (5V)

A	B	C	D	F
0	0	0	0	0 $F = D$
0	0	0	1	1
0	0	1	0	0 $F = D$
0	0	1	1	1
0	1	0	0	1 $F = D'$
0	1	0	1	0
0	1	1	0	0 $F = 0$
0	1	1	1	0
1	0	0	0	0 $F = 0$
1	0	0	1	0
1	0	1	0	0 $F = D$
1	0	1	1	1
1	1	0	0	1 $F = 1$
1	1	0	1	1
1	1	1	0	1 $F = 1$
1	1	1	1	1

 

can be 0, 1, the variable, or its complement

4-64

Three-State Gate

- A circuit that exhibits three states
 - logic 1, logic 0, and **high-impedance (z)**
- The high-impedance state acts like an open circuit (disconnected)
- The most commonly used three-state gate is the buffer gate
 - $C=0 \rightarrow$ disabled (high-impedance) ; $C=1 \rightarrow$ enabled (pass)
 - Can be used at the output of a function without altering the internal implementation


 


Fig. 4-29 Graphic Symbol for a Three-State Buffer


4-65

Implementation with 3-State Gates

 - A large number of three-state gate outputs can be connected with wires to form a common line (bus) without logic conflicts
 - Very convenient for implementing some circuits (ex: multiplexer)
 - Only one buffer can be in the active state at any given time
- One way to ensure that no more than one control input is active at any given time is to use a decoder



(a) 2-to-1- line mux

 

(b) 4 - to - 1 line mux

4-66