



# Chapter 6

---

## Registers and Counters

6-1



## Outline

---

- Registers
- Shift Registers
- Ripple Counters
- Synchronous Counters
- Other Counters

6-2


## Registers and Counters

- Register:
  - A set of flip-flops, possibly with added combinational gates, that perform data-processing tasks
  - Store and manipulate information in a digital system
- Counter:
  - A register that goes through a predetermined sequence of states
    - A special type of register
  - Employed in circuits to sequence and control operations

6-3
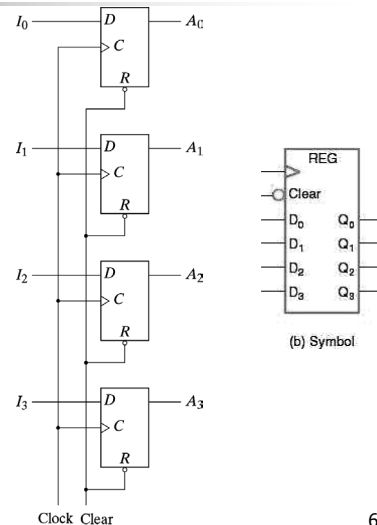
## The Simplest Register

- Consist of only flip-flops
- Triggered by common clock input
- The *Clear* input goes to the R (reset) input of all flip-flops
  - $Clear = 0 \rightarrow$  all flip-flops are reset **asynchronously**
- The *Clear* input is useful for cleaning the registers to all 0's prior to its clocked operation
  - Must maintain at logic 1 during normal operations



6-4

## Register with Parallel Load

- When  $Load = 1$ , all the bits of data inputs are transferred into the registers
  - Parallel loaded
- When  $Load = 0$ , the outputs of the flip-flops are connected to their respective inputs
  - Keep no change

control data loading at the input side

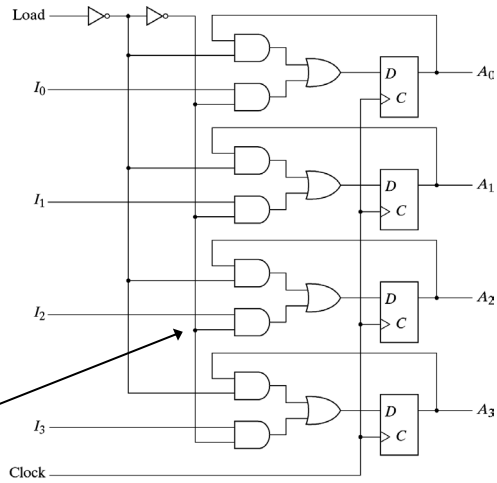


Fig. 6-2 4-Bit Register with Parallel Load

6-5

## Outline

- Registers
- Shift Registers
- Ripple Counters
- Synchronous Counters
- Other Counters

6-6

## The Simplest Shift Register

- Shift register: a register capable of shifting its binary information in one or both directions
- The simplest form: consist of only a chain of flip-flops in cascade


 


Fig. 6-3 4-Bit Shift Register

6-7
 
## Serial Transfer


- Serial mode: information is transferred and manipulated one bit at a time
- Parallel mode: all the bits of the registers are transferred at the same time
- Shift control: determine when and how many times of the registers are shifted
- Register A is connected in circular mode in this circuit



(a) Block diagram

6-8

## Serial Transfer Example

 


Timing Pulse	Shift Register A	Shift Register B
Initial value	1 0 1 1	0 0 1 0
After T1	1 1 0 1	1 0 0 1
After T2	1 1 1 0	1 1 0 0
After T3	0 1 1 1	0 1 1 0
After T4	1 0 1 1	1 0 1 1

6-9
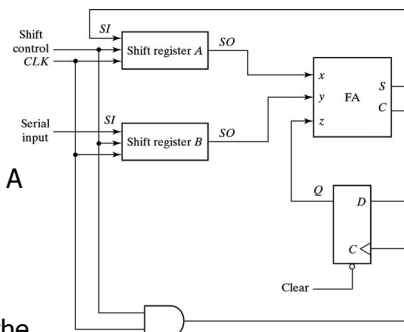
## Serial Adder

- The bits of two binary numbers are added one pair at a time through a single full adder (FA) circuit
- Initialization:
  - A = augend; B = addend
  - Carry flip-flop is cleared to 0
- For each clock pulse:
  - A new sum bit is transferred to A
  - A new carry is transferred to Q
  - Both registers are shifted right
- To add three or more numbers:
  - Shift in the next number from the serial input while B is shifted to the FA
  - A will accumulate their sum




6-10

## Serial v.s. Parallel

- Serial adders:
  - Use shift registers
  - A sequential circuit
  - Require only one FA and a carry flip-flop
  - Slower but require less equipment
- Parallel adders:
  - Use registers with parallel load for sum
  - Basically a pure combinational circuit
  - $n$  FAs are required
  - Faster

6-11

## Redesign the Serial Adder

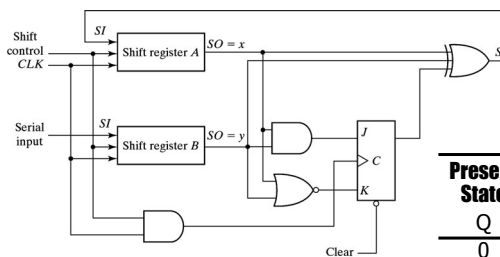

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

Present State	Inputs		Next State	Outputs	F/F Inputs	
Q	X	Y	Q	S	J <sub>Q</sub>	K <sub>Q</sub>
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0


6-12

# Universal Shift Register

- The most general shift register has the following capabilities:
  - A *clear* control to clear the register to 0
  - A *clock* input to synchronize the operations
  - A *shift-right (left)* control to enable the shift right (left) operation and the *serial input* and *output* lines associated with the shift right (left)
  - A *parallel-load* control to enable a parallel transfer and the *n* input lines associated with the parallel transfer
  - *n* parallel output lines
  - A control state that leaves the information in the register unchanged in the presence of the clock

6-13

# 4-Bit Universal Shift Register

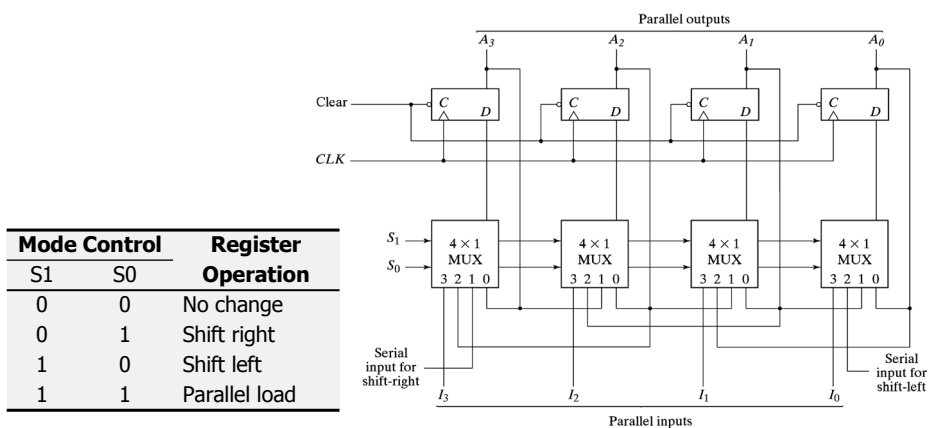


6-14

# Outline

- Registers
- Shift Registers
- **Ripple Counters**
- Synchronous Counters
- Other Counters

6-15

# Binary Ripple Counter

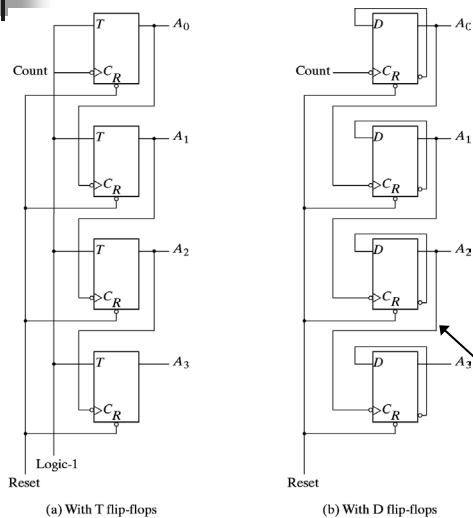

**Binary Count Sequence**

A3	A2	A1	A0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

the output transition triggers the next flip-flop

(a) With T flip-flops

(b) With D flip-flops

6-16



## BCD Ripple Counter

- The count will return to 0 after 9
- Q1: always complemented
- Q2: inverted when Q8 = 0 and Q1 = 1 → 0
- Q4: inverted when Q2 = 1 → 0
- Q8: when Q1 = 1 → 0  
if (Q2 = Q4 = 1) Q8 is inverted  
else Q8 = 0

 
 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

6-17

## Three-Decade BCD Counter

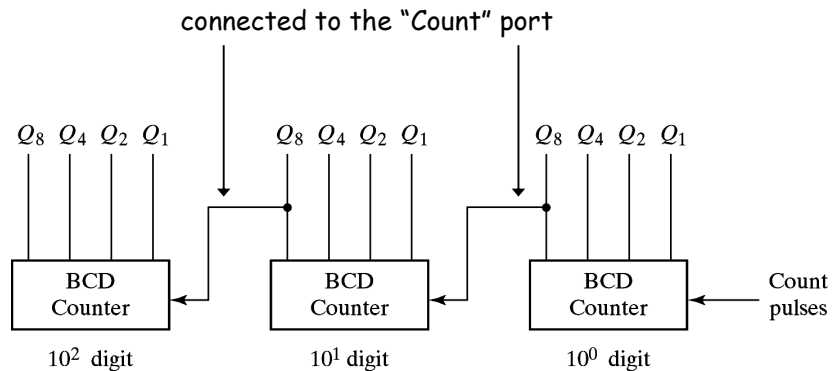


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

6-18



## Outline

---

- Registers
- Shift Registers
- Ripple Counters
- Synchronous Counters
- Other Counters

6-19



## Ripple v.s. Synchronous

---

- Ripple counters:
  - Flip-flops are triggered by the outputs of another flip-flops
    - Triggering source may not be the same for each flip-flop
  - The flip-flops are changed serially
- Synchronous counters:
  - Flip-flops are triggered by common clock pulses
    - Triggering sources are the same for all flip-flops
  - All operations are performed simultaneously

6-20


# Binary Counter

**J=0,K=0: no change**  
**J=1,K=1: complement**

0→1→...→15  
 →0→1→...

complemented when  
 all the lower bits are "1"  
 (checked by a AND chain)

triggered by  
 positive clock edge

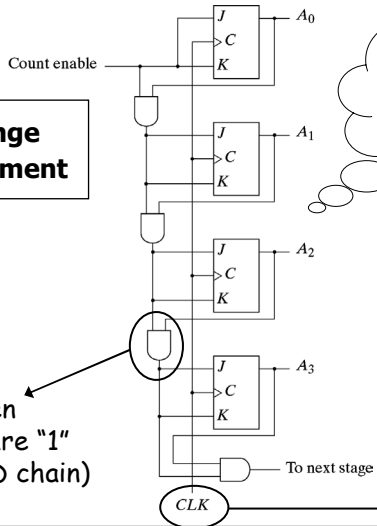


6-21
 
# Up-Down Binary Counter

Up: 0000→0001→0010→...  
 Down: 1111→1110→1101→...

take the complemented  
 values for count-down  
 calculation



6-22

## Design a BCD Counter

- Go through normal sequential circuit design procedure


Present State				Next State				Output	Flip-Flop Inputs			
$Q_8$	$Q_4$	$Q_2$	$Q_1$	$Q_8$	$Q_4$	$Q_2$	$Q_1$	$y$	$T_{Q_8}$	$T_{Q_4}$	$T_{Q_2}$	$T_{Q_1}$
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$$T_{Q_1} = 1 \quad T_{Q_4} = Q_2 Q_1 \quad y = Q_8 Q_1$$

$$T_{Q_2} = Q_8' Q_1 \quad T_{Q_8} = Q_8 Q_1 + Q_4 Q_2 Q_1$$

6-23

## Binary Counter with Parallel Load

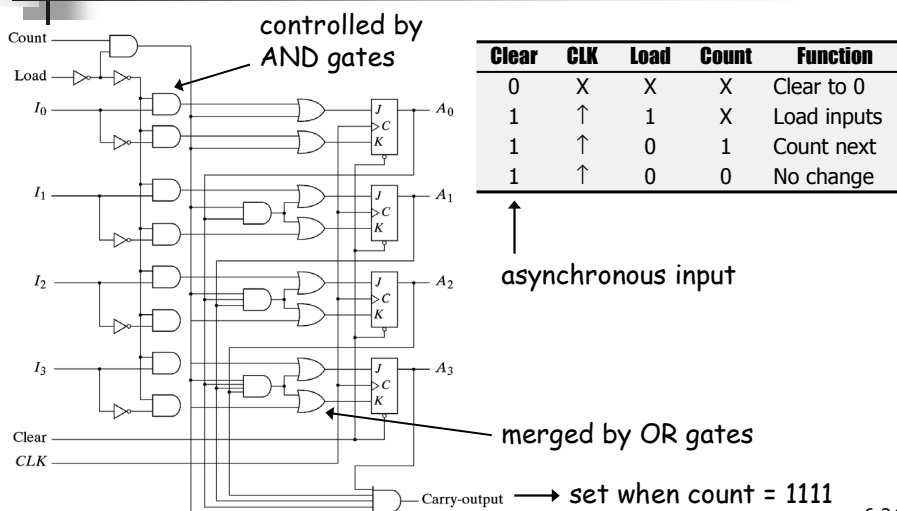

## Achieve a BCD Counter

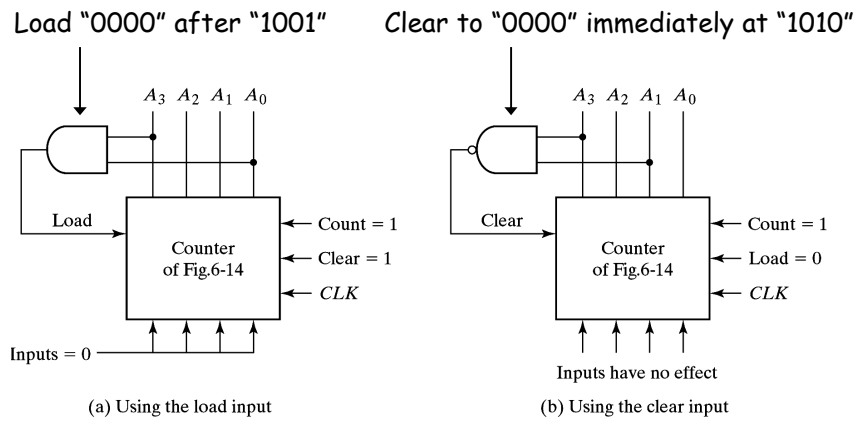


Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load

6-25


## Outline

- Registers
- Shift Registers
- Ripple Counters
- Synchronous Counters
- Other Counters

6-26

 
# Counter with Unused States

- If the machine falls into the unused states, we have to bring it back !!
  - Cannot assign the used states as don't cares



(a) Logic diagram


Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

 

(b) State diagram


6-27

# Ring Counter

 


 (a) Ring-counter (initial value = 1000)

Ring counter: a circular shift register with only one flip-flop being set at any time



(b) Counter and decoder

 


(c) Sequence of four timing signals

6-28
 
# Johnson Counter

- Double the number of states of a ring counter by switch-tail connection
- If this counter falls into an unused state, it will never come back to normal states !!
- To avoid this situation, use some gates to form the input equation of each flip-flop instead of connecting directly
  - Ex:  $D_c = (A + C) B$



(a) Four-stage switch-tail ring counter

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding