

# Chapter 4

## Electrical Characteristics of CMOS

Jin-Fu Li

Department of Electrical Engineering  
National Central University  
Jungli, Taiwan

# Outline

- ☐ Resistance & Capacitance Estimation
- ☐ DC Response
- ☐ Logic Level and Noise Margins
- ☐ Transient Response
- ☐ Delay Estimation
- ☐ Transistor Sizing
- ☐ Power Analysis
- ☐ Scaling Theory

# Resistance Estimation

## □ Resistance



- $R = (\rho / t)(L / W)$ , where  $(\rho, t, L, W)$  is (*resistivity, thickness, conductor length, conductor width*)

## □ Sheet resistance

- $R_s = \Omega / \square$
- Thus  $R = R_s (L / W)$

1 rectangular block

$$R = R_s (L / W)$$

  


4 rectangular block


$$R = R_s (2L / 2W) = R_s (L / W)$$
 
# Drain-Source MOS Resistance

- A simplified linear model of MOS is useful at the logic level design
- RC model of an NMOS



 - The drain-source resistance at any point on the current curve as shown below



# Drain-Source Resistance

- The resistance at point a
  - The current is approximated by
    - $I_{ds} \approx \beta_n (V_{gs} - V_t) V_{ds}$
  - Thus the resistance is
    - $R_n \approx 1 / \beta_n (V_{gs} - V_t)$
- The resistance at point b
  - The full non-saturated current must be used so that
    - $I_{ds} = \frac{1}{2} \beta_n [2(V_{gs} - V_t) V_{ds} - V_{ds}^2]$
  - Thus the resistance is
    - $R_n = 2 / \beta_n [2(V_{gs} - V_t) - V_{ds}]$

# Drain-Source Resistance

- The resistance at point c
  - The current is
    - $I_{ds} \approx \frac{1}{2} \beta_n (V_{gs} - V_t)^2$
  - Thus the resistance is
    - $R_n = 2V_{ds} / \beta_n (V_{gs} - V_t)^2$
  - $R_n$  is a function of both  $V_{gs}$  and  $V_{ds}$
- These equations show that it is not possible to define a constant value for  $R_n$
- However,  $R_n$  is inversely proportion to  $\beta_n$  in all cases, i.e.,
  - $R_n \propto 1 / \beta_n$
  - $\beta_n = k(W / L)$  ,  $W/L$  is called *aspect ratio*

# Capacitance Estimation

- The switching speed of MOS circuits are heavily affected by the parasitic capacitances associated with the MOS device and interconnection capacitances
- The total load capacitance on the output of a CMOS gate is the sum of
  - *Gate capacitance*
  - *Diffusion capacitance*
  - *Routing capacitance*
- Understanding the source of parasitic loads and their variations is essential in the design process


# MOS-Capacitor Characteristics

- The capacitance of an MOS is varied with the applied voltages
- Capacitance can be calculated by
  - $C = \frac{\epsilon_0 \epsilon_x}{d} A$
  - $\epsilon_x$  is dielectric constant
  - $\epsilon_0$  is permittivity of free space
- Depend on the gate voltage, the state of the MOS surface may be in
  - Accumulation
  - Depletion
  - Inversion


 
# MOS Capacitor Characteristics


- When  $V_g < 0$ , an *accumulation* layer is formed
  - The negative charge on the gate attracts holes toward the silicon surface
  - The MOS structure behaves like a parallel-plate capacitor



$$C_o = \frac{\epsilon_0 \epsilon_{SiO_2}}{t_{ox}} A$$
 
# MOS Capacitor Characteristics

- When a small positive voltage is applied to the gate, a depletion layer is formed
  - The positive gate voltage repels holes, leaving a negatively charged region depleted of carriers




$$C_{dep} = \frac{\epsilon_0 \epsilon_{Si}}{d} A$$

$$C_{gb} = \frac{C_0 C_{dep}}{C_0 + C_{dep}}$$
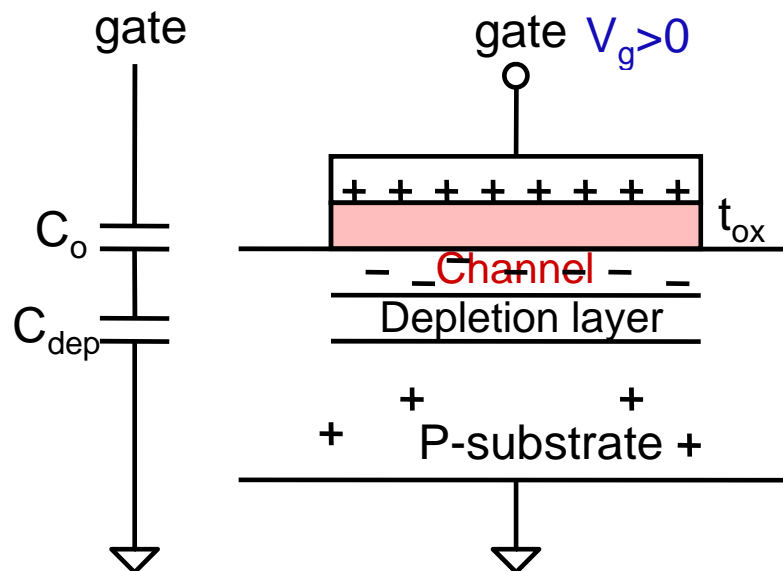
# MOS Capacitor Characteristics

- When the gate voltage is further increased, an n-type channel (inversion layer) is created
- If the MOS is operated at high frequency, the surface charge is not able to track fast moving gate voltages



*Low frequency*


$$C_{gb} = C_0$$

*High frequency*

$$C_{gb} = \frac{C_0 C_{dep}}{C_0 + C_{dep}} = C_{min}$$
 
# MOS Capacitor Characteristics



- Consequently, the dynamic gate capacitance as a function of gate voltage, as shown below



- The minimum capacitance depends on the depth of the depletion region, which depends on the substrate doping density
 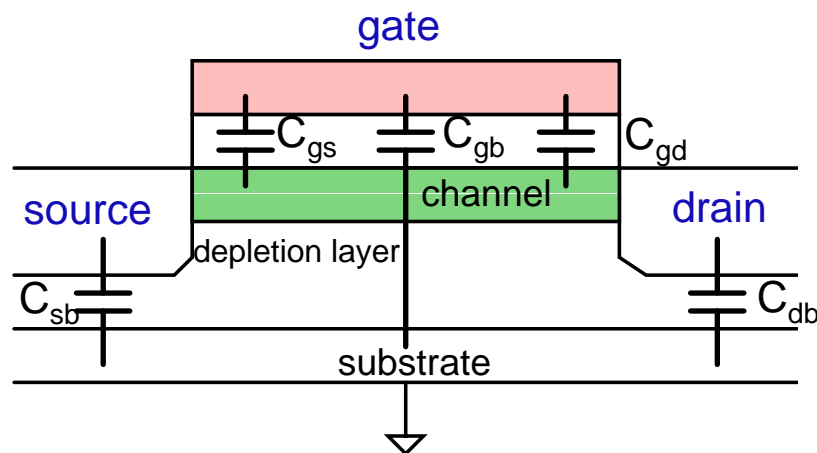
# MOS Device Capacitances

- The parasitic capacitances of an MOS transistor are shown as below
  - $C_{gs}$ ,  $C_{gd}$ : gate-to-channel capacitances, which are lumped at the source and the drain regions of the channel, respectively
  - $C_{sb}$ ,  $C_{db}$ : source and drain-diffusion capacitances to bulk
  - $C_{gb}$ : gate-to-bulk capacitance



# Variation of Gate Capacitance

□ The behavior of the gate capacitance in the three regions of operation is summarized as below


- Off region ( $V_{gs} < V_t$ ):  $C_{gs} = C_{gd} = 0$ ;  $C_g = C_{gb}$
- Non-saturated region ( $V_{gs} - V_t > V_{ds}$ ):  $C_{gs}$  and  $C_{gd}$  become significant. These capacitances are dependent on gate voltage. Their value can be estimated as

$$C_{gd} = C_{gs} = \frac{1}{2} \frac{\epsilon_0 \epsilon_{SiO_2}}{t_{ox}} A$$

- Saturated region ( $V_{gs} - V_t < V_{ds}$ ): The drain region is pinched off, causing  $C_{gd}$  to be zero.  $C_{gs}$  increases to approximately  $C_{gs} = \frac{2}{3} \frac{\epsilon_0 \epsilon_{SiO_2}}{t_{ox}} A$
 
# Approximation of the $C_g$



- The  $C_g$  can be further approximated with
  - $C_g = C_{ox} A$ , where  $C_{ox} = \frac{\epsilon_o \epsilon_{SiO_2}}{t_{ox}}$
- The gate capacitance is determined by the gate area, since the thickness of oxide is associated with process of fabrication
- For example, assume that the thickness of silicon oxide of the given process is  $150 \times 10^{-8} \mu m$ . Calculate the capacitance of the MOS shown below



$$C_g = \frac{3.9 \times 8.854 \times 10^{-14}}{150 \times 10^{-8}} \times 2 = 25.5 \times 2 \times 10^{-4} pF \approx 0.005 pF$$
  
# Diffusion Capacitance

- Diffusion capacitance  $C_d$  is proportional to the diffusion-to-substrate junction area



$$C_d = C_{ja} \times (ab) + C_{jp} \times (2a + 2b)$$

$C_{ja}$  = junction capacitance per micron square

$C_{jp}$  = periphery capacitance per micron



# Junction Capacitance


- Semiconductor physics reveals that a PN junction automatically exhibits capacitance due to the *opposite polarity charges* involved. This is called *junction* or *depletion* capacitance and is found at every drain or source region of a MOS
- The junction capacitance is varies with the junction voltage, it can be estimate as

$$C_j = C_{j0} \left(1 - \frac{V_j}{V_b}\right)^{-m}$$

- $C_j$  = junction voltage (negative for reverse bias)
- $C_{j0}$  = zero bias junction capacitance ( $V_j = 0$ )
- $V_b$  = built-in junction voltage  $\sim 0.6V$
 
# Single Wire Capacitance


- Routing capacitance between metal and substrate can be approximated using a parallel-plate model



- In addition, a conductor can exhibit capacitance to an adjacent conductor on the same layer
 
# Multiple Conductor Capacitances


- Modern CMOS processes have multiple routing layers
  - The capacitance interactions between layers can become quite complex
- Multilevel-layer capacitance can be modeled as below



$$C_2 = C_{21} + C_{23} + C_{22}$$
 
# A Process Cross Section


- Interlayer capacitances of a two-level-metal process



# Inductor

 
## □ For bond wire inductance

■ 
$$L = \frac{\mu}{2\pi} \ln\left(\frac{4h}{d}\right)$$


 
## □ For on-chip metal wires

■ 
$$L = \frac{\mu}{2\pi} \ln\left(\frac{8h}{w} + \frac{w}{4h}\right)$$




## □ The inductance produces $L di/dt$ noise especially for ground bouncing noise. Note that when CMOS circuit are clocked, the current flow changes greatly

$$V = L \frac{di}{dt}$$
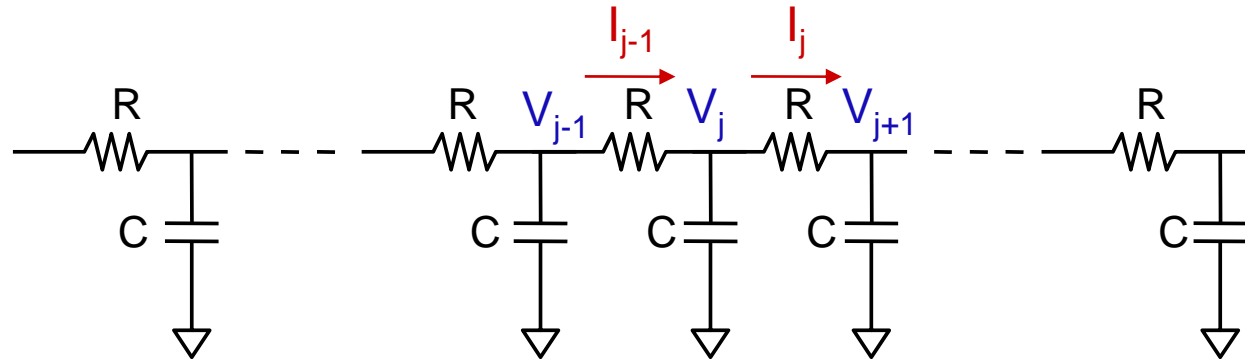
# Distributed RC Effects

- The propagation delay of a signal along a wire mainly depends on the distributed resistance and capacitance of the wire
- A long wire can be represented in terms of several RC sessions, as shown below



- The response at node  $V_j$  with respect to time is then given by

- $CdV = Idt \Rightarrow C \frac{dV_j}{dt} = (I_{j-1} - I_j) = \frac{(V_{j-1} - V_j)}{R} - \frac{(V_j - V_{j+1})}{R}$

# Distributed RC Effects

- As the number of sections in the network becomes large (and the sections become small), the above expression reduces to the differential form

- $rc \frac{dV}{dt} = \frac{d^2V}{dx^2} \Rightarrow t_x = kx^2$

- $r$  : resistance per unit length

- $c$  : capacitance per unit length

- Alternatively, a discrete analysis of the circuit shown in the previous page yields an approximate signal delay of

- $t_n = 0.7 \times \frac{RCn(n+1)}{2}$  , where n=number of sections

- $t_1 = 0.7 \frac{rc l^2}{2}$

# Wire Segmentation with Buffers

- To optimize speed of a long wire, one effective method is to segment the wire into several sections and insert buffers within these sections
- Consider a poly bus of length 2mm that has been divided into two 1mm sections.
  - Assume that  $t_x = 4 \times 10^{-15} x^2$
  - With buffer 
$$t_p = 4 \times 10^{-15} \times 1000^2 + t_{buf} + 4 \times 10^{-15} \times 1000^2$$
$$= 4ns + t_{buf} + 4ns = 8ns + t_{buf}$$
  - Without buffer  $t_p = 4 \times 10^{-15} \times 2000^2 = 16ns$
  - By keeping the buffer delay small, significant gain can be obtained with buffer insertion




# Crosstalk

- A capacitor does not like to change its voltage instantaneously.
- A wire has high capacitance to its neighbor.
  - When the neighbor switches from 1-→ 0 or 0-→1, the wire tends to switch too.
  - Called capacitive *coupling* or *crosstalk*.
- Crosstalk effects
  - Noise on nonswitching wires
  - Increased delay on switching wires

# Crosstalk Delay

- Assume layers above and below on average are quiet
  - Second terminal of capacitor can be ignored
  - Model as  $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- Effective  $C_{\text{adj}}$  depends on behavior of neighbors
  - *Miller effect*


B	$\Delta V$	$C_{\text{eff(A)}}$	MCF
Constant	$V_{\text{DD}}$	$C_{\text{gnd}} + C_{\text{adj}}$	1
Switching with A	0	$C_{\text{gnd}}$	0
Switching opposite A	$2V_{\text{DD}}$	$C_{\text{gnd}} + 2 C_{\text{adj}}$	2

 
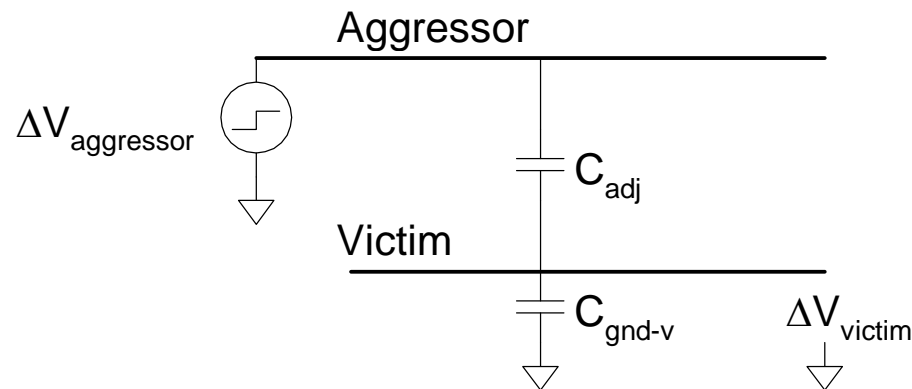
# Crosstalk Noise

- Crosstalk causes noise on nonswitching wires
- If victim is floating:
  - model as capacitive voltage divider

$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$




# Driven Victim

- Usually victim is driven by a gate that fights noise
  - Noise depends on relative resistances
  - Victim driver is in linear region, agg. in saturation
  - If sizes are same,  $R_{\text{aggressor}} = 2-4 \times R_{\text{victim}}$


$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \frac{1}{1+k} \Delta V_{\text{aggressor}}$$
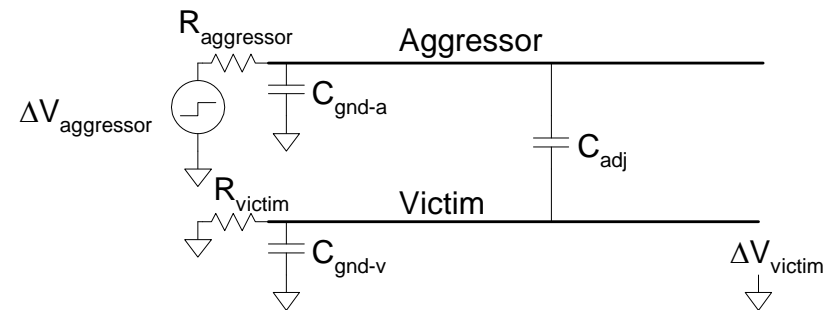
$$k = \frac{\tau_{\text{aggressor}}}{\tau_{\text{victim}}} = \frac{R_{\text{aggressor}} (C_{\text{gnd-a}} + C_{\text{adj}})}{R_{\text{victim}} (C_{\text{gnd-v}} + C_{\text{adj}})}$$


 
# Simulation Waveforms

□ Simulated coupling for  $C_{adj} = C_{victim}$



# DC Response

□ DC Response:  $V_{out}$  vs.  $V_{in}$  for a gate

□ Ex: Inverter

■ When  $V_{in} = 0 \rightarrow V_{out} = V_{DD}$

■ When  $V_{in} = V_{DD} \rightarrow V_{out} = 0$


■ In between,  $V_{out}$  depends on transistor size and current

■ By KCL, must settle such that

$$I_{dsn} = |I_{dsp}|$$

■ We could solve equations

 ■ But graphical solution gives more insight



# Transistor Operation


- Current depends on region of transistor behavior
- For what  $V_{in}$  and  $V_{out}$  are NMOS and PMOS in
  - Cutoff?
  - Linear?
  - Saturation?

# NMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 




# NMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


# PMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$  $V_{dsp} > V_{gsp} - V_{tp}$	$V_{gsp} < V_{tp}$  $V_{dsp} < V_{gsp} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 


# PMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$


$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 

 
# I-V Characteristics

- Make pMOS is wider than nMOS such that  $\beta_n = \beta_p$




# Current & $V_{out}$ , $V_{in}$

 



# Load Line Analysis

- For a given  $V_{in}$ :
  - Plot  $I_{dsn}$ ,  $I_{dsp}$  vs.  $V_{out}$
  - $V_{out}$  must be where |currents| are equal in

 
  
# DC Transfer Curve


□ Transcribe points onto  $V_{in}$  vs.  $V_{out}$  plot



# Operation Regions

□ Revisit transistor operating regions


Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

 



 
# Beta Ratio

- If  $\beta_p / \beta_n \neq 1$ , switching point will move from  $V_{DD}/2$
- Called *skewed gate*
- Other gates: collapse into equivalent inverter


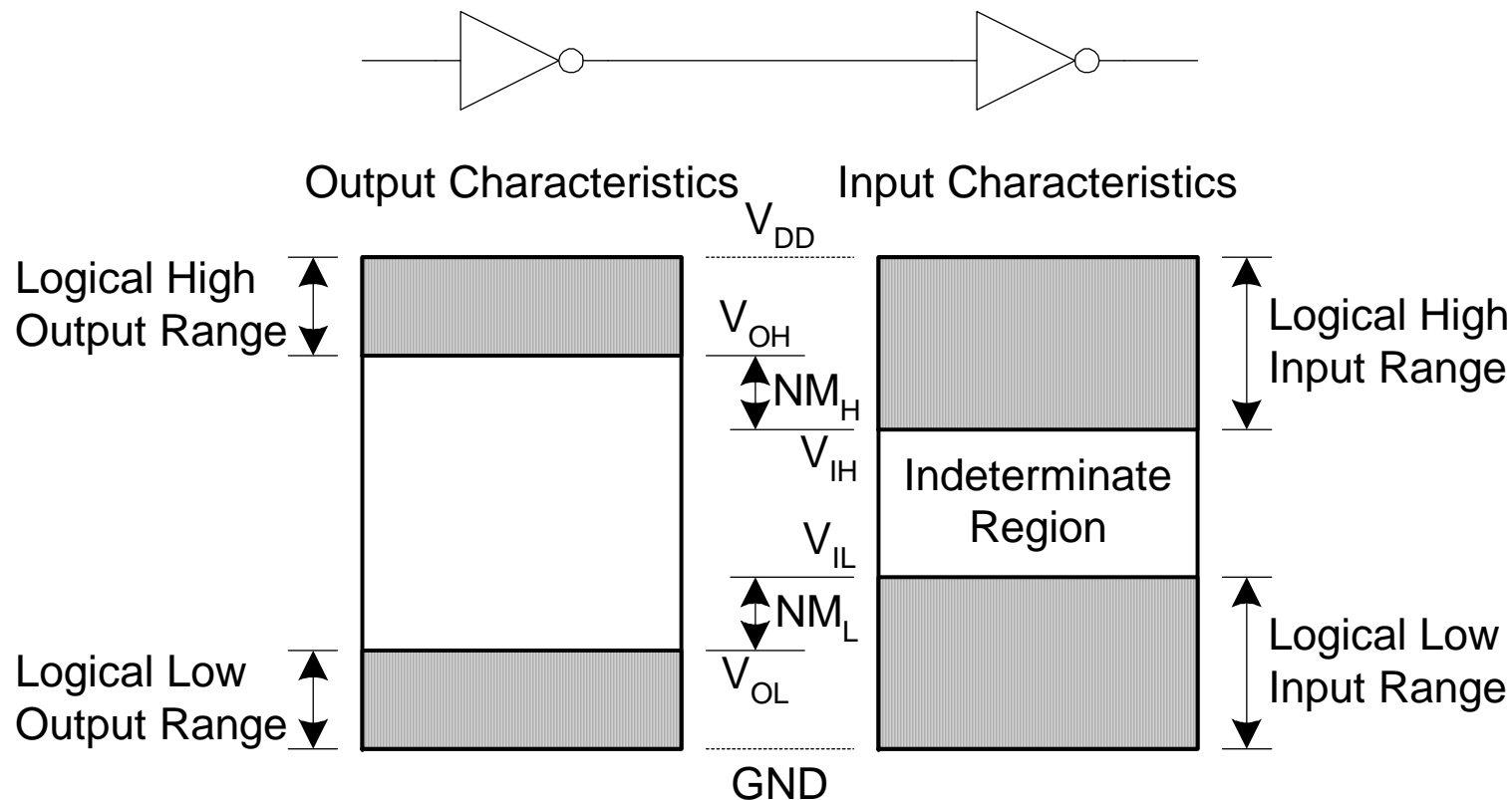
# Noise Margin

- How much noise can a gate input see before it does not recognize the input?




# Transient Analysis

- *DC analysis* tells us  $V_{\text{out}}$  if  $V_{\text{in}}$  is constant
- *Transient analysis* tells us  $V_{\text{out}}(t)$  if  $V_{\text{in}}(t)$  changes

# Switching Characteristics
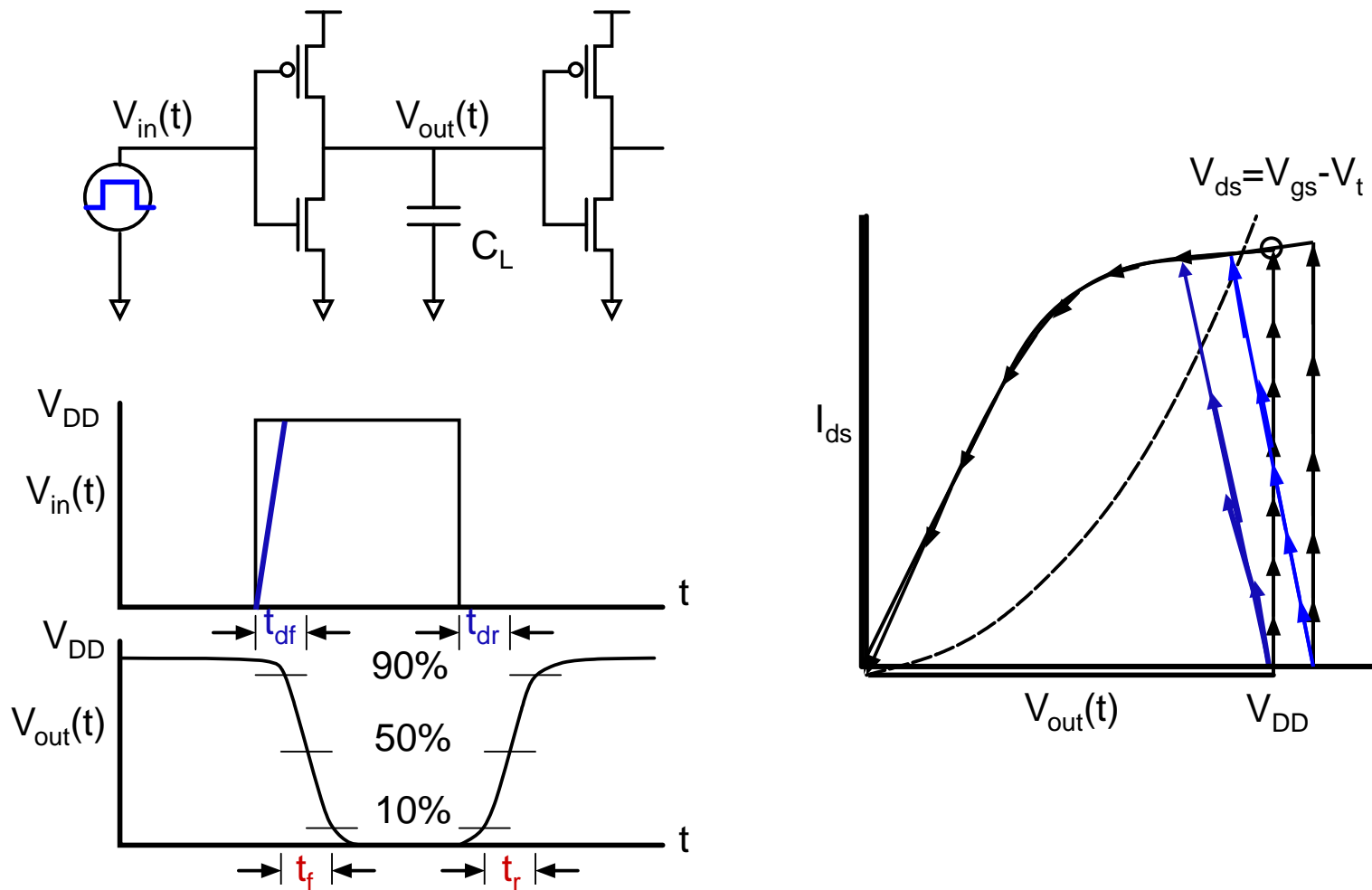
## □ Switching characteristics for CMOS inverter



# Switching Characteristics

## □ Rise time ( $t_r$ )

- The time for a waveform to rise from 10% to 90% of its steady-state value

## □ Fall time ( $t_f$ )

- The time for a waveform to fall from 90% to 10% steady-state value


## □ Delay time ( $t_d$ )

- The time difference between input transition (50%) and the 50% output level. (This is the time taken for a logic transition to pass from input to output)
- High-to-low delay ( $t_{df}$ )
- Low-to-high delay ( $t_{dr}$ )


# Fall Time of the Inverter

## □ Equivalent circuit for fall-time analysis

Input rising

 

 Saturated  $V_{out} \geq V_{DD} - V_{tn}$



Nonsaturated  $0 < V_{out} \leq V_{DD} - V_{tn}$

## □ The fall time consists of two intervals

- $t_{f1}$  = period during which the capacitor voltage,  $V_{out}$ , drops from  $0.9V_{DD}$  to  $(V_{DD} - V_{tn})$
- $t_{f2}$  = period during which the capacitor voltage,  $V_{out}$ , drops from  $(V_{DD} - V_{tn})$  to  $0.1V_{DD}$

# Timing Calculation

- $t_{f1}$  can be calculated with the current-voltage equation as shown below, while in saturation

- $C_L \frac{dV_{out}}{dt} + \frac{\beta_n}{2} (V_{DD} - V_{tn})^2 = 0$

- $t_{f2}$  also can be obtained by the same way

- Finally, the fall time can be estimated with

$$t_f \approx k \times \frac{C_L}{\beta_n V_{DD}}$$

- Similarly, the rise time can be estimated with

- $t_r \approx k \times \frac{C_L}{\beta_p V_{DD}}$

- Thus the propagation delay is

- $t_p \approx k \times \frac{C_L}{V_{DD}} \left( \frac{1}{\beta_n} + \frac{1}{\beta_p} \right)$


# Design Challenges

- $\beta_n = \beta_p$  , *rise time=fall time*
  - This implies  $W_p = 2-3W_n$
- *Reduce  $C_L$* 
  - Careful layout can help to reduce the diffusion and interconnect capacitance
- *Increase  $\beta_n$  and  $\beta_p$* 
  - Increase the transistor sizes also increases the diffusion capacitance as well as the gate capacitance. The latter will increase the fan-out factor of the driving gate and adversely affect its speed
- *Increase  $V_{DD}$* 
  - Designers don't have too much control over this


 
# Gate Delays

- Consider a 3-input NAND gate as shown below



- When pull-down path is conducting

- $$\beta_{neff} = \frac{1}{(1/\beta_{n1}) + (1/\beta_{n2}) + (1/\beta_{n3})}$$


- For  $\beta_{n1} = \beta_{n2} = \beta_{n3} \Rightarrow \beta_{neff} = \frac{\beta_n}{3}$

- When the pull-down path is conducting

- Only one p-transistor has to turn on to raise the output.  
Thus  $\beta_{peff} = \beta_p$
 
# Gate Delays

- Graphical illustration of the effect of series transistors



- In general, the fall time  $t_f$  is  $mt_f$  ( $t_f/m$ ) for  $m$  n-transistors in series (parallel). Similarly the rise time  $t_r$  for  $k$  p-transistors in series (parallel) is  $kt_r$  ( $t_r/k$ )

# Switch-Level RC Model

## □ RC modeling

- Transistors are regarded as a resistance discharging or charging a capacitance

## □ Simple RC modeling


- Lumped RCs

- $t_{df} = \sum R_{pulldown} \times \sum C_{pulldown-path}$

## □ Elmore RC modeling

- Distributed RCs

- $t_d = \sum_i R_i C_i$

 

# Example

□ Consider a 4-input NAND as shown below

■ Simple RC model

$$t_{df} = \sum R_{pulldown} \times \sum C_{pulldown-path}$$

$$= (R_{N1} + R_{N2} + R_{N3} + R_{N4}) \times (C_{out} + C_{ab} + C_{bc} + C_{cd})$$

$$t_{dr} = R_{p4} \times C_{out}$$


■ Elmore RC model

$$t_d = \sum_i R_i C_i$$

$$t_{df} = (R_{N1} \times C_{cd}) + [(R_{N1} + R_{N2}) \times C_{bc}]$$

$$+ [(R_{N1} + R_{N2} + R_{N3}) \times C_{ab}]$$
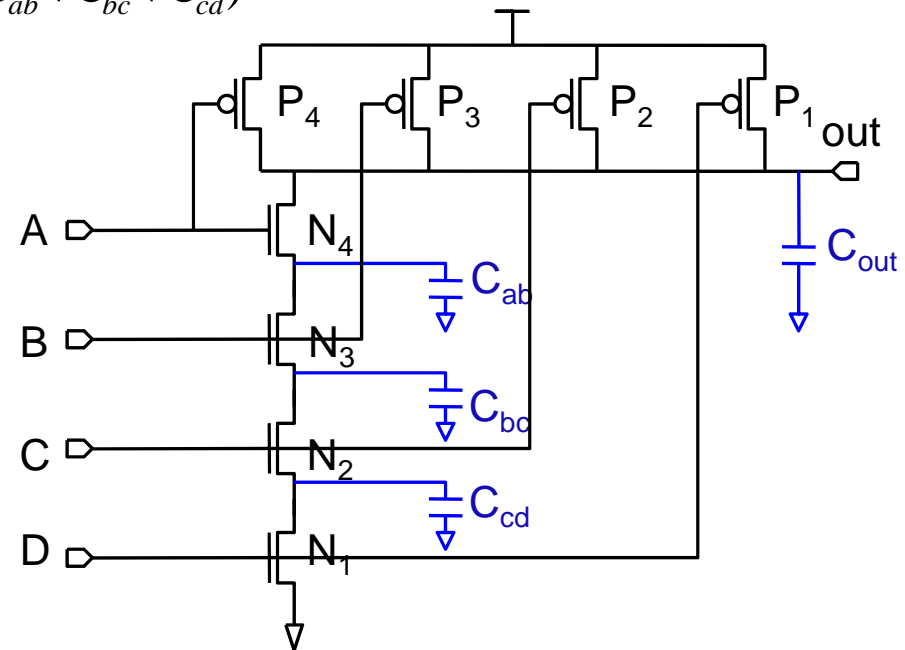
$$+ [(R_{N1} + R_{N2} + R_{N3} + R_{N4}) \times C_{out}]$$




# Cascaded CMOS Inverter

- As discussed above, if we want to have approximately the same rise and fall times for an inverter, for current CMOS process, we must make
  - $W_p = 2-3W_n$
  - Increase layout area and dynamic power dissipation
- In some cascaded structures it is possible to use minimum or equal-size devices without compromising the switching response
- In the following, we illustrate two examples to explain why it is possible


# Cascaded CMOS Inverter

## □ Example 1:

 

$$\begin{aligned}
 t_{inv-pair} &= t_{fall} + t_{rise} \\
 &= R 3C_{eq} + 2 \frac{R}{2} 3C_{eq} \\
 &= 3RC_{eq} + 3RC_{eq} \\
 &= 6RC_{eq}
 \end{aligned}$$


## □ Example 2:

 

$$\begin{aligned}
 t_{inv-pair} &= t_{fall} + t_{rise} \\
 &= R 2C_{eq} + 2 R 2C_{eq} \\
 &= 6RC_{eq}
 \end{aligned}$$
 
# Stage Ratio

- To drive large capacitances such as long buses, I/O buffers, etc.
  - Using a chain of inverters where each successive inverter is made larger than the previous one until the last inverter in the chain can drive the large load in the time required
  - The ratio by which each stage is increased in size is called stage ratio
- Consider the circuit shown below
  - It consists of  $n$ -cascaded inverters with stage-ratio  $a$  driving a capacitance  $C_L$



# Stage Ratio

- The delay through each stage is  $at_d$ , where  $t_d$  is the average delay of a minimum-sized inverter driving another minimum-sized inverter
- Hence the delay through  $n$  stages is  $nat_d$
- If the ratio of the load capacitance to the capacitance of a minimum inverter,  $C_L/C_g$ , is  $R$ , then  $a^n=R$ 
  - Hence  $\ln(R)=n\ln(a)$
  - Thus the total delay is  $\ln(R)(a/\ln(a))t_d$
  - The optimal stage ratio may be determined from

- $a_{opt} = e^{\frac{k+a_{opt}}{a_{opt}}}$  where  $k$  is  $\frac{C_{drain}}{C_{gate}}$



# Power Dissipation

## □ Instantaneous power

- The value of power consumed at any given instant

- $P(t) = v(t)i(t)$

## □ Peak power

- The highest power value at any given instant; peak power determines the component's thermal and electrical limits and system packaging requirements

- $P_{peak} = Vi_{peak}$

## □ Average power

- The total distribution of power over a time period; average power impacts the battery lifetime and heat dissipation


- $$P_{ave} = \frac{1}{T} \int_t^{t+T} P(t)dt = \frac{V}{T} \int_t^{t+T} i(t)dt$$

# Power Analysis for CMOS Circuits

- Two components of power consumption in a CMOS circuit
  - Static power dissipation
    - Caused by the leakage current and other static current
  - Dynamic power dissipation
    - Caused by the total output capacitance
    - Caused by the *short-circuit* current
- The total power consumption of a CMOS circuit is
  - $P_t = P_s + P_{sw} + P_{sc}$
  - $P_s$ : static power (leakage power);  $P_{sw}$ : switching power;  $P_{sc}$ : short-circuit power
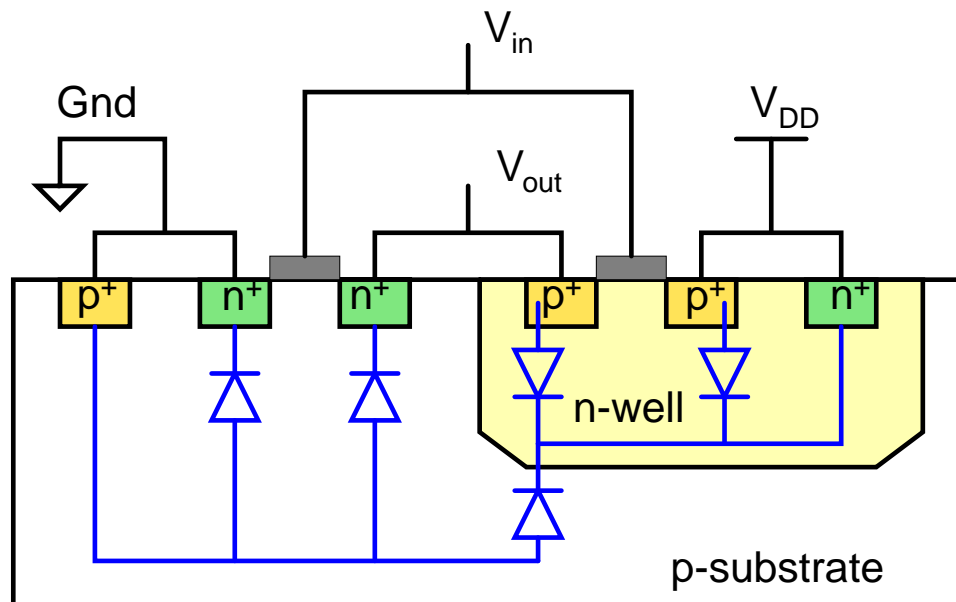
# Static Power

- ❑ Static dissipation is major contributed by
  - Reverse bias leakage between diffusion regions and the substrate
  - Subthreshold conduction



PN junction reverse bias leakage current


$$i_0 = i_s (e^{qV/KT} - 1)$$

$$P_s = \sum_1^n I_{leakage} \times V_{supply}$$

n=number of devices
 
# Dynamic Power Dissipation

- Switching power
  - Caused by charging and discharging the output capacitive load
- Consider an inverter operated at a switching frequency  $f=1/T$



$$P_{sw} = \frac{1}{T} \int_0^T i_o(t) v_o(t) dt$$

$$i_p = i_o = C_L \frac{dv_o}{dt}$$

$$i_n = -i_o = -C_L \frac{dv_o}{dt}$$

$$P_{sw} = \frac{1}{T} \left[ \int_0^{V_{DD}} C_L v_o dv_o - \int_{V_{DD}}^0 C_L v_o dv_o \right]$$

$$P_{sw} = \frac{C_L V_{DD}^2}{T} = f C_L V_{DD}^2$$

# Power & Energy


- Energy consumption of an inverter (from  $0 \rightarrow V_{DD}$ )
  - The energy drawn from the power supply is
    - $E = QV = C_L V_{DD}^2$
  - The energy stored in the load capacitance is
    - $E_{cap} = \int_0^{V_{DD}} C v_o dv_o = \frac{1}{2} C_L V_{DD}^2$
  - The output from  $V_{DD} \rightarrow 0$ 
    - The  $E_{cap}$  is consumed by the pull-down NMOS
- Low-energy design is more important than low-power design
  - Minimize the product of power and delay

# Short-Circuit Power Dissipation

- Even if there were no load capacitance on the output of the inverter and the parasitics are negligible, the gate still dissipates switching energy
- If the input changes slowly, both the NMOS and PMOS transistors are ON, an excess power is dissipated due to the short-circuit current
- We are assuming that the rise time of the input is equal to the fall time
- The short-circuit power is estimated as
  - $P_{sc} = I_{mean} V_{DD}$
 
# Short-Circuit Power Dissipation

□  $I_{mean}$  can be estimated as follows



$$I_{mean} = 2 \times \frac{1}{T} \left[ \int_{t_1}^{t_2} i(t) dt + \int_{t_2}^{t_3} i(t) dt \right]$$

$$I_{mean} = \frac{4}{T} \left[ \int_{t_1}^{t_2} i(t) dt \right]$$

# Short-Circuit Power Dissipation

- The NMOS transistor is operating in saturation, hence the above equation becomes

$$I_{mean} = \frac{4}{T} \left[ \int_{t_1}^{t_2} \frac{\beta}{2} (V_{in}(t) - V_T)^2 dt \right]$$

$$V_{in}(t) = \frac{V_{DD}}{t_r} t$$

$$t_1 = \frac{V_T}{V_{DD}} t_r$$


$$t_2 = \frac{t_r}{2}$$

$$P_{sc} = \frac{\beta}{12} (V_{DD} - 2V_T)^3 \tau f \quad (t_r = t_f = \tau)$$




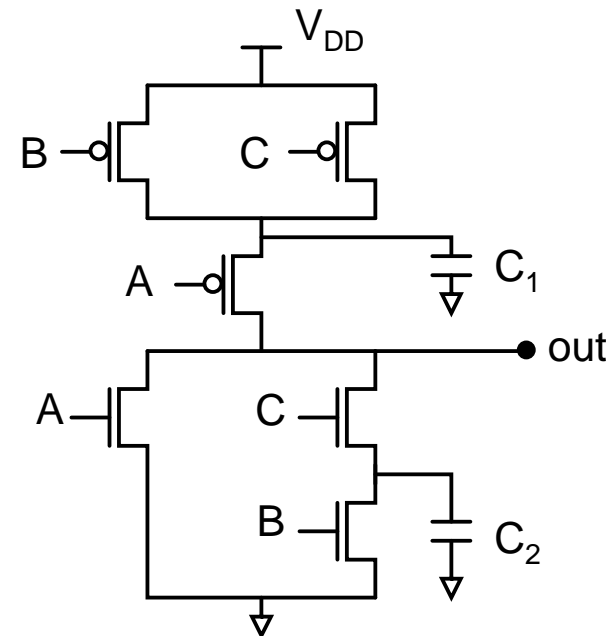
# Power Analysis for Complex Gates

- The dynamic power for a complex gate cannot be estimated by the simple expression  $C_L V_{DD} f$
- Dynamic power dissipation in a complex gate
  - Internal cell power
  - Capacitive load power
- Capacitive load power
  - $P_L = \alpha C_L V_{DD}^2 f$
- Internal cell power
  - $P_{\text{int}} = \sum_{i=1}^n \alpha_i C_i V_i V_{DD} f$



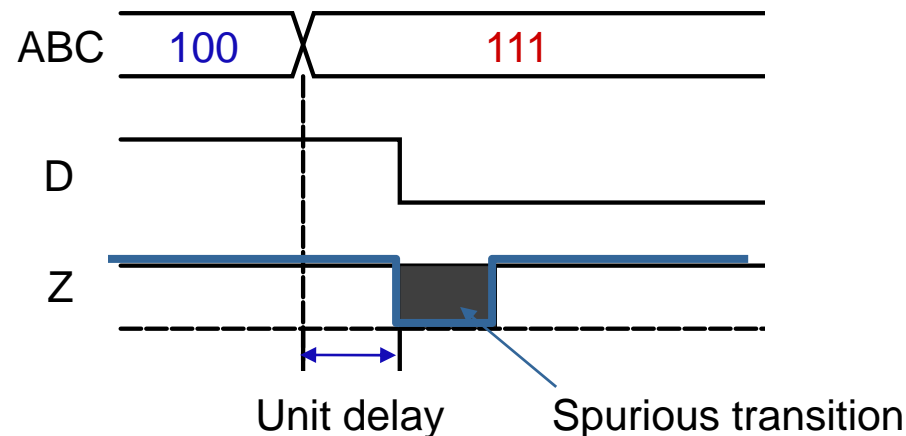 
# Glitch Power Dissipation

- In a static logic gate, the output or internal nodes can switch before the correct logic value is being stable. This phenomenon results in spurious transitions called glitches


 
# Rules for Avoiding Glitch Power

- Balance delay paths; particularly on highly loaded nodes



- Insert, if possible, buffers to equalize the fast path
- Avoid if possible the cascaded design
- Redesign the logic when the power due to the glitches is an important component

# Principles for Power Reduction

## □ Switching power dissipation

- $P_L = \alpha C_L V_{DD}^2 f$

- $P_{\text{int}} = \sum_{i=1}^n \alpha_i C_i V_i V_{DD} f$

## □ Prime choice: *reduce voltage*

- Recent years have seen an acceleration in supply voltage reduction
- Design at very low voltage still open question (0.6V...0.9V by 2010)

## □ *Reduce switching activity*

## □ *Reduce physical capacitance*

# Layout Guidelines for LP Designs



- ❑ Identify, in your circuit, the high switching nodes
- ❑ Keep the wires of high activity nodes short
- ❑ Use low-capacitance layers (e.g., metal2, metal 3, etc.) for high capacitive nodes and busses
- ❑ Avoid, if possible, the use of dynamic logic design style
- ❑ For any logic design, reduce the switching activity, by logic reordering and balanced delays through gate tree to avoid glitch problem
- ❑ In non-critical paths, use minimum size devices whenever it is possible without degrading the overall performance requirements
- ❑ If pass-transistor logic style is used, careful design should be considered

# Sizing Routing Conductors

- Why do metal lines have to be sized?
  - Electromigration
  - Power supply noise and integrity (i.e., satisfactory power and signal voltage levels are presented to each gate)
  - RC delay
- Electromigration is affected by
  - Current density
  - Temperature
  - Crystal structure
- For example, the limiting value for 1  $\mu\text{m}$ -thick aluminum is  $J_{Al} = 1 \rightarrow 2\text{mA} / \mu\text{m}$

# Power & Ground Bounce

- An example of ground bounce

  


# Approaches for Coping with $L(di/dt)$

- Multiple power and ground pins
  - Restrict the number of I/O drivers connected to a single supply pins (reduce the  $di/dt$  per supply pin)
- Careful selection of the position of the power and ground pins on the package
  - Avoid locating the power and ground pins at the corners of the package (reduce the  $L$ )
- Increase the rise and fall times
  - Reduce the  $di/dt$
- Adding decoupling capacitances on the board
  - Separate the bonding-wire inductance from the inductance of the board interconnect



 
# Contact Replication

- Current tends to concentrate around the perimeter in a contact hole
  - This effect, called *current crowding*, puts a practical upper limit on the size of the contact
  - When a contact or a via between different layers is necessary, make sure to maximize the contact perimeter (not area)


 
# Charge Sharing

- Charge  $Q=CV$
- A bus example is illustrated to explain the charge sharing phenomenon
  - A bus can be modeled as a capacitor  $C_b$
  - An element attached to the bus can be modeled as a capacitor  $C_s$



$$Q_T = C_b V_b + C_s V_s \quad V_R = \frac{Q_T}{C_T} = (C_b V_b + C_s V_s) / (C_b + C_s)$$
$$C_T = C_b + C_s$$


# Design Margining

- The operating condition of a chip is influenced by three major factors
  - Operating temperature
  - Supply voltage
  - Process variation
- One must aim to design a circuit that will reliably operate over all extremes of these three variables
- Design corners
  - Simulating circuits at all corners is needed
    - SS
    - TT
    - FF

# Package Issues

- Packaging requirements
  - Electrical: low parasitics
  - Mechanical: reliable and robust
  - Thermal: efficient heat removal
  - Economical: cheap
- Bonding techniques

## Wire Bonding

 


# Yield Estimation


$$Y = \frac{\text{No. of good chips per wafer}}{\text{Total number of chips per wafer}} \times 100\%$$

$$\text{Die cost} = \frac{\text{Wafer cost}}{\text{Dies per wafer} \times \text{Die yield}}$$
 
$$\text{Dies per wafer} = \frac{\pi \times (\text{wafer diameter}/2)^2}{\text{die area}} - \frac{\pi \times \text{wafer diameter}}{\sqrt{2} \times \text{die area}}$$



# Die Cost

 

Single die

Wafer



Going up to 12" (30cm)

# Scaling Theory

- Consider a transistor that has a channel width  $W$  and a channel length  $L$
- We wish to find out how the main electrical characteristics change when both dimensions are reduced by a scaling factor  $S > 1$  such that the new transistor has sizes
  - $\tilde{W} = \frac{W}{S} \quad \tilde{L} = \frac{L}{S}$
- Gate area of the scaled transistor
  - $\tilde{A} = \frac{A}{S^2}$
- The aspect ratio of the scaled transistor
  - $\frac{W}{L} = \frac{\tilde{W}}{\tilde{L}}$

# Scaling Theory

- The oxide capacitance is given by
  - $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$
  - If the new transistor has a thinner oxide that is decreased as  $\tilde{t}_{ox} = \frac{t_{ox}}{S}$ , then the scaled device has
$$\tilde{C}_{ox} = SC_{ox}$$
- The transconductance is increased in the scaled device to
  - $\tilde{\beta} = S\beta$
- The resistance is reduced in the scaled device to
  - $\tilde{R} = \frac{1}{S\beta(V_{DD} - V_T)} = \frac{R}{S}$
  - Assume that the supply voltage is not altered



# Scaling Theory

- On the other hand, if we can scale the voltages in the scaled device to the new values of

- $\tilde{V}_{DD} = \frac{V_{DD}}{S} \quad \tilde{V}_T = \frac{V_T}{S}$

- The resistance of the scaled device would be unchanged with  $\tilde{R} = R$

- The effects of scaling the voltage, consider a scaled MOS with reduced voltages of

- $\tilde{V}_{DS} = \frac{V_{DS}}{S} \quad \tilde{V}_{GS} = \frac{V_{GS}}{S}$

- The current of the scaled device is given by

- $\tilde{I}_D = \frac{S\beta}{2} \left[ \left( \frac{V_{GS}}{S} - \frac{V_T}{S} \right) \frac{V_{DS}}{S} \right] = \frac{I_D}{S}$

- The power dissipation of the scaled device is

- $\tilde{P} = \tilde{V}_{DS} \tilde{I}_D = \frac{V_{DS} I_D}{S^2} = \frac{P}{S^2}$

# Summary

- We have presented models that allow us to estimate circuit timing performance, and power dissipation
- Guidelines for low-power design have also been presented
- The concepts of design margining were also introduced
- The scaling theory has also introduced