

Chapter 7

Sequential Circuits

Jin-Fu Li

Advanced Reliable Systems (ARES) Lab.
Department of Electrical Engineering
National Central University
Jungli, Taiwan

Outline

- Latches & Registers
- Sequencing Timing Diagram


Sequencing

□ *Combinational logic*


- Output depends on current inputs

□ *Sequential logic*

 - Output depends on current and previous inputs
- Requires separating previous, current, future
- Called *state* or *tokens*
- Ex: FSM, pipeline




Finite State Machine

 

Pipeline


Sequencing Elements

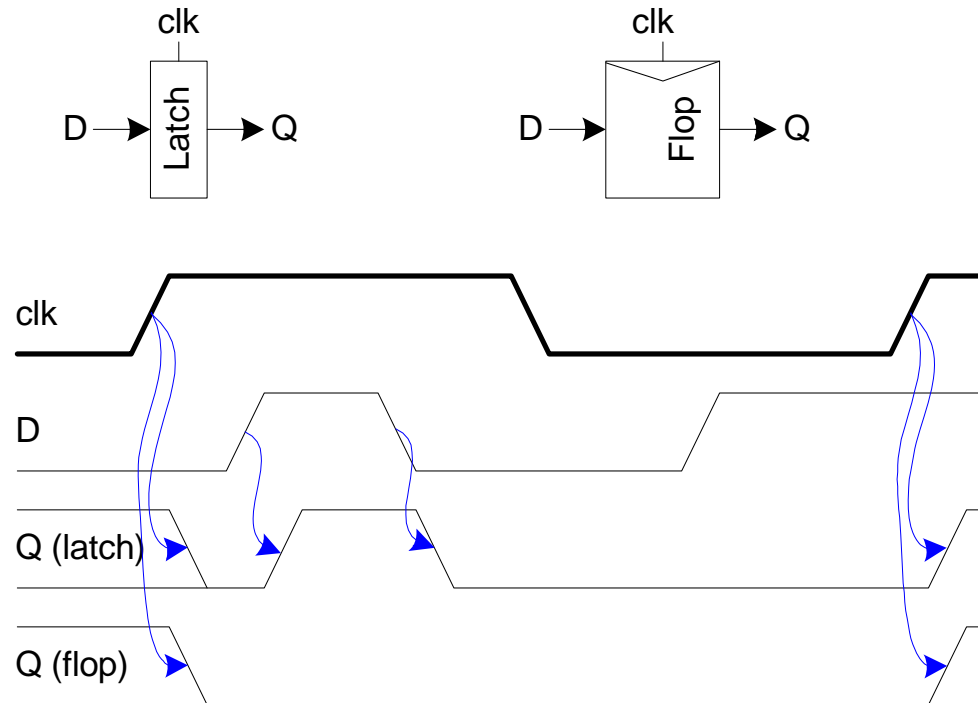- **Latch:** Level sensitive
 - A.k.a. transparent latch, D latch
- **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger




Latches

❑ Negative-level sensitive latch

 


❑ Positive-level sensitive latch

 


Registers

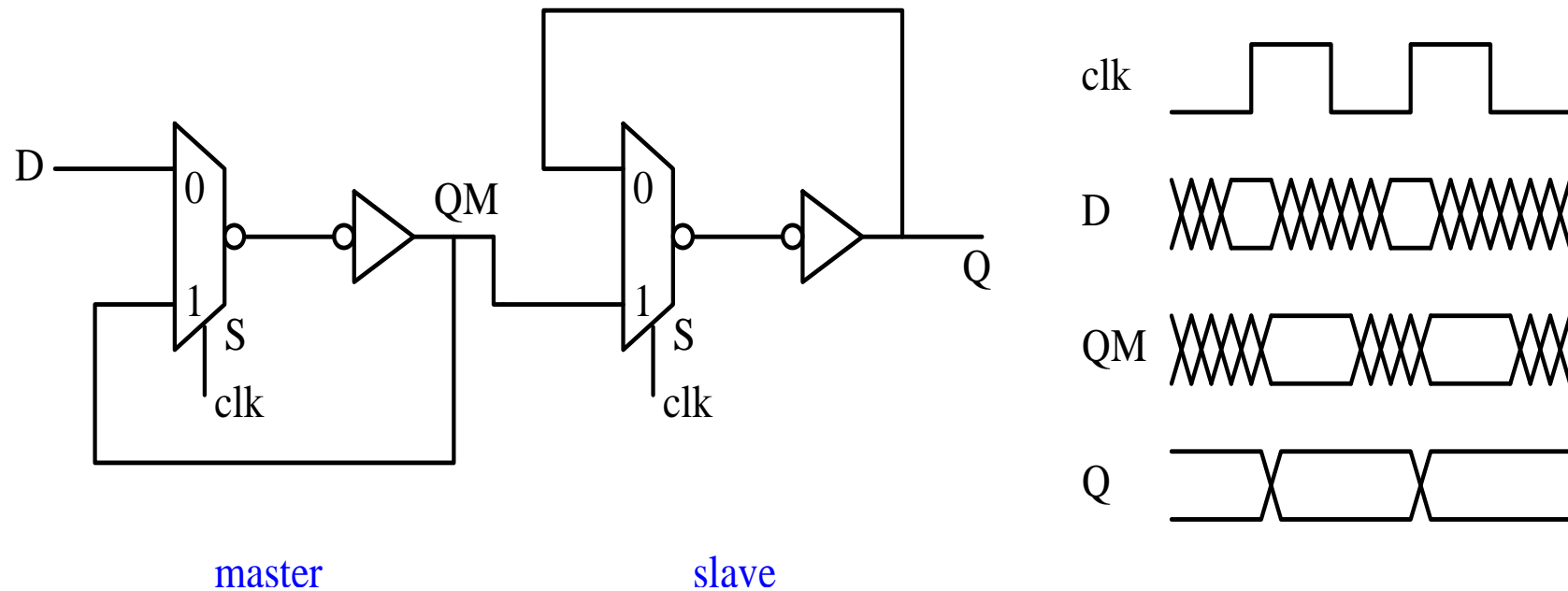- Positive-edge triggered register (single-phase clock)




Registers

 - Operations of the positive-edge triggered register




Registers

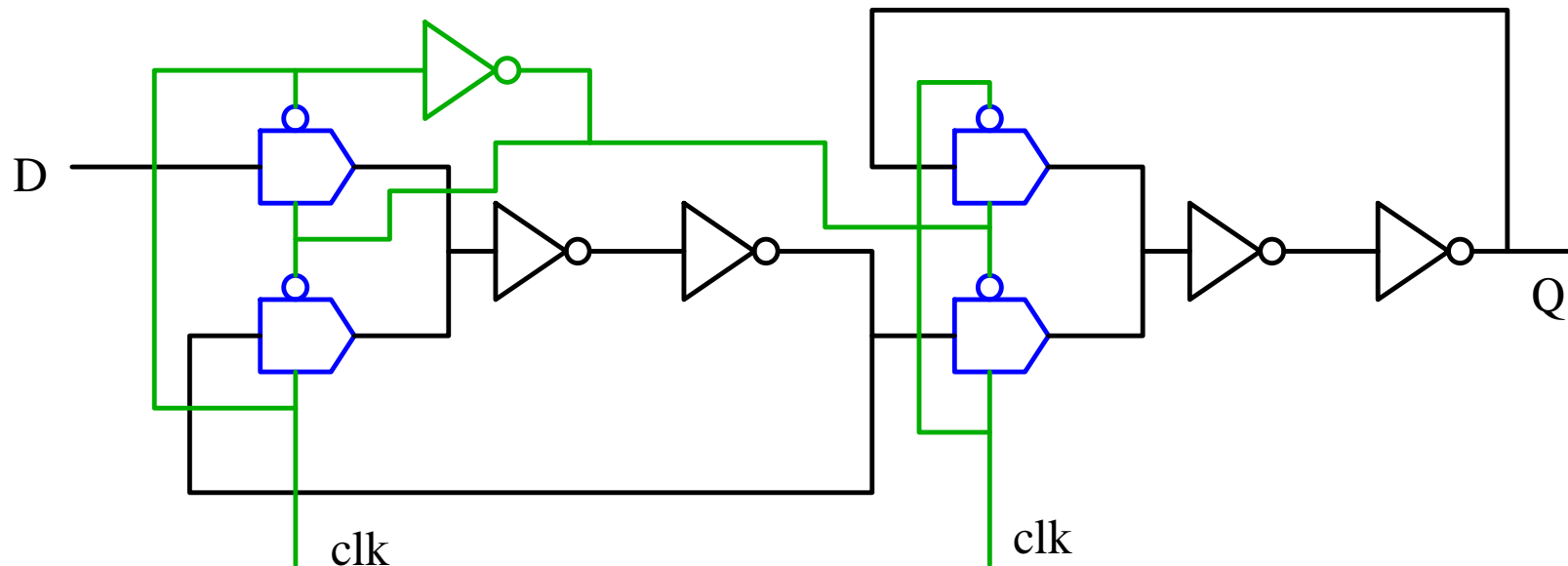- ❑ CMOS circuit implementation of the positive-edge triggered register




Single-Phase Latch



□ Positive active-static latch

 

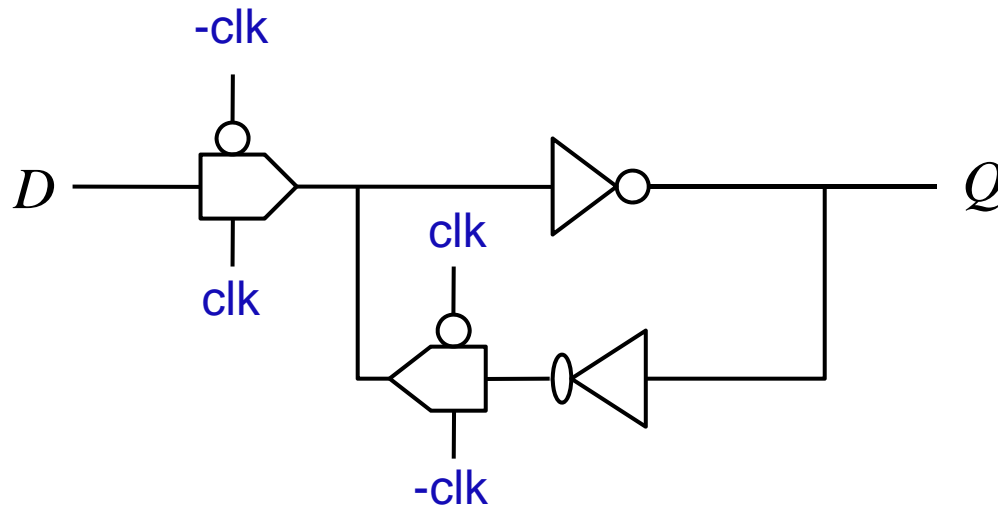1. Low area cost
2. Driving capability of D must override the feedback inverter




Typical Latch Symbolic Layouts

  


CVSL (Differential) Style Register

 - The following figure shows latches based on a CVSL structure
 - An N and a P version are shown that are cascaded to form a register




Double-Edge Triggered Register

 - The following figure shows latches that may be used to clock data on both edges of the clock




Double-Edge Triggered Register

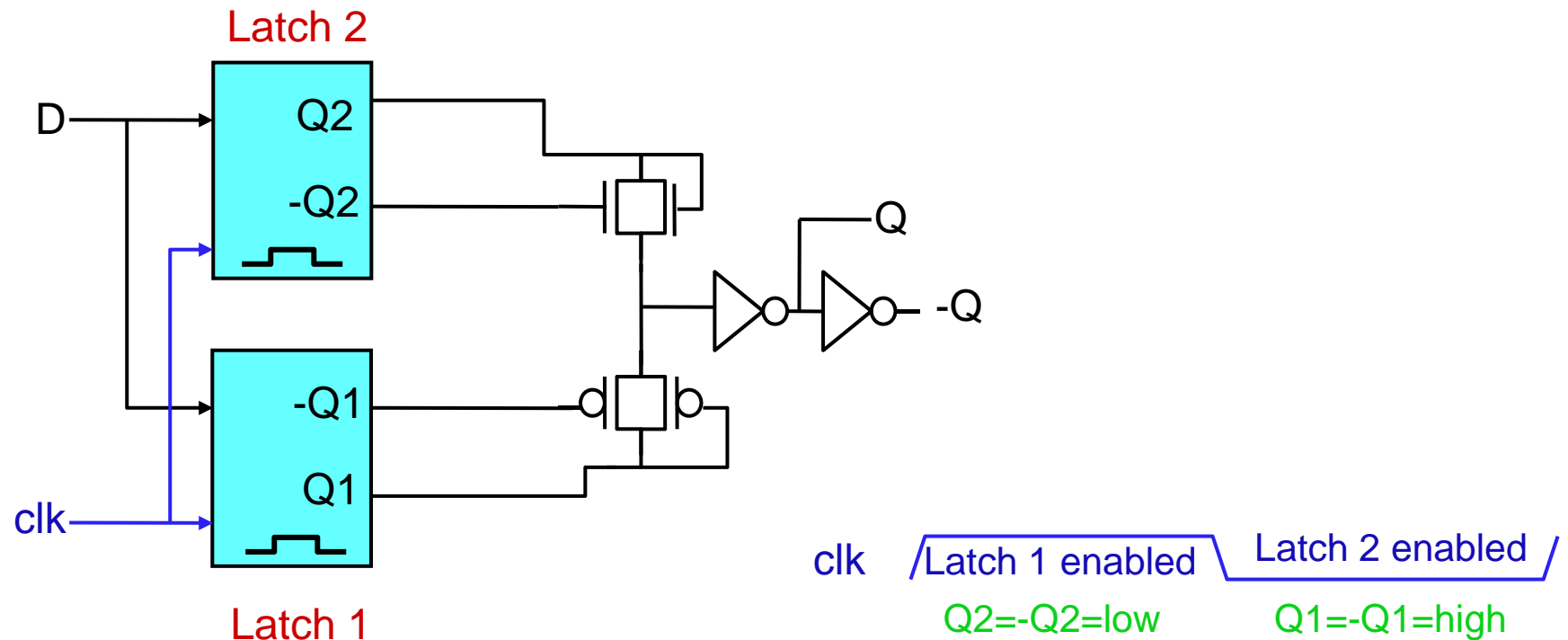- Double-edge triggered register can be implemented by combining Latch 1 & Latch 2 as follows




Asynchronously Register

- Asynchronously resettable register

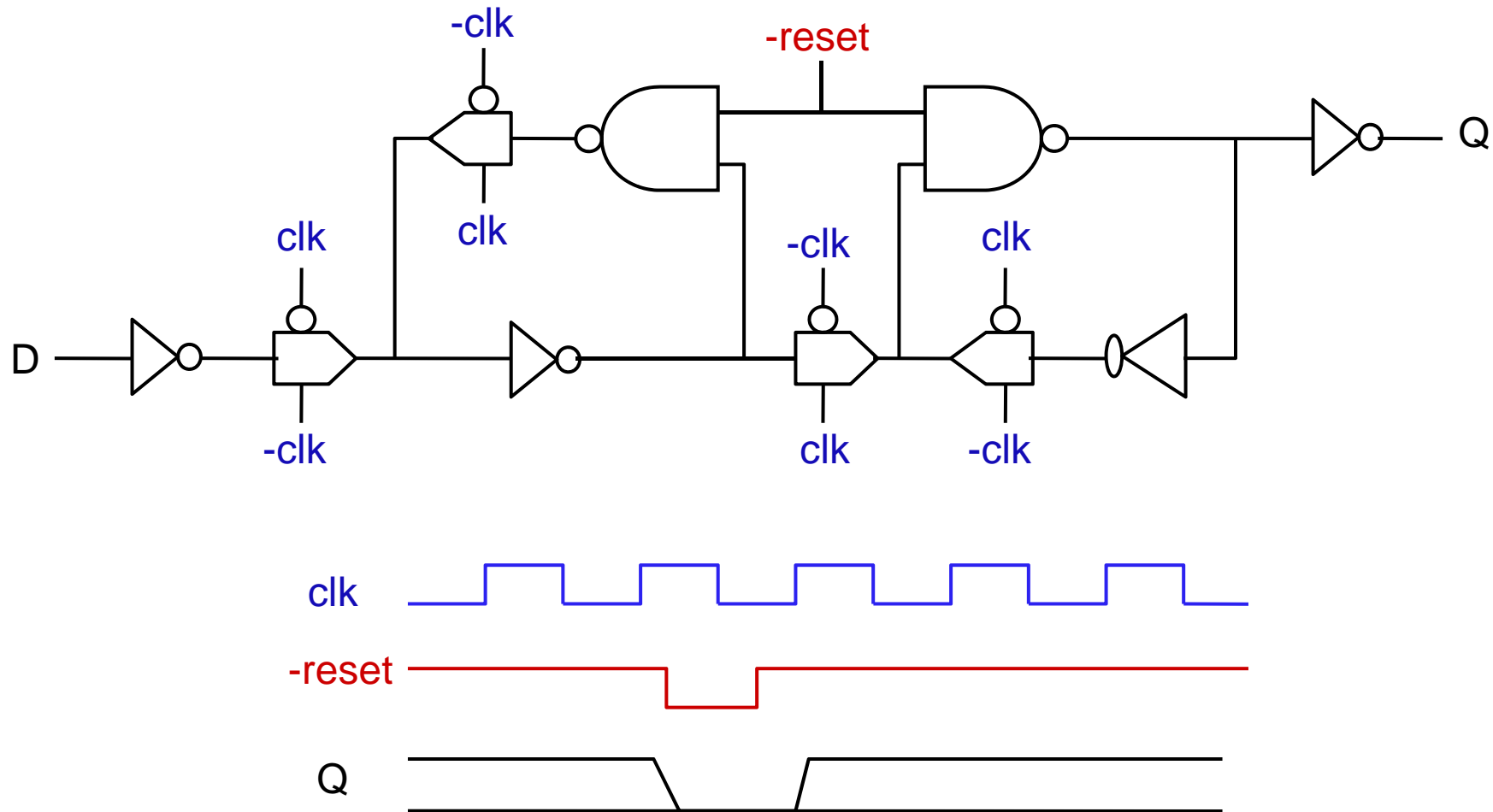


Asynchronously Register

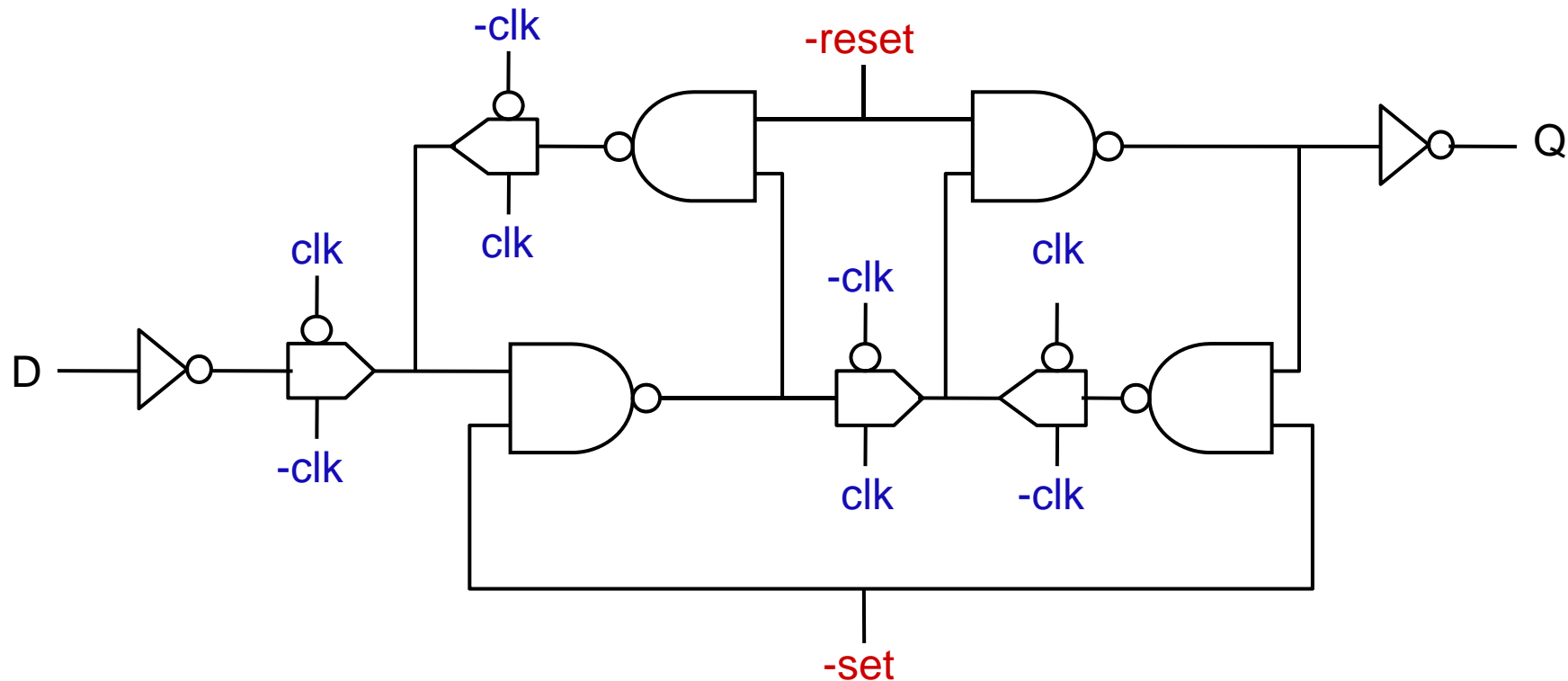- Asynchronously resettable and settable register




Dynamic Latches & Registers

□ Dynamic single clock latches

 


□ Dynamic single clock registers

 


Dynamic Latches

□ Clock active high latch

 


D_n	CLK	X_n	Q_n
0	H	1	0
1	H	0	1
1	L	X_{n-1}	Q_{n-1}
0	L	1	Q_{n-1}

□ Clock active high latch with buffer

 


Dynamic Latches

□ Clock active low latch

 


D_n	CLK	X_n	Q_n
0	L	1	0
1	L	0	1
1	H	0	Q_{n-1}
0	H	X_{n-1}	Q_{n-1}

□ Clock active low latch with buffer

 

Dynamic Latches

 
- Clock active high and low latches without feedback



- The problem of leakage current
 - Assume that the capacitance of node X is 0.002pF and the leakage current I is 1nA
 - Therefore, $T = CV/I = 0.002\text{pF} \times 5\text{V} / 1\text{nA} = 100\text{us}$
 - That is, the latch needs to be refreshed each 100us. Otherwise, the output Q will become high

Sequencing Methods






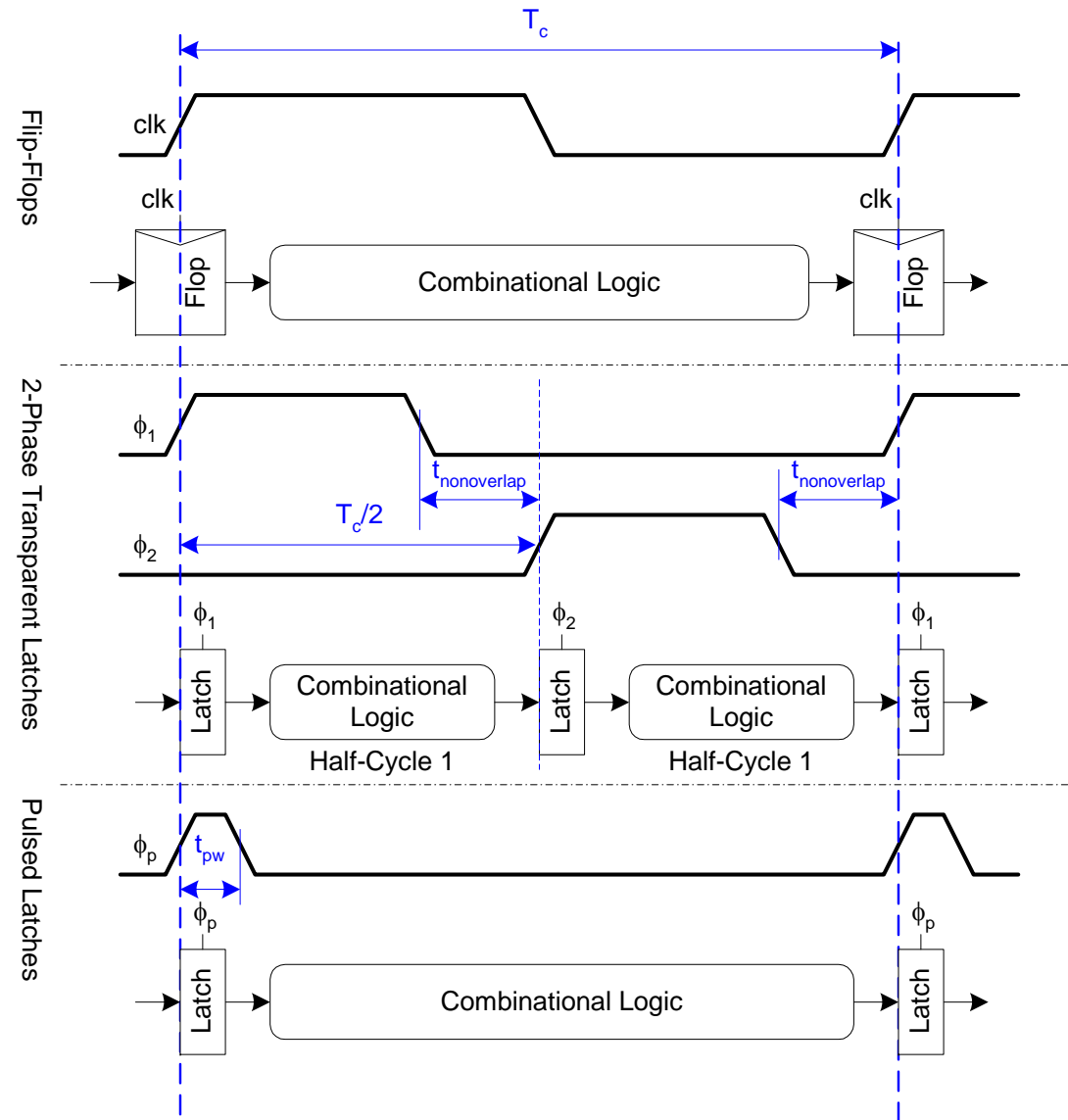
- Flip-flops
- 2-Phase Latches
- Pulsed Latches



Timing Diagrams


Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk-Q Prop Delay
t_{ccq}	Latch/Flop Clk-Q Cont. Delay
t_{pdq}	Latch D-Q Prop Delay
t_{pcq}	Latch D-Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

      


Max-Delay: Flip-Flops
 
$$t_{pd} \leq T_c - \underbrace{(t_{\text{setup}} + t_{pcq})}_{\text{sequencing overhead}}$$




Max Delay: 2-Phase Latches
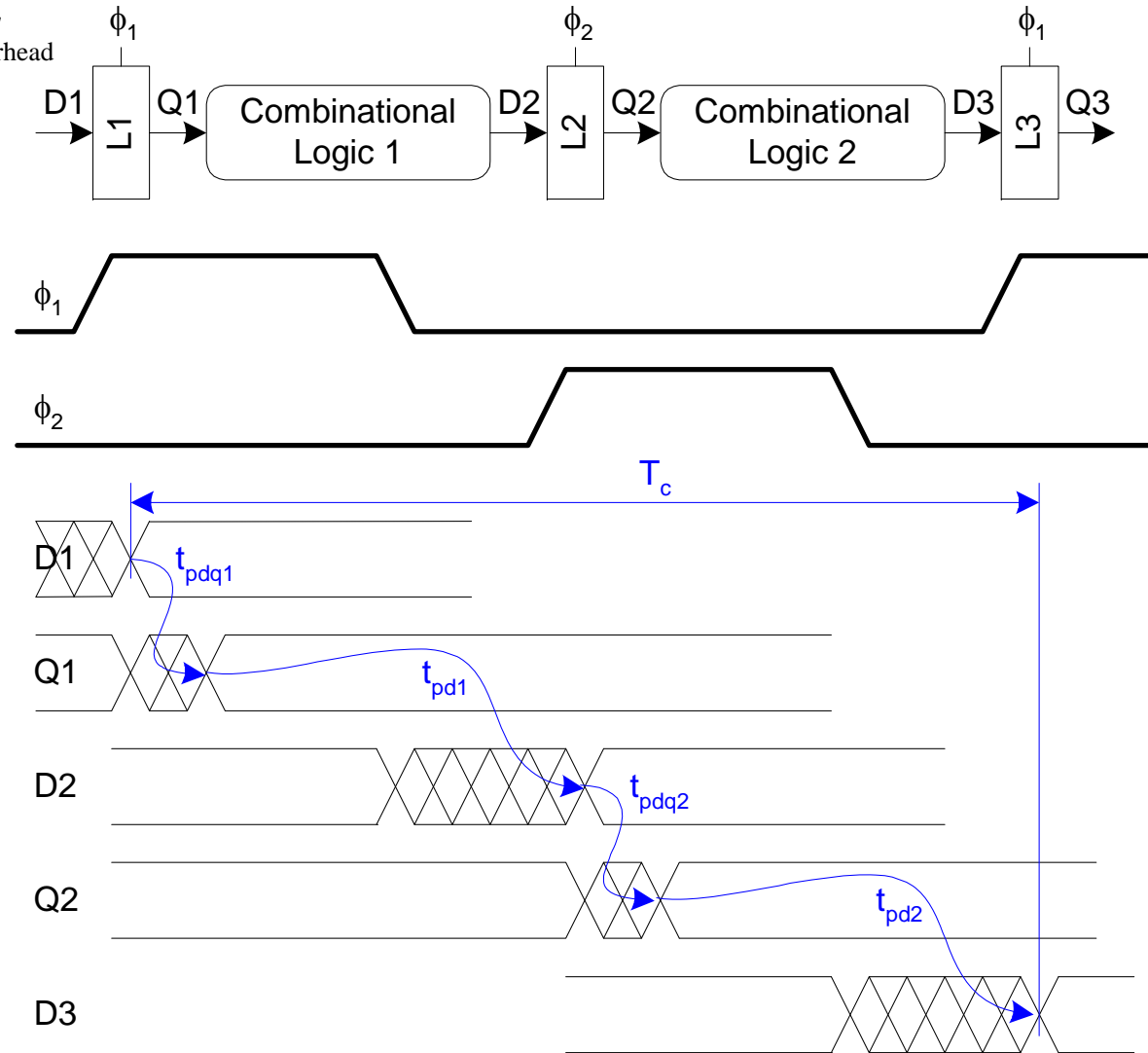
$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$




Max Delay: Pulsed Latches
 
$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw})}_{\text{sequencing overhead}}$$



Min-Delay: Flip-Flops
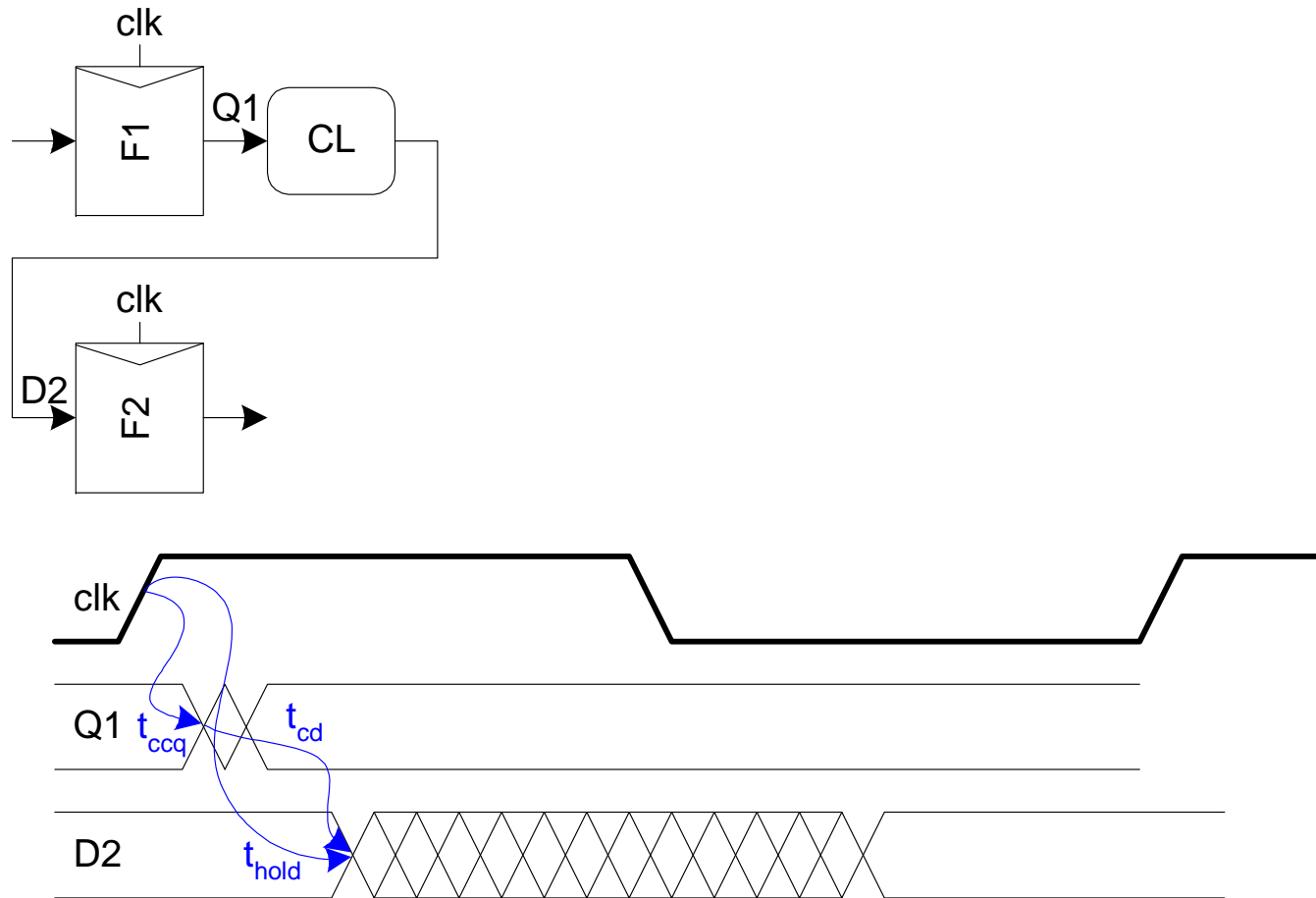
$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$




Min-Delay: 2-Phase Latches

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}}$$

Hold time reduced by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.


But a flop is made of two latches!

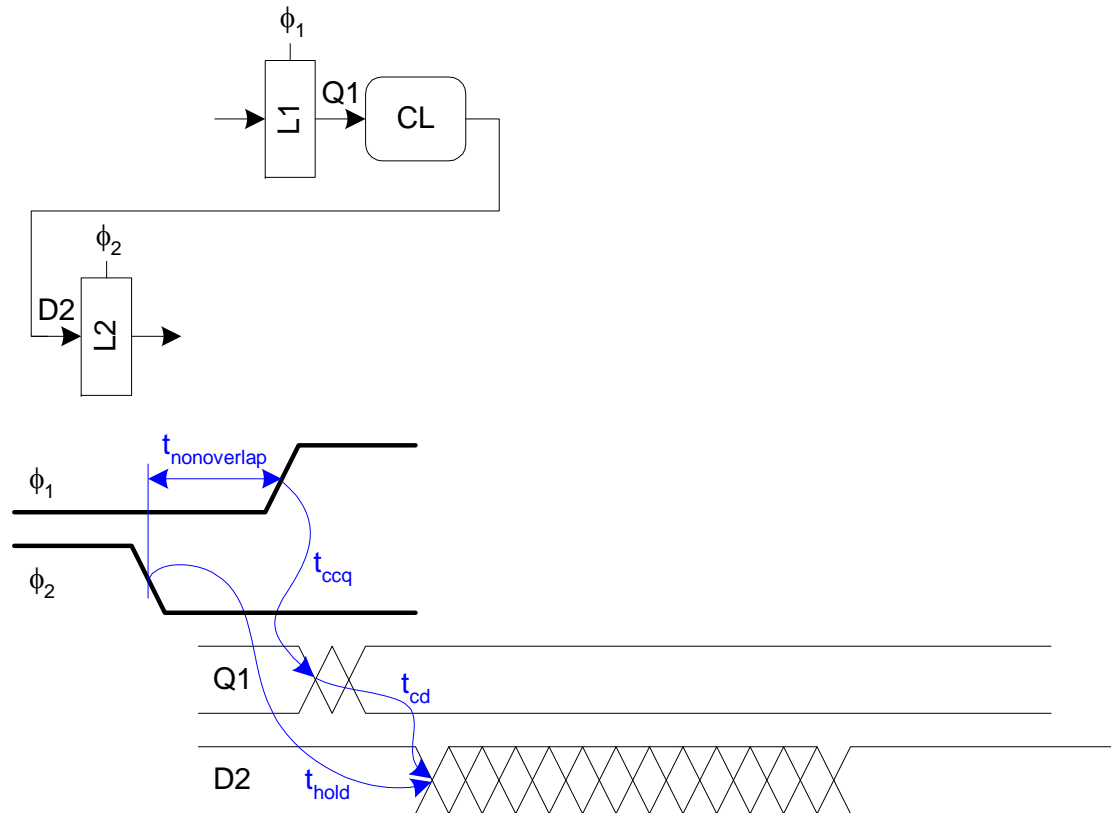

Min-Delay: Pulsed Latches

$$t_{cd} \geq t_{\text{hold}} - t_{ccq} + t_{pw}$$


Hold time increased
by pulse width

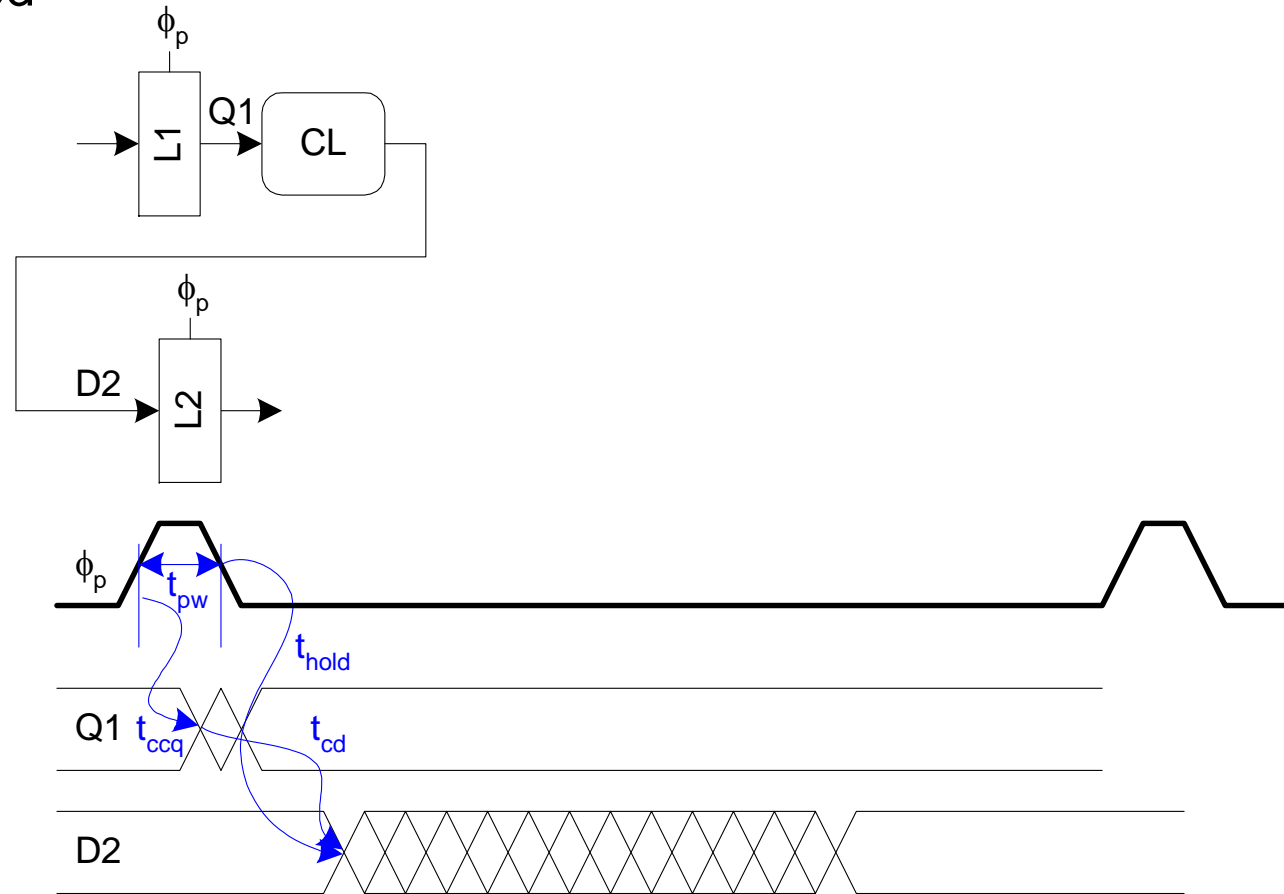

Time Borrowing

- In a flop-based system:
 - Data launches on one rising edge
 - Must setup before next rising edge
 - If it arrives late, system fails
 - If it arrives early, time is wasted
 - Flops have hard edges
- In a latch-based system
 - Data can pass through latch while transparent
 - Long cycle of logic can borrow time into next
 - As long as each loop completes in one cycle

Time Borrowing Example

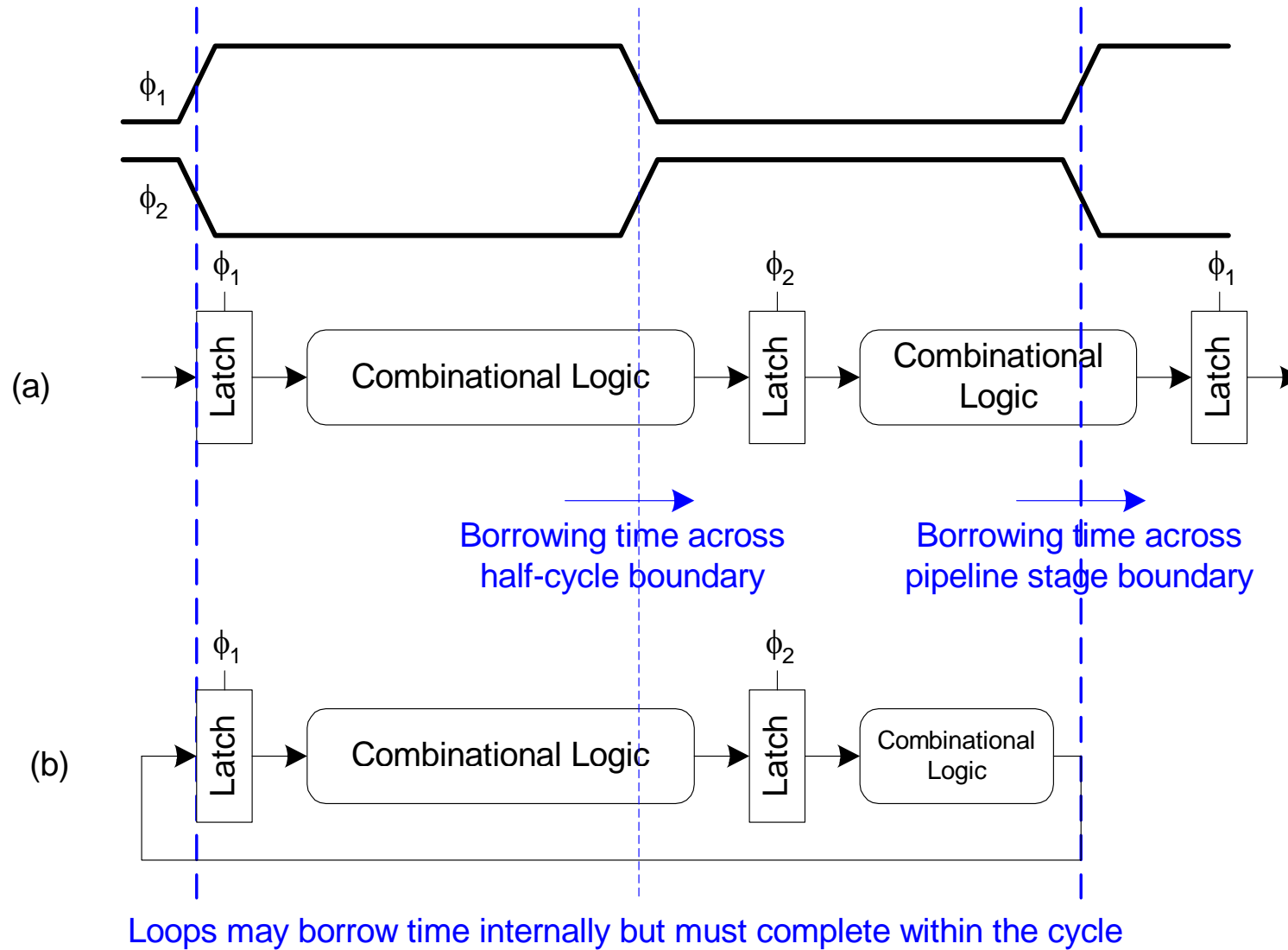


How Much Borrowing?

2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$

Pulsed Latches
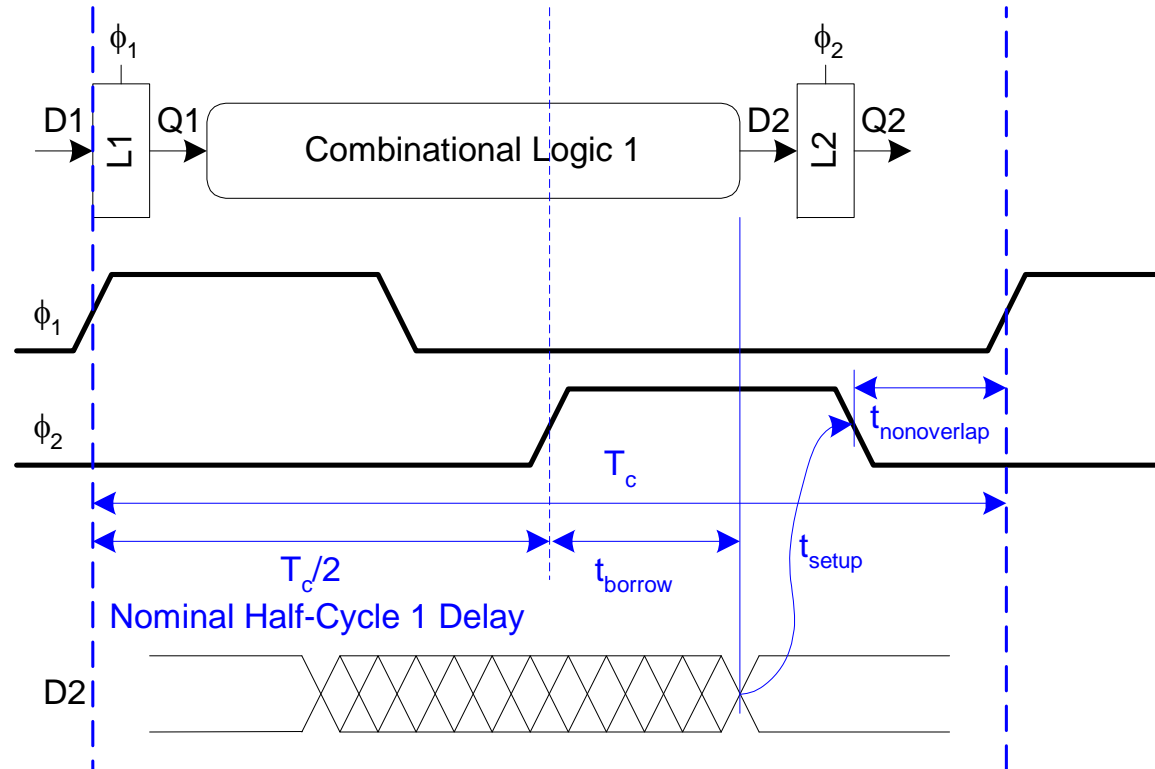
$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$





Clock Skew

- We have assumed zero clock skew
- Clocks really have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay
 - Decreases time borrowing

Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
 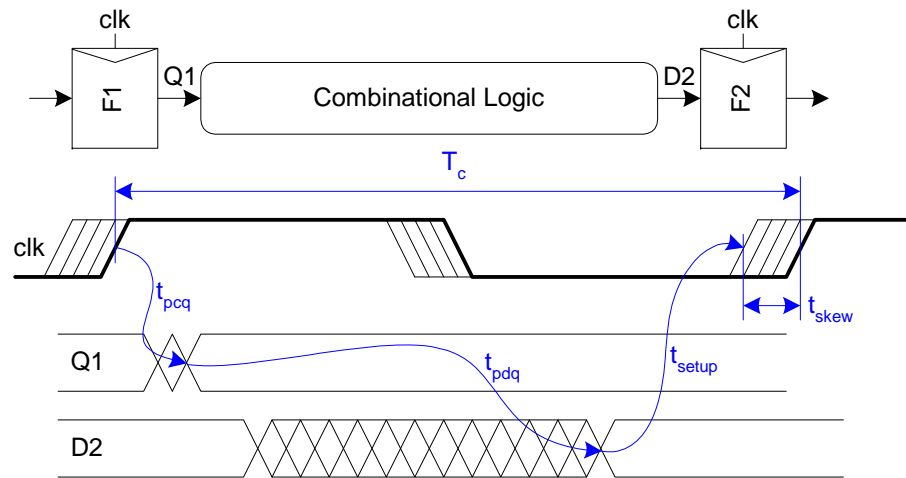
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




Skew: Latches

2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$
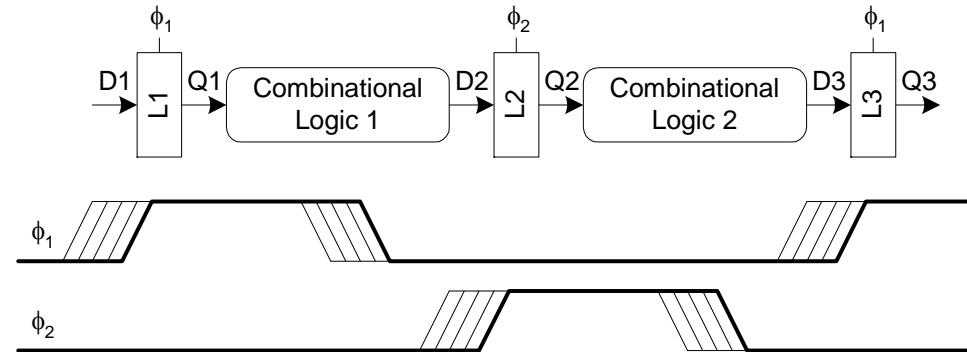
$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$



Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw} + t_{\text{skew}})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{\text{hold}} + t_{pw} - t_{ccq} + t_{\text{skew}}$$


$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$

Two-Phase Clocking

- If setup times are violated, reduce clock speed
- If hold times are violated, chip fails at any speed
- In this class, working chips are most important
 - No tools to analyze clock skew
- An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)

Safe Flip-Flop

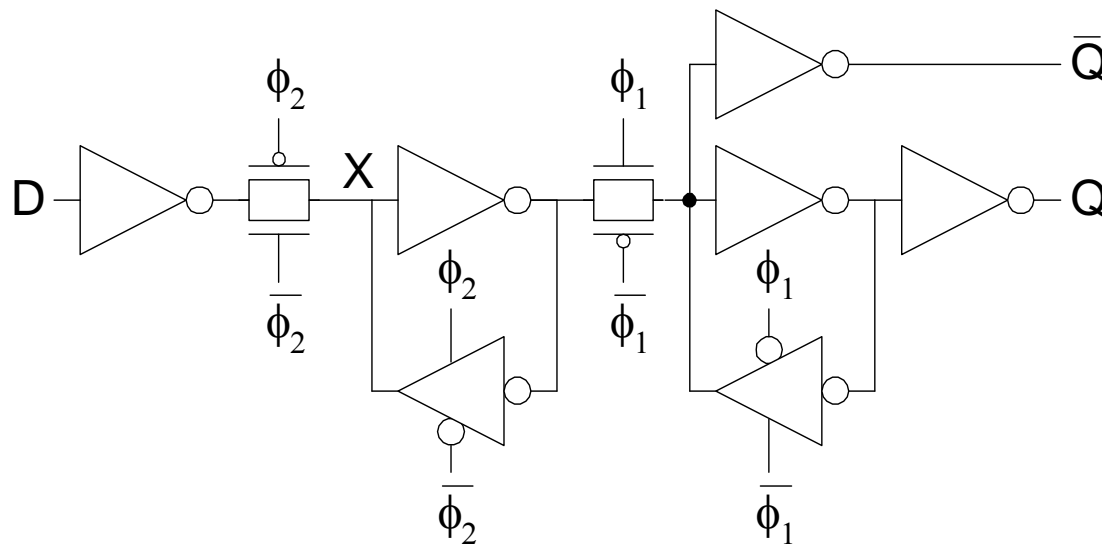- In class, use flip-flop with nonoverlapping clocks
 - Very slow - nonoverlap adds to setup time
 - But no hold times
- In industry, use a better timing analyzer
 - Add buffers to slow signals if hold time is at risk




Clock Distribution

- In a large CMOS chip, clock distribution is a serious problem
 - For example,
 - $V_{dd}=5V$
 - $C_{reg}=2000pF$ (20K register bits @ 0.1pF)
 - $T_{clk}=10ns$
 - $T_{rise/fall}=1ns$
 - $I_{peak}=C(dv/dt)=(2000p)\times(5/1n)=10A$
 - $P_d=C(V_{dd})^2f=2000p\times25\times100=5W$
- Methods for reducing the values of I_{peak} and P_d
 - Reduce C
 - Interleaving the rise/fall time


Clock Distribution

- Clocking is a floorplanning problem because clock delay varies with position on the chip
- Ways to improve clock distribution
 - Physical design
 - Make clock delays more even
 - At least more predictable
 - Circuit design
 - Minimizing delays using several stages of drivers
- Two most common types of physical clocking networks
 - H-tree clock distribution
 - Balanced-tree clock distribution

H-Tree Clock Distribution

 


H-Tree Clock Distribution

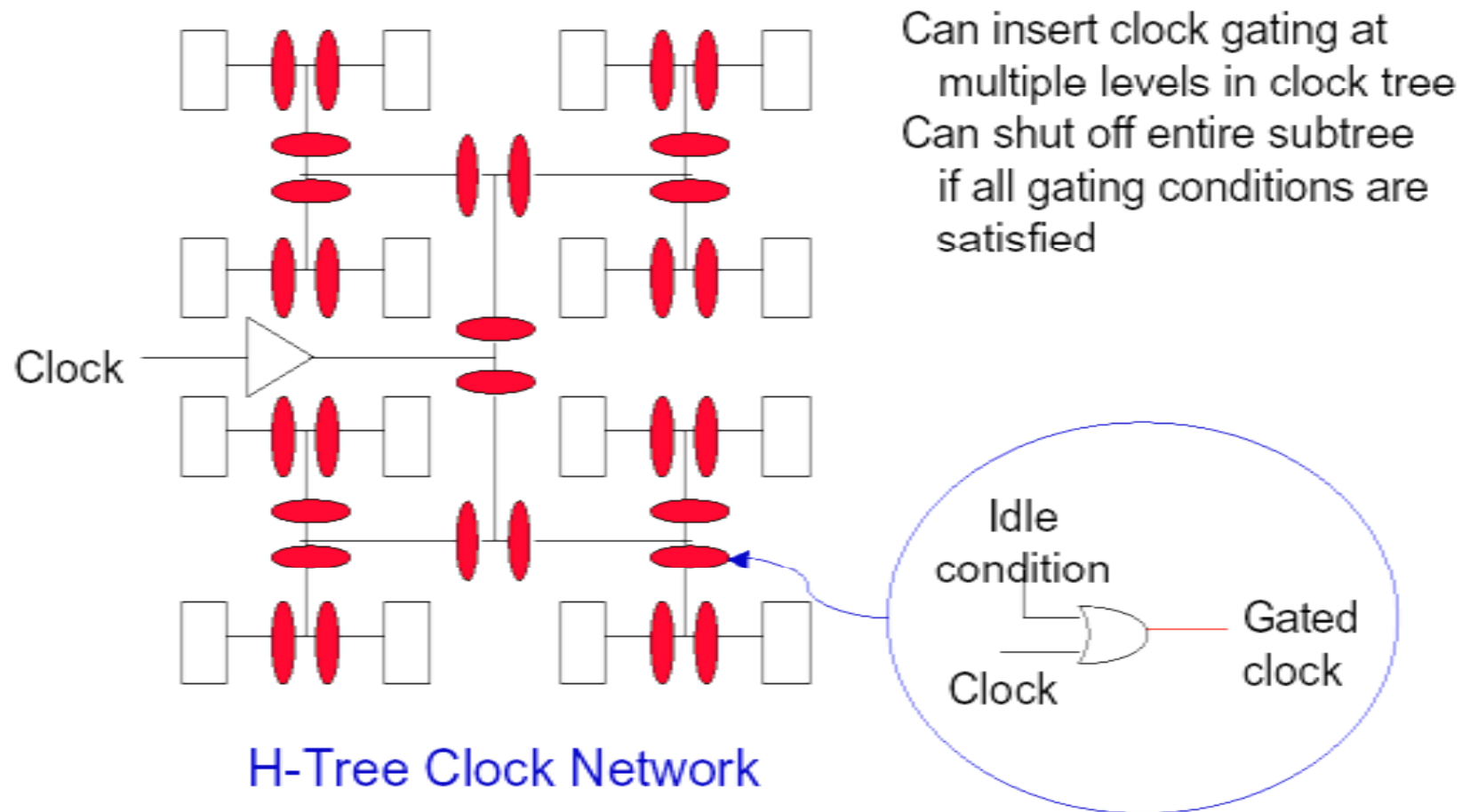


Source: Prof. Irwin

Balanced-Tree Clock Distribution

 


Reduce Clocking Power

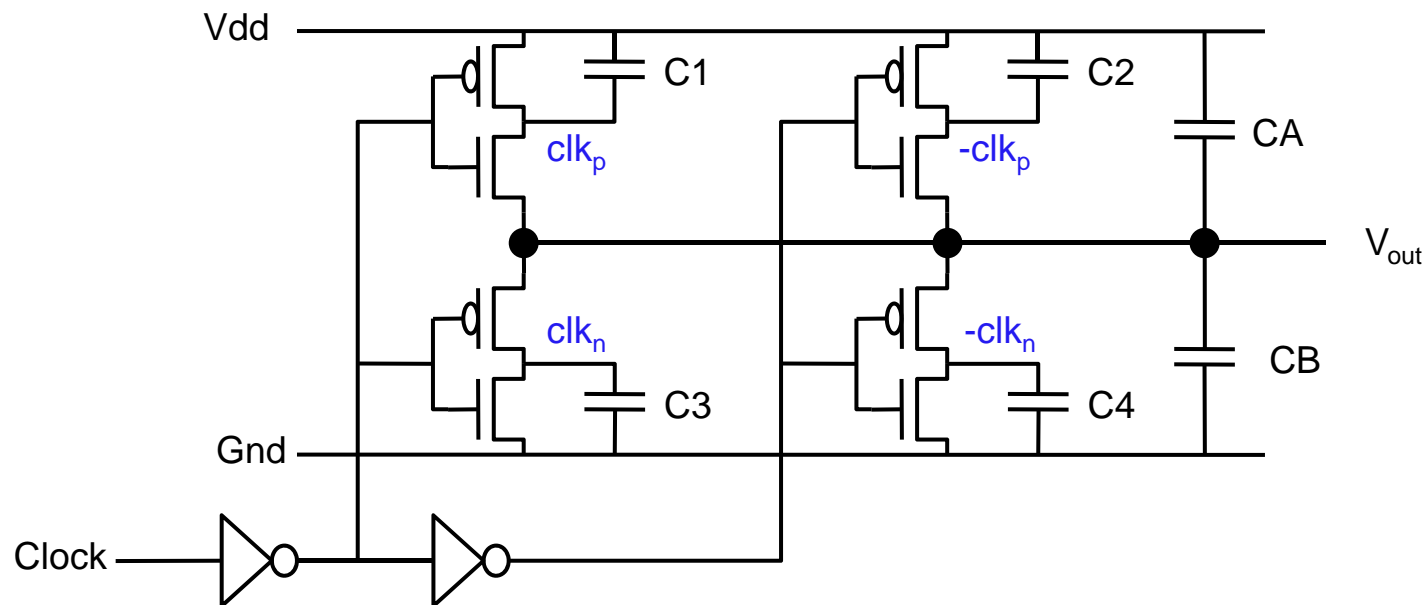
- Techniques used to reduce the high dynamic power dissipation
 - Use a low capacitance clock routing line such as metal3. This layer of metal can be, for example, dedicated to clock distribution only
 - Using low-swing drivers at the top level of the tree or in intermediate levels



Power & Ground Distribution

 

(a) Finger-shaped network

 

(b) Network with multiple supply pins

Source: Prof. Irwin