

Chapter 1

Introduction to Memories

Jin-Fu Li

Advanced Reliable Systems (ARES) Lab.

Dept. of Electrical Engineering

National Central University

Jhongli, Taiwan

Outline


- Importance of Embedded Memories
- Overview of Memory Structures

Embedded Memory – The Key to SOC

- Embedded memory is becoming more central to integrated circuit design
- Historically, ICs were dominated by the logic functions, with memory being external
- Today, an SOC contains many memory blocks of different sizes, shapes and functionality
 - Typically, embedded memories represent about 30%~50% SOC area
- The Semiconductor Industry Association (SIA) predicts that 90% of the SOC's surface will be memory in 2011

Embedded Memory – The Key to SOC

- SOC memory continues to increase

 

Source: SIA, ITRS, 2000

Embedded Memory – Advantages

- Area
 - Embedding multiple memories on a single SOC reduces the amount of silicon used
- Performance
 - Embedding faster, wider memories and moving them closer to processor can increase system performance substantially
- Power
 - Embedded memories eliminate the need to drive off-chip capacitance between the stand-alone memories and other system chips
- Design reuse
 - By reusing embedded memories, system designers can significantly reduce develop time and cost

Embedded Memory – Quality

- During manufacture
 - Yield
 - Exponential yield model
 - $Y = e^{-\sqrt{AD}}$, where A and D denote the area and defect density, respectively
- After manufacture
 - Reliability
- During use
 - Soft error rate


Quality During Manufacture

- Issues of embedded memory
 - As the density of transistors is increased, the D is increased compared to logic
 - About 2X logic for high density 6-T SRAM
- Solutions
 - Redundancy & laser repair using ATE
 - Error correction code (ECC)
- Redundancy & repair
 - Achieve yield parity with logic, or better
 - About 3% area overhead
 - Recommended over 1Mb

Quality During Manufacture


- Corrects <5 defects per Mb
- Laser repair manufacturing flow
- ECC
 - Detect/repair defects in individual words
 - 25-30% area overhead
 - * Ex: 6 extra bits for single bit correction in 32 bit words
 - Latency penalty
 - * At least one clock cycle latency penalty

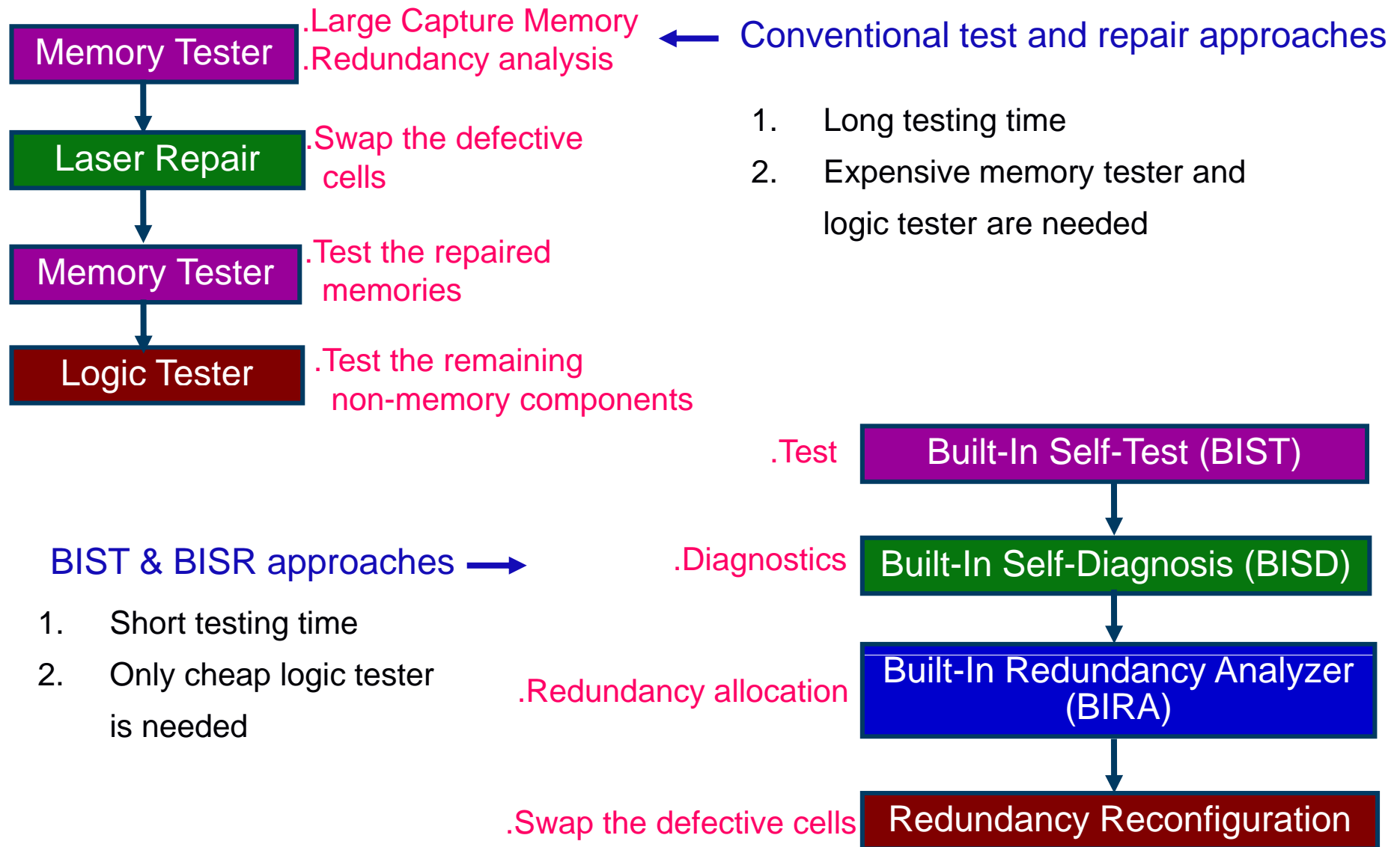Quality-Insurance Strategies for Memories




Introduction to Memories

- Overview of semiconductor memory types

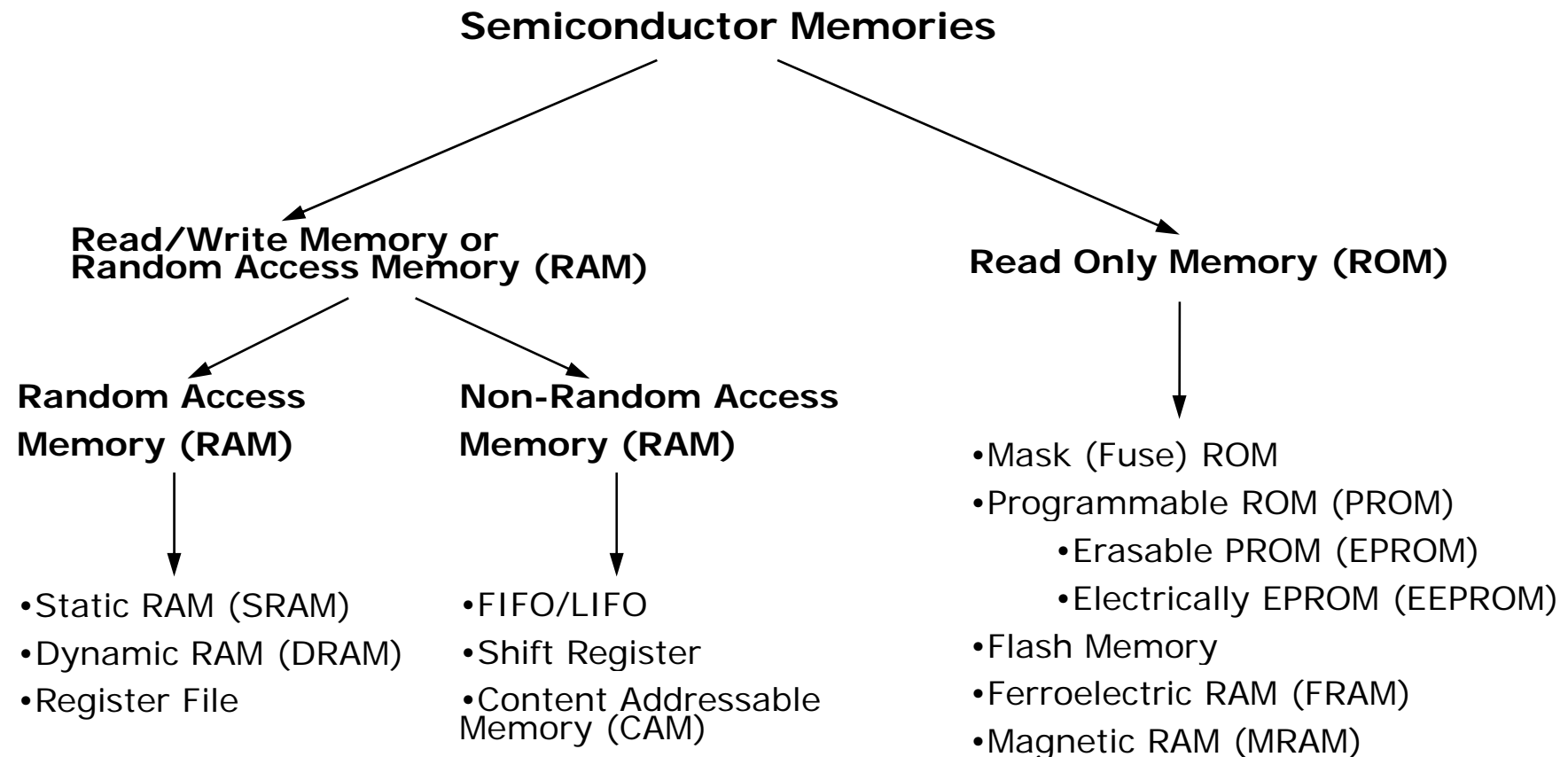


Memory Elements – Memory Architecture

 
- Volatile memories may be divided into the following categories
 - Random access memory
 - Serial access memory
 - Content addressable memory
- Memory architecture



1-D Memory Architecture

 


n select signals: S_0-S_{n-1}

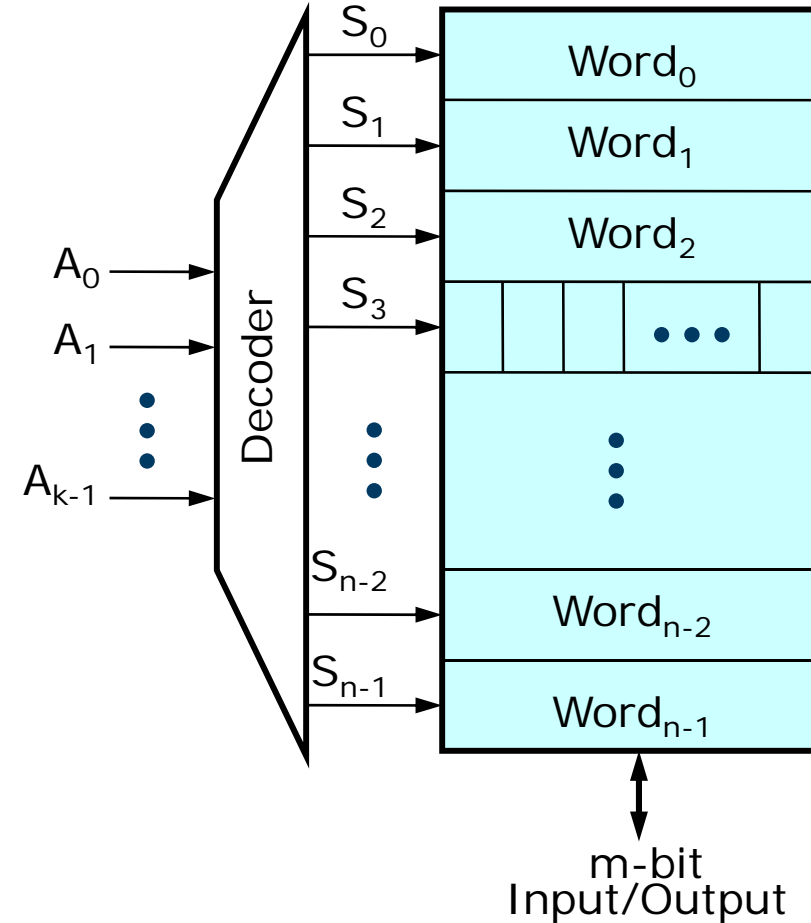


n select signals are reduced to k address signals: A_0-A_{k-1}


2-D Memory Architecture

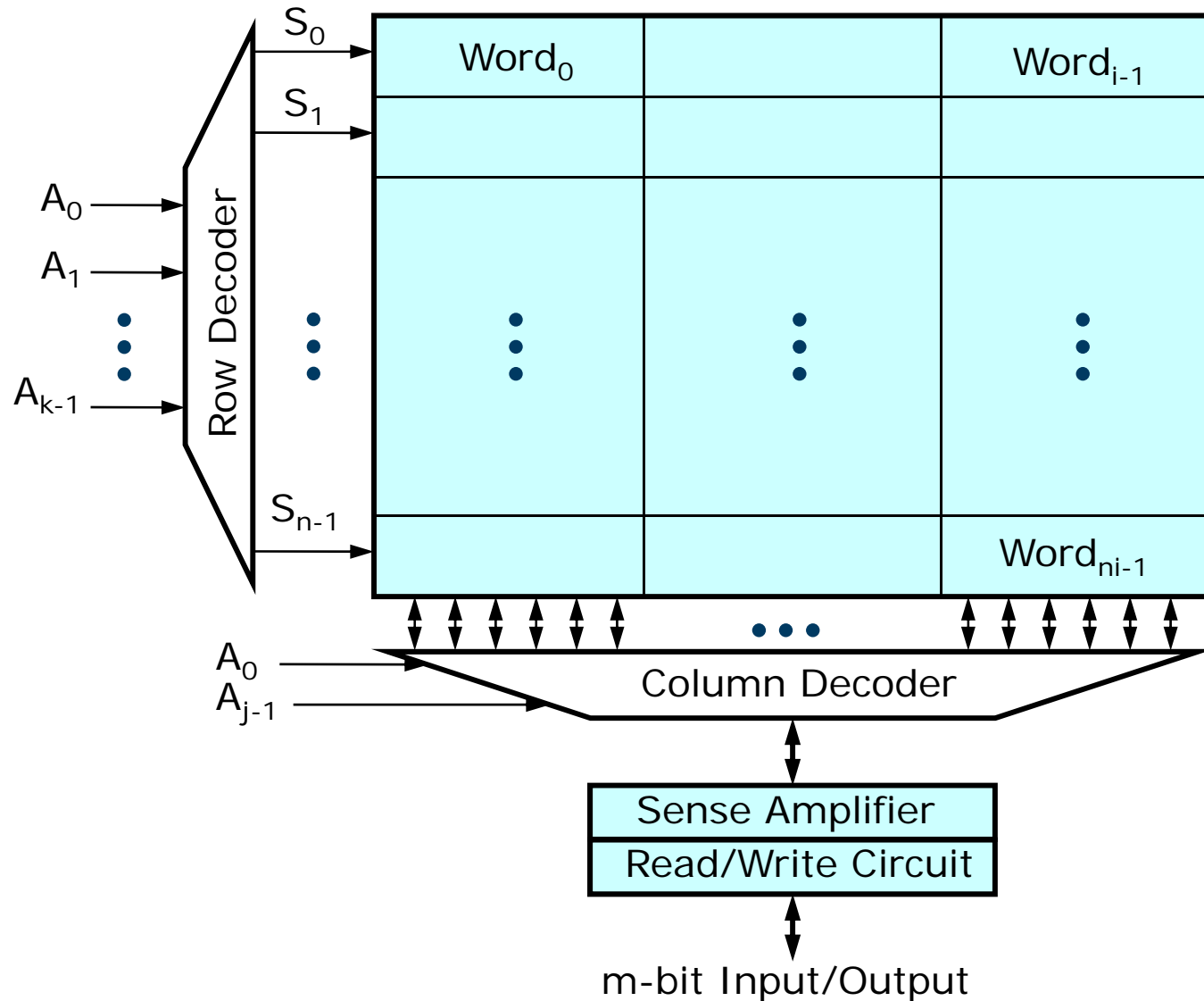

3-D Memory Architecture

 


Conceptual 2-D Memory Organization

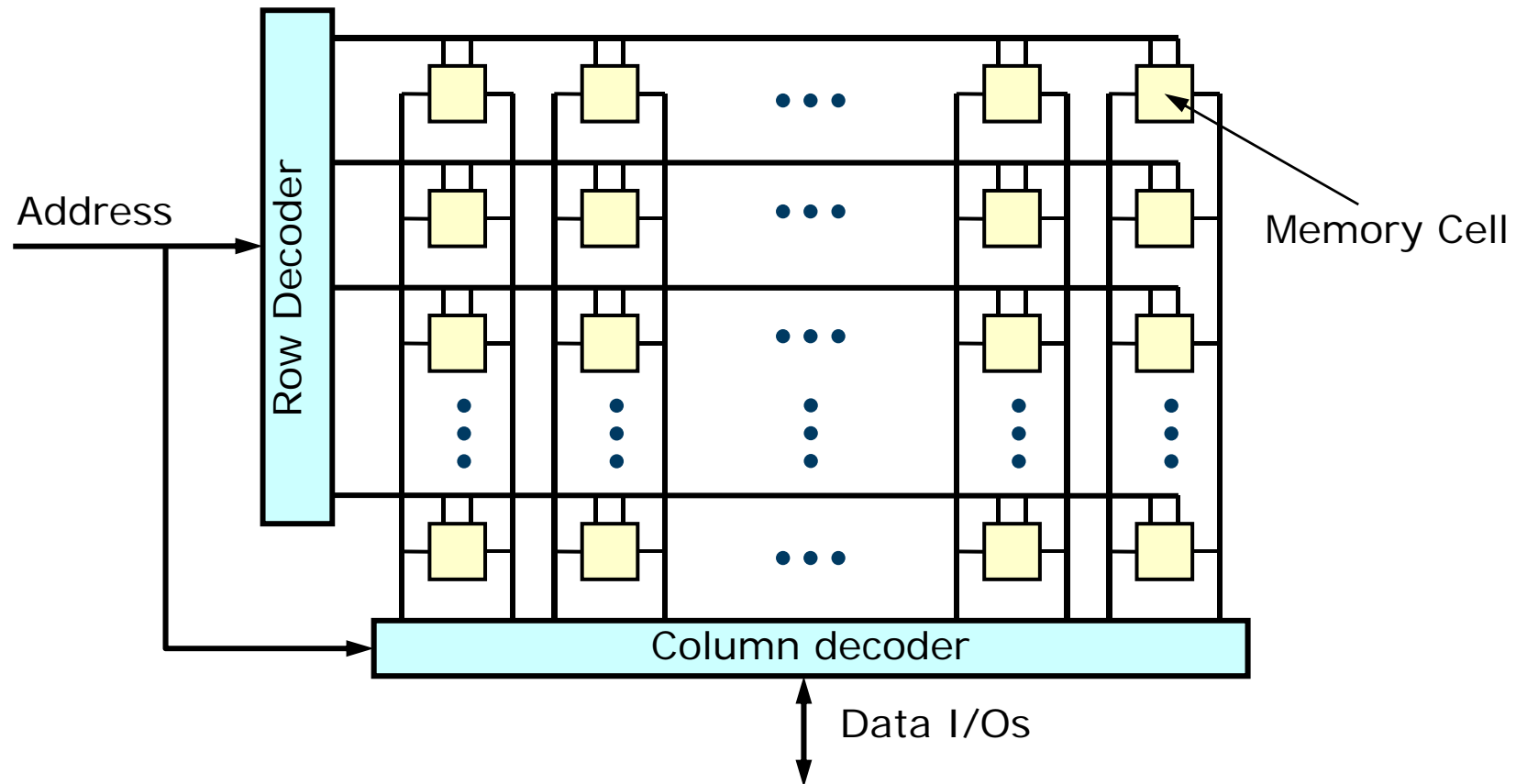


Memory Elements – RAM

Generic RAM circuit

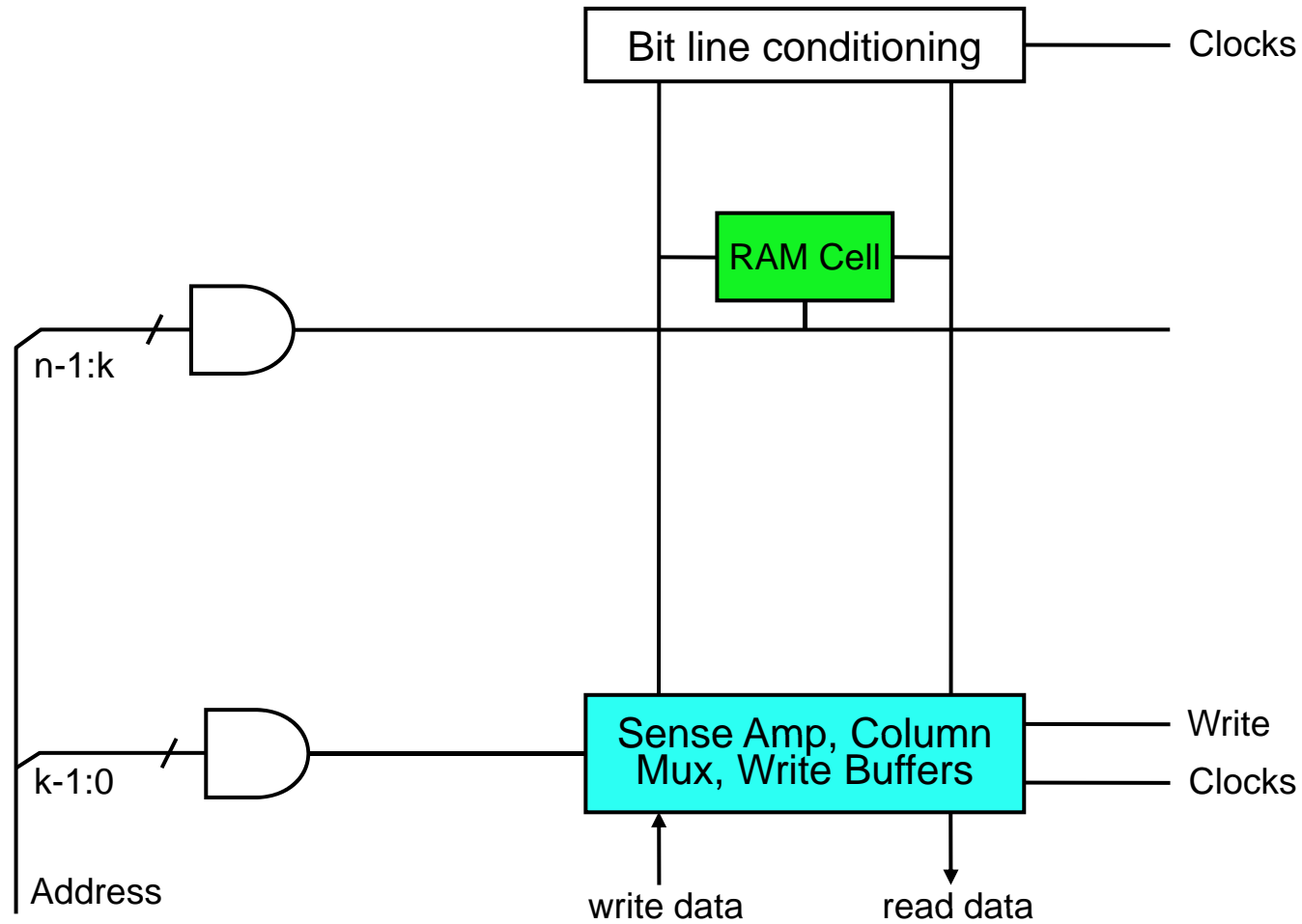


Memory Elements – RAM Cells

6-T SRAM cell


 


4-T SRAM cell

 


Memory Elements – RAM Cells

1-T DRAM cell

 
 


Layout of 1-T DRAM (right)

 

Memory Elements – DRAM Retention Time



Write and hold operations in a DRAM cell

 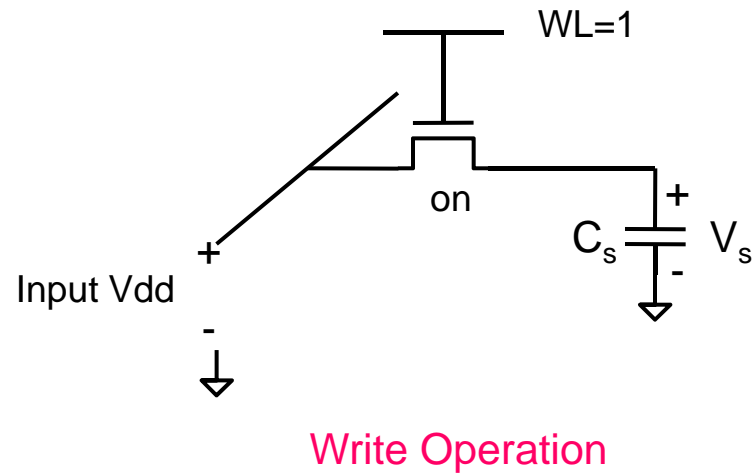

$$V_s = V_{\max} = V_{DD} - V_{tn}$$
$$Q_{\max} = C_s (V_{DD} - V_{tn})$$

Memory Elements – DRAM Retention Time

Charge leakage in a DRAM Cell

  

$$I_L = - \left(\frac{dQ_s}{dt} \right)$$

$$I_L = - C_s \left(\frac{dV_s}{dt} \right)$$

$$I_L \approx - C_s \left(\frac{\Delta V_s}{\Delta t} \right)$$

$$t_h = | \Delta t | \approx \left(\frac{C_s}{I_L} \right) \Delta V_s$$

Memory Elements – DRAM Refresh Operation

As an example, if $I_L=1\text{nA}$, $C_s=50\text{fF}$, and the difference of V_s is 1V, the hold time is


$$t_h = \frac{50 \times 10^{-15}}{1 \times 10^{-9}} \times 1 = 0.5 \mu\text{s}$$

Memory units must be able to hold data so long as the power is applied. To overcome the charge leakage problem, DRAM arrays employ a **refresh operation** where the data is periodically read from every cell, amplified, and rewritten.

The refresh cycle must be performed on every cell in the array with a minimum refresh frequency of about

$$f_{\text{refresh}} \approx \frac{1}{2t_h}$$

Memory Elements – DRAM Read Operation

 



$$Q_s = C_s V_s$$

$$Q_s = C_s V_f + C_{bit} V_f$$



$$V_f = \left(\frac{C_s}{C_s + C_{bit}} \right) V_s$$

This shows that $V_f < V_s$ for a store logic 1. In practice, V_f is usually reduced to a few tenths of a volt, so that the design of the sense amplifier becomes a critical factor



Memory Elements – RAM Read Operation

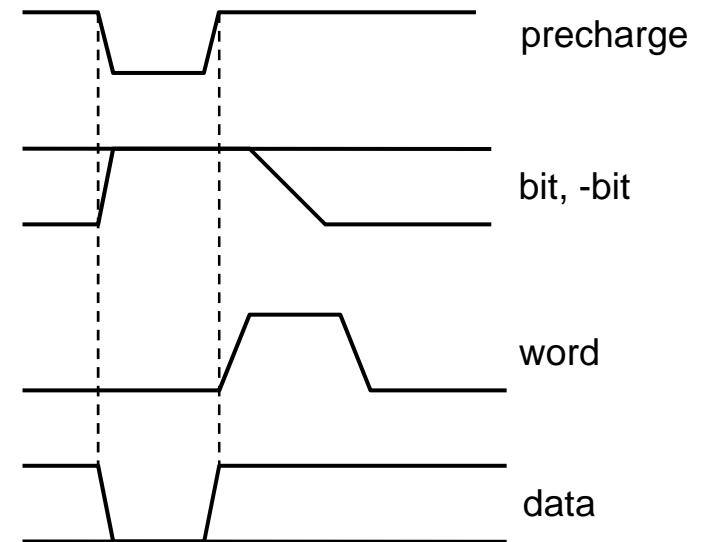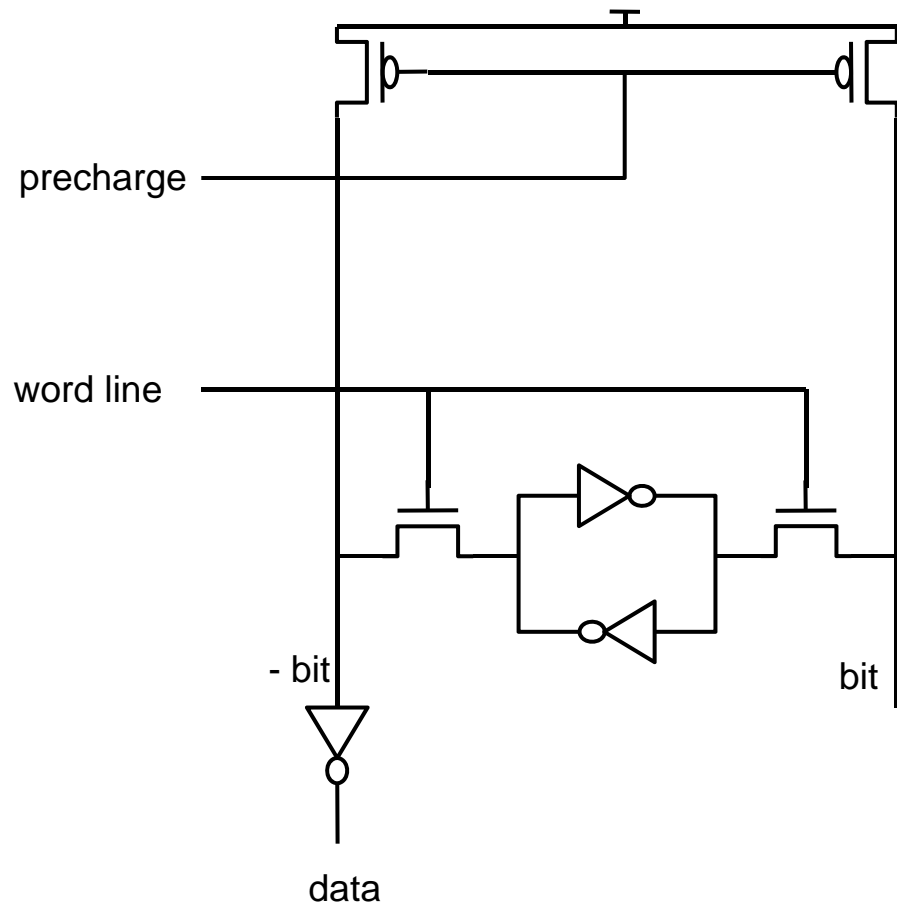

Memory Elements – RAM Write Operation

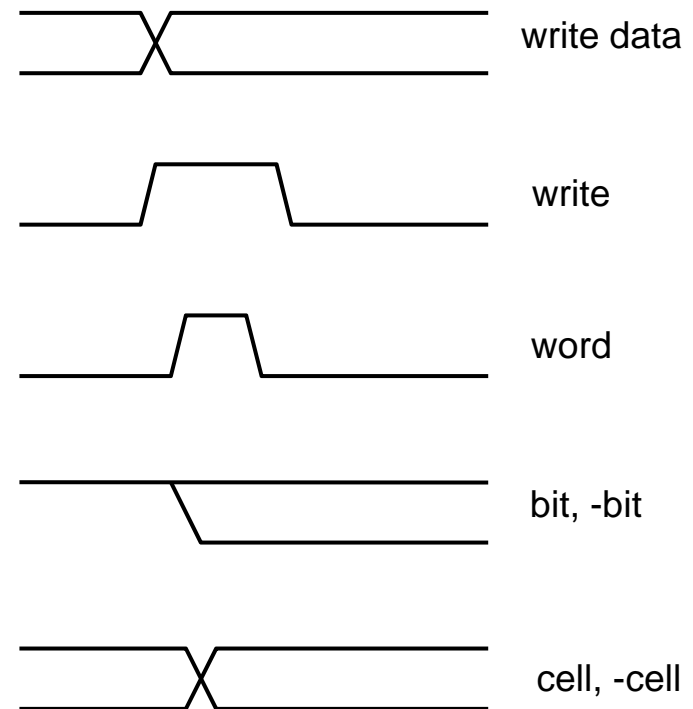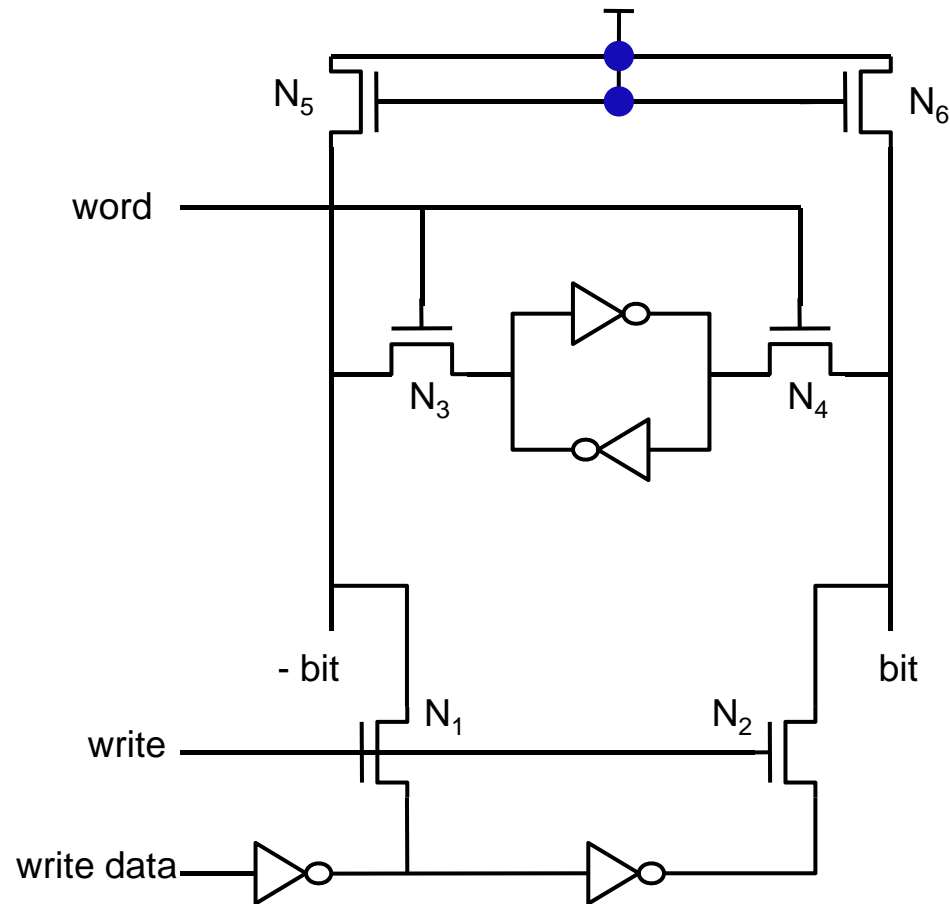


Memory Elements – Row Decoder

 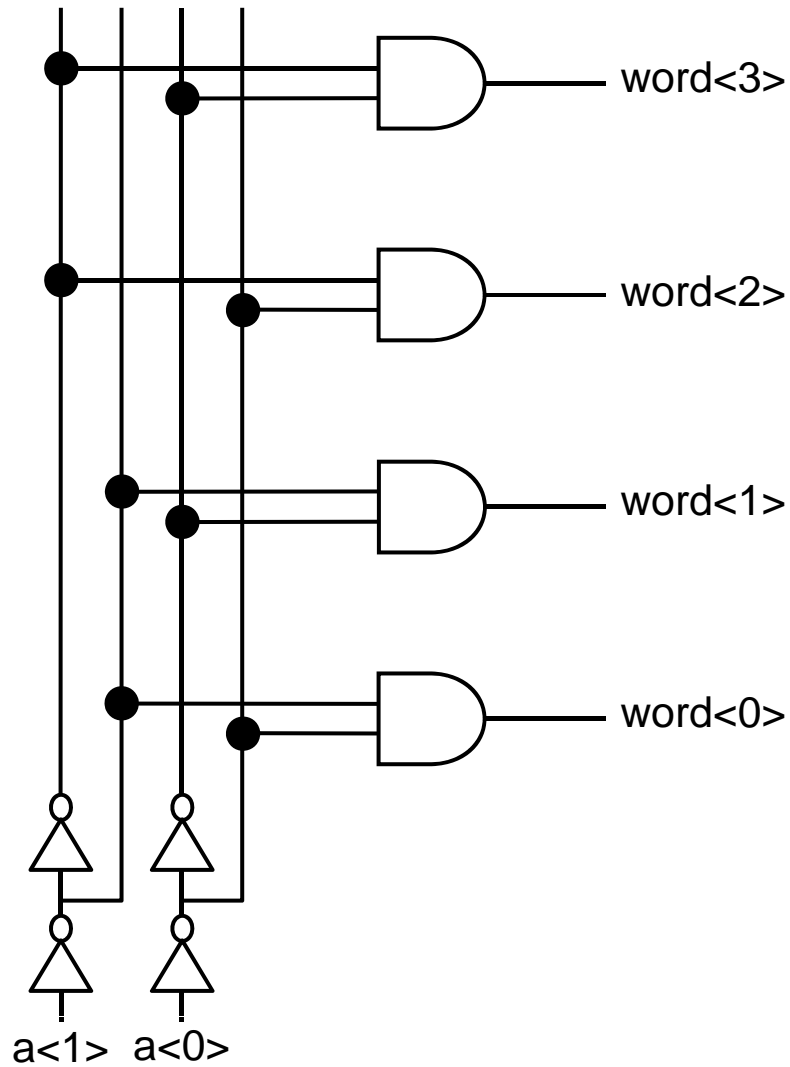


Memory Elements – Row Decoder

Predecode circuit

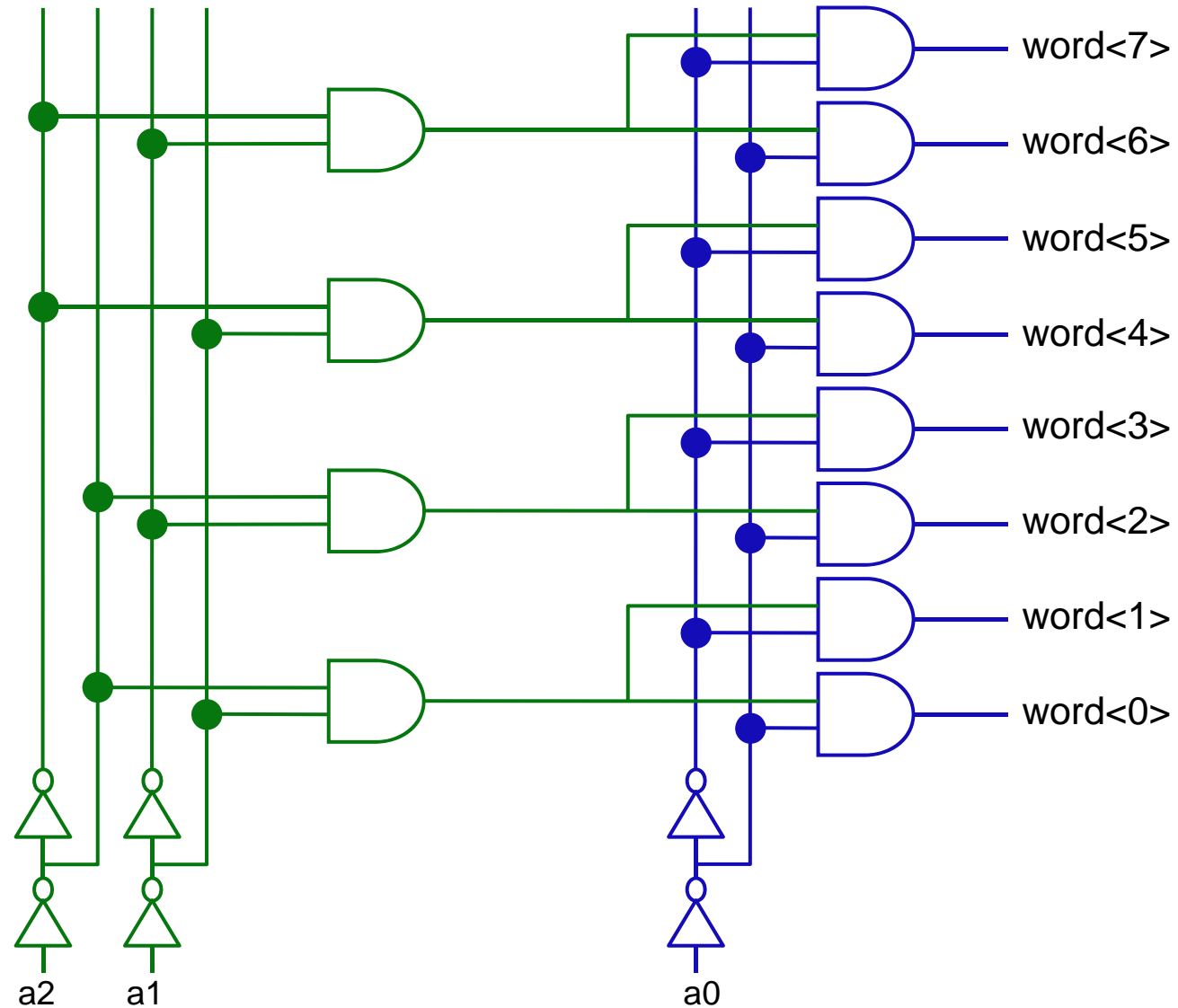


Memory Elements – Row Decoder


Actual implementation

 



Pseudo-nMOS example

 

Memory Elements – Column Decoder

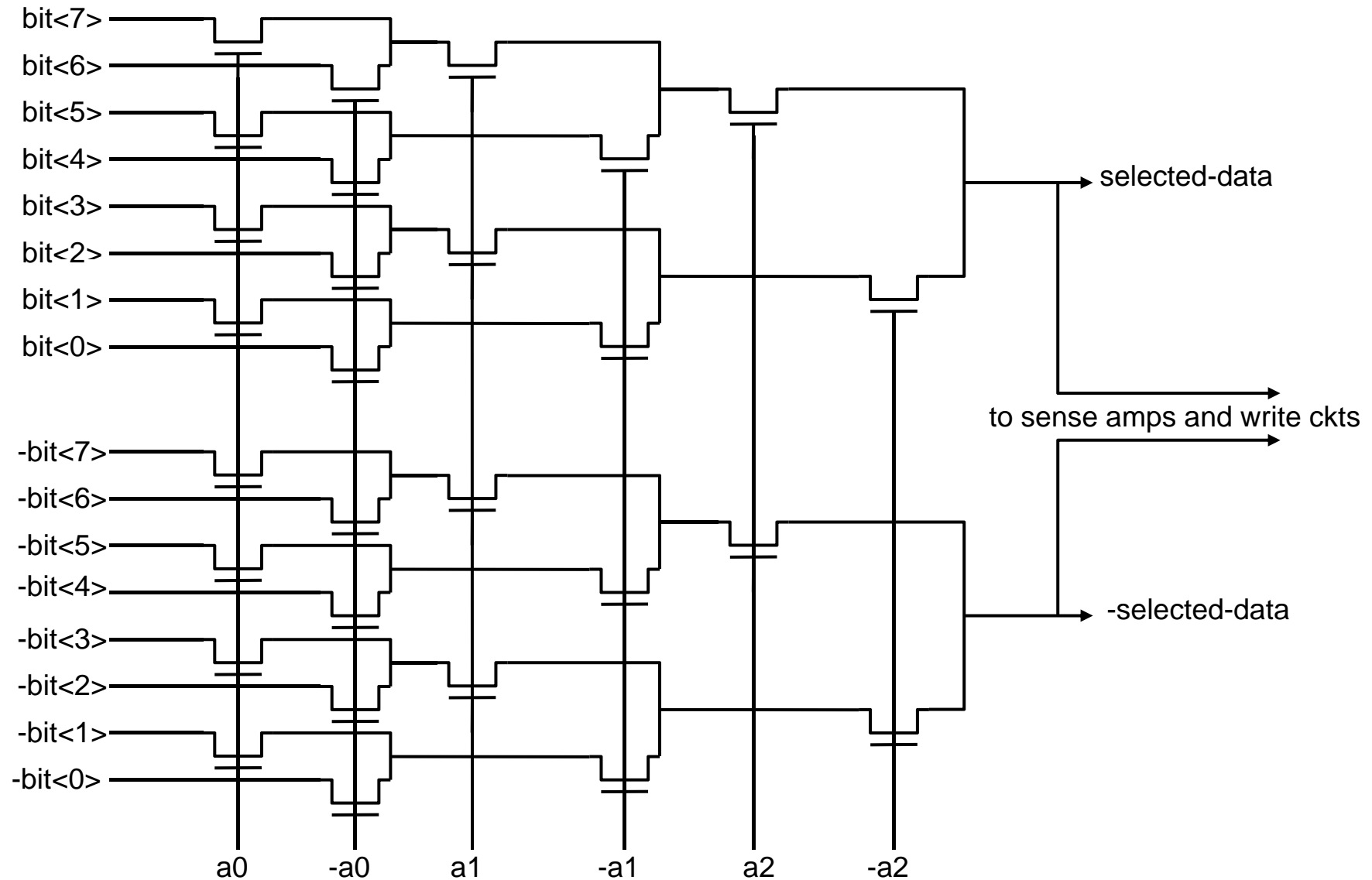


Memory Elements – Multi-Ported RAM

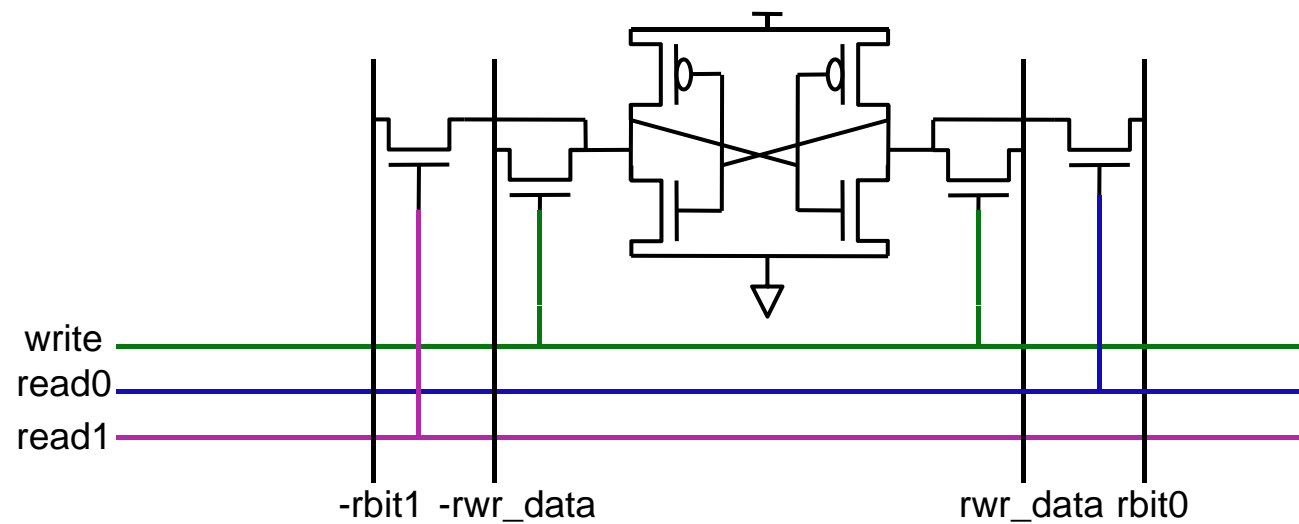 

Memory Elements – ROM


A 4x 4-bit NOR-based ROM array

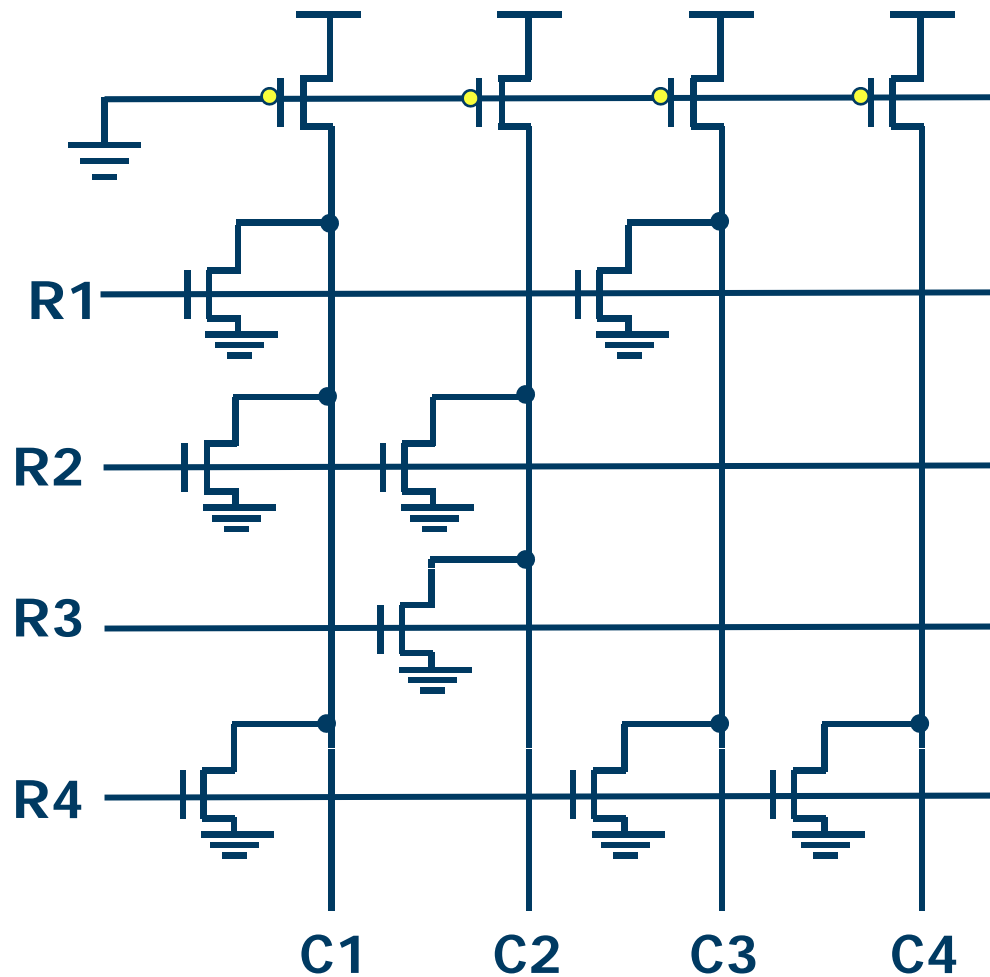

R1	R2	R3	R4	C1	C2	C3	C4
1	0	0	0	0	1	0	1
0	1	0	0	0	0	1	1
0	0	1	0	1	0	0	1
0	0	0	1	0	1	1	0

Memory Elements – ROM

A 4x 4-bit NAND-based ROM array

 

R1	R2	R3	R4	C1	C2	C3	C4
0	1	1	1	0	1	0	1
1	0	1	1	0	0	1	1
1	1	0	1	1	0	0	1
1	1	1	0	0	1	1	0

Memory Elements – ROM

Typical ROM architecture

