

# Chapter 3 Basics of VLSI Testing (2)

---

Jin-Fu Li

Advanced Reliable Systems (ARES) Laboratory  
Department of Electrical Engineering  
National Central University  
Jhongli, Taiwan

# Outline

---

- Testing Process
- Fault Modeling
- Test Pattern Generation
- Fault Simulation
- Design-for-Testability

# Test Process

---

## □ The testing problem

- *Given a set of faults in the circuit under test (or device under test), how do we obtain a certain (small) number of test patterns which guarantees a certain (high) fault coverage?*


## □ Test process

- What faults to test? (***fault modeling***)
- How are test pattern obtained? (***test pattern generation***)
- How is test quality (fault coverage) measured? (***fault simulation***)?
- How are test vectors applied and results evaluated? (***ATE/BIST***)
 
# Defect Categories

---

- Defect categories
  - Random defects, which are independent of designs and processes
  - Systematic defects, which depend on designs and processes used for manufacturing
- For example, random defects might be caused by random particles scattered on a wafer during manufacturing



A resistive open defect [Source: Cadence]

# Logical Fault Models

---

- Systematic defects might be caused by process variations, signal integrity, and design integrity issues.
- It is possible both random and systematic defects could happen on a single die
- With the continuous shrinking of feature sizes, somewhere below the 180nm technology node, system defects have a larger impact on yield than random defects
- Logical faults
  - *Logical faults represent the physical defects on the behaviors of the systems*


# Single Stuck-At Fault

---

- *Single (line) stuck-at fault*
  - The given line has a constant value (0/1) independent of other signal values in the circuit
- Properties
  - Only one line is faulty
  - The faulty line is permanently set to 0 or 1
  - The fault can be at an input or output of a gate
  - Simple logical model is independent of technology details
  - It reduces the complexity of fault-detection algorithms
- One stuck-at fault can model more than one kind of defect


# Single Stuck-At Fault Example

- A circuit with single stuck-at fault

 
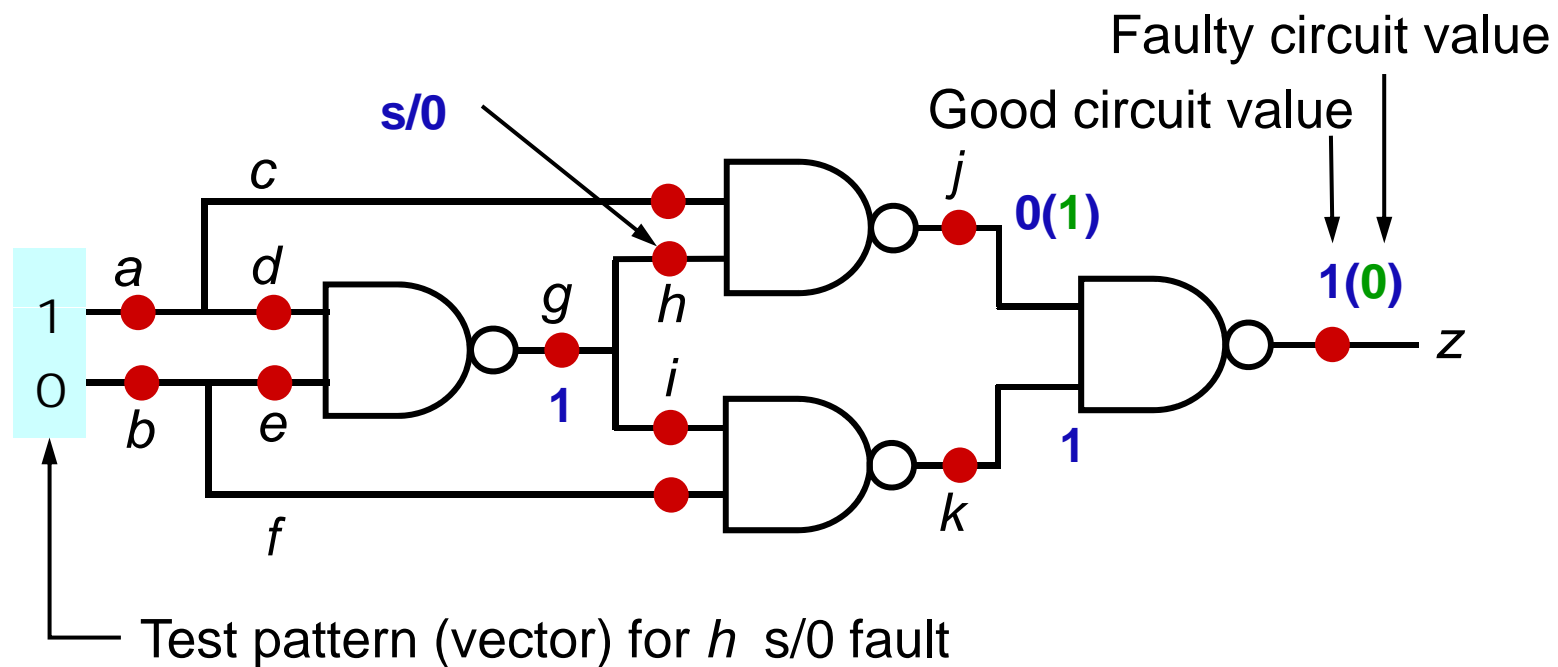
# Number of Single Stuck-At Faults

- Number of fault sites in a Boolean gate circuit
  - $\#PI + \#gates + \#(fanout\ branches)$
- Example: XOR circuit has 12 fault sites (●) and 24 single stuck-at faults





# Test & Test Set

□ A **test** for a fault  $\alpha$  in a circuit  $C$  is an input combination for which the output(s) of  $C$  is different when  $\alpha$  is present than when it is not.


■ A.k.a. test pattern or test vector

■ X detect  $\alpha$  then  $f(X) \oplus f_{\alpha}(X) = 1$

□ A **test set** for a class of faults  $A$  is a set of tests  $T$  such that  $\forall \alpha \in A, \exists t \in T$  and  $t$  detects  $\alpha$

■ The test set for a fault  $\alpha$  is  $T_{\alpha} = f \oplus f_{\alpha}$

■ For example,

 

$$\begin{aligned} T_{\alpha} &= f \oplus f_{\alpha} \\ &= (X_1X_2 + X_3X_4) \oplus X_1X_2 \\ &= \overline{X_1}X_3X_4 + \overline{X_2}X_3X_4 \\ &= \{0011, 0111, 1011\} \end{aligned}$$


# Testing & Diagnosis

---

- **Testing** is a process which includes test pattern generation, test pattern application, and output evaluation.
- **Fault detection** tells whether a circuit is fault-free or not
- **Fault location** provides the location of the detected fault
- **Fault diagnosis** provides the location and the type of the detected fault
  - The input  $X$  distinguishes a fault  $\alpha$  from another fault  $\beta$  iff  $f_{\alpha}(X) \neq f_{\beta}(X)$ , i.e.,  $f_{\alpha}(X) \oplus f_{\beta}(X) = 1$

# Testing & Diagnosis

□ Example:

 


a	b	c	$C_{a/0}$	$C_{a/1}$	$C_{b/0}$	$C_{b/1}$	$C_{c/0}$	$C_{c/1}$
0	0	0	0	1	0	1	0	1
0	1	1	1	1	0	1	0	1
1	0	1	0	1	1	1	0	1
1	1	1	1	1	1	1	0	1


- $C_{a/0}$  and  $C_{c/0}$  are detected by the test pattern (1,0)
- If we apply two test patterns: (1,0) & (0, 1)
  - Two corresponding outputs are faulty  $\rightarrow C_{c/0}$
  - Only the output with respect to the input (1,0) is faulty  $\rightarrow C_{a/0}$

# Functional vs. Structural Test

- Consider a 64-bit adder as shown below

 

**Functional Test**

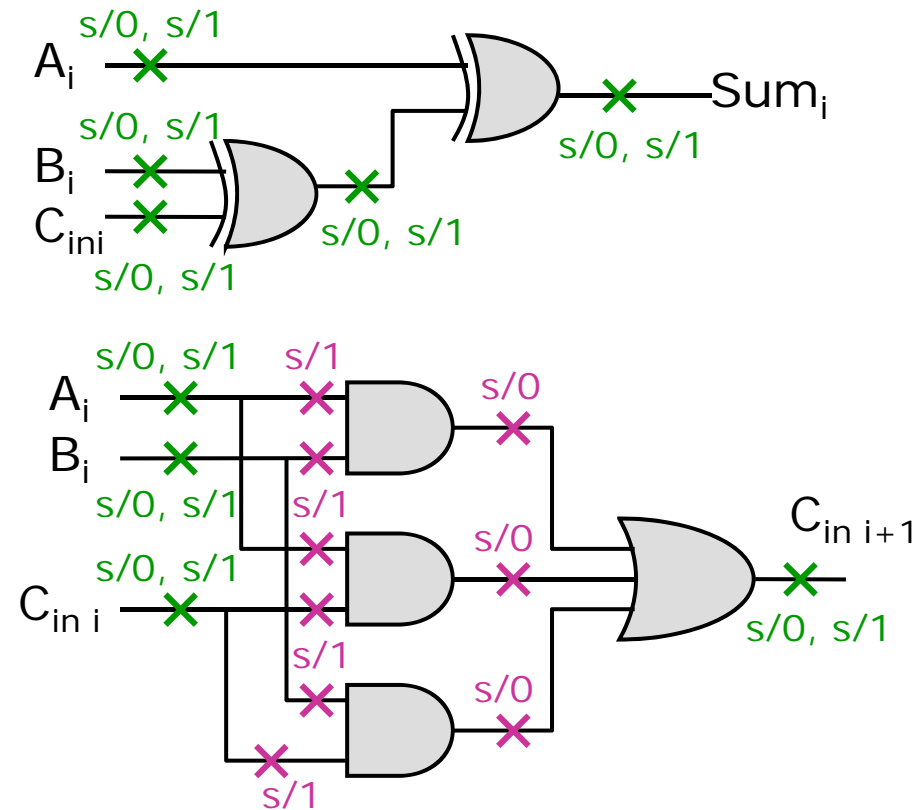

**Structural Test**

# Functional vs. Structural Test

---

## □ Functional test

- Generate complete set of tests for circuit input-output combinations
- 129 inputs & 65 outputs
- $2^{129} = 680,564,733,841,876,926,926,749,214,863,536,422,912$  test patterns are required
- Using 1 GHz ATE, would take  **$2.15 \times 10^{22}$  years**

## □ Structural test

- 64 bit slices and each slice has 27 faults (using fault collapsing)
- At most  $64 \times 27 = 1728$  faults, thus only 1728 test patterns are required
- Takes  **$0.000001728$  seconds** on 1 GHz ATE

# Algorithm Types of Test Pattern Generation

---

- Exhaustive test generation
  - Completely exercise the fault-free behavior
  - Appropriate only when the number of PIs is small
  - Detects all the universal faults (i.e., all combinational faults)
- Pseudoexhaustive test generation
  - Test most of universal faults by applying exhaustive test on subsets of PIs
- Pseudorandom test generation
  - Generate test pattern deterministically
  - Patterns have many characteristics of random patterns but are repeatable

# Algorithm Types of Test Pattern Generation

---

- Algorithmic (deterministic) test generation
  - Algebraic (symbolic) techniques
    - SPOOFs
    - Line condition equations
    - Boolean difference
  - Path-oriented techniques
    - Single-path sensitization
    - D-algorithm
    - PODEM
    - FAN
  - Produces higher-efficiency test patterns, but its cost is more expensive

# Test Pattern Generation Procedure


---

- *Fault activation or excitation*
  - Specify inputs so as to generate the appropriate value at the fault site, i.e., 0 for s/1 and 1 for s/0
- *Fault propagation*
  - Select a path from the fault site to an output and specify other signal values to propagate the fault (error signal) along the path to the output
- *Line justification*
  - Specify input values so as to produce the signal values specified in fault activation and fault propagation, i.e., perform *consistency* check


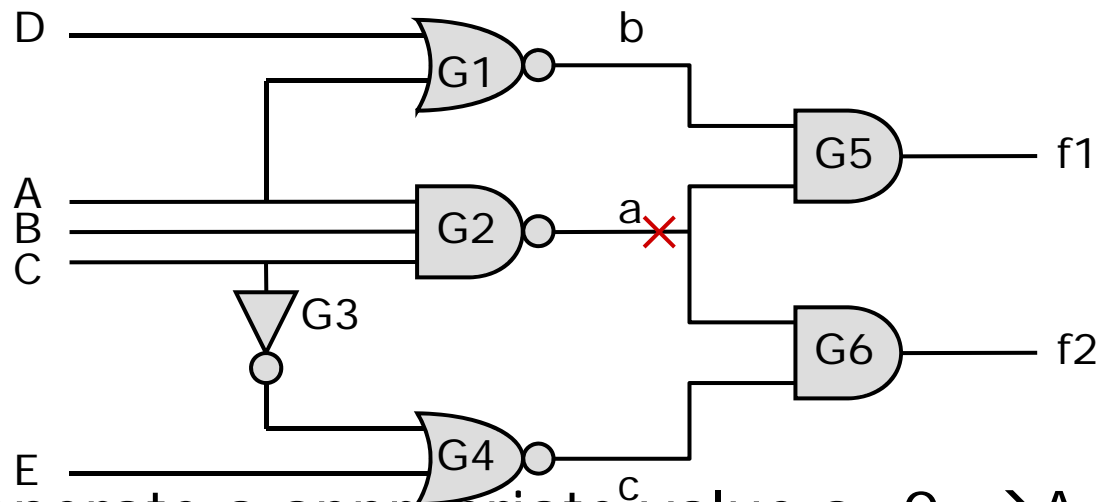
# An Example

- Use single-path sensitization to derive a test set for  $a=0$  in the following circuit



- Generate a appropriate value  $a=0$ .  $\rightarrow A=B=C=1$
- Choose a path via G5  $\rightarrow b=1 \rightarrow A=D=0$ . Contradiction!
- Try another path via G6  $\rightarrow c=1 \rightarrow C=1$  and  $E=0$ . OK!  
Therefore,  $T=ABCE'$

# Fault Simulation

---

## □ Fault simulation

- In general, simulating a circuit in the presence of faults is known as fault simulation

## □ The main goals of fault simulation

- Measuring the effectiveness of the test patterns
- Guiding the test pattern generator program
- Generating fault dictionaries


## □ Outputs of fault simulation

- Fault coverage - fraction (or percentage) of modeled faults detected by test vectors
- Set of undetected faults
 
# Elements of Fault Simulation

---

- The fault simulation process is illustrated as below



- The fault simulator affects the speed of overall fault simulation

# Design for Testability

---

## □ Definition


- A fault is **testable** if there exists a well-specified procedure to expose it, which is implementable with a reasonable cost using current technologies. A circuit is **testable with respect to a fault set** when each and every fault in this set is testable

## □ Definition

- **Design for testability (DFT)** refers to those design techniques that make test generation and test application cost-effective
- Electronic systems contain three types of components: (a) digital logic, (b) memory blocks, and (c) analog or mixed-signal circuits
- Here, we only discuss DFT techniques for digital logic
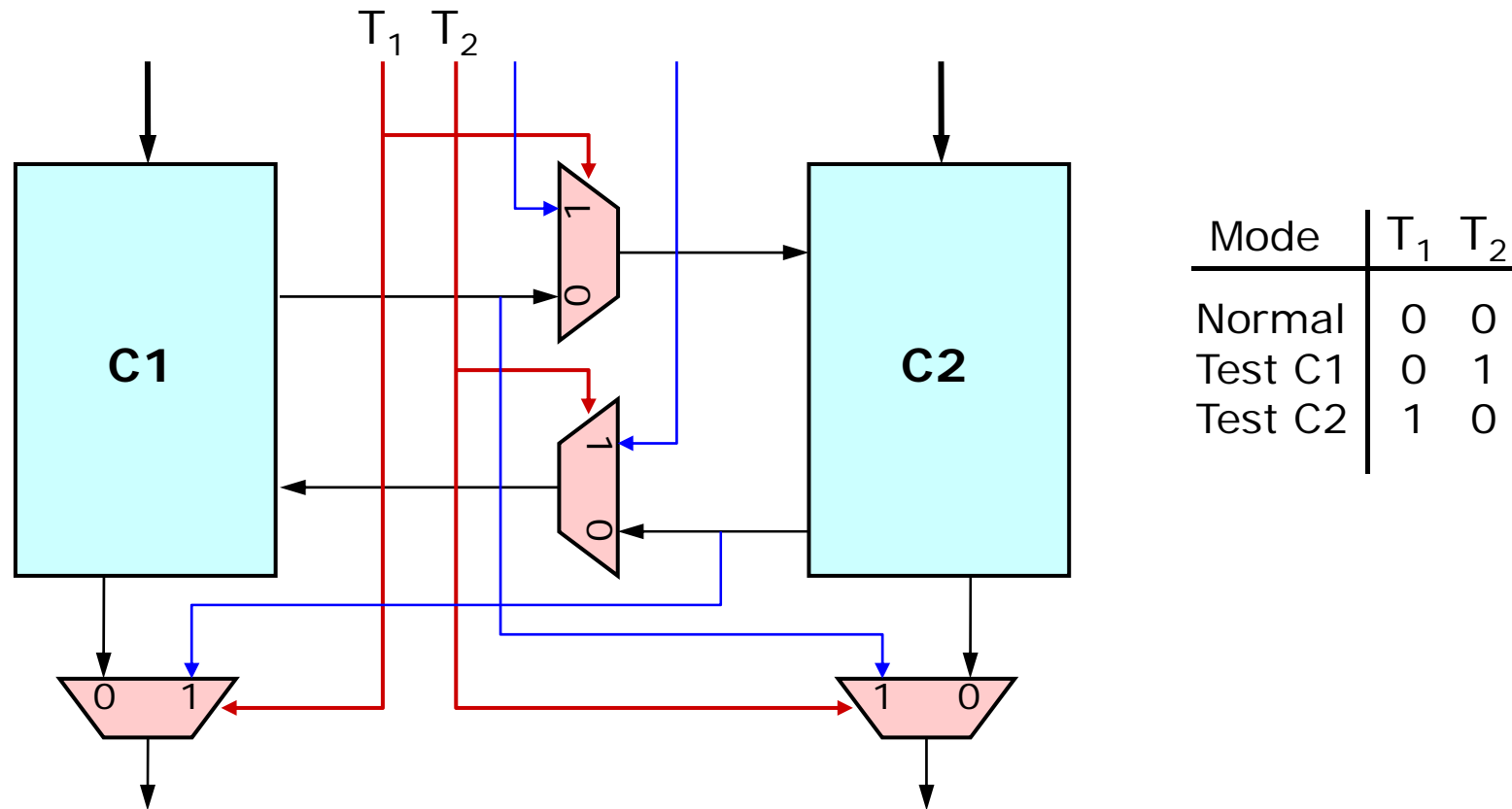
# Ad Hoc DFT Guidelines


- Partition large circuits into smaller subcircuits to reduce test generation cost (using MUXed and/or scan chains)


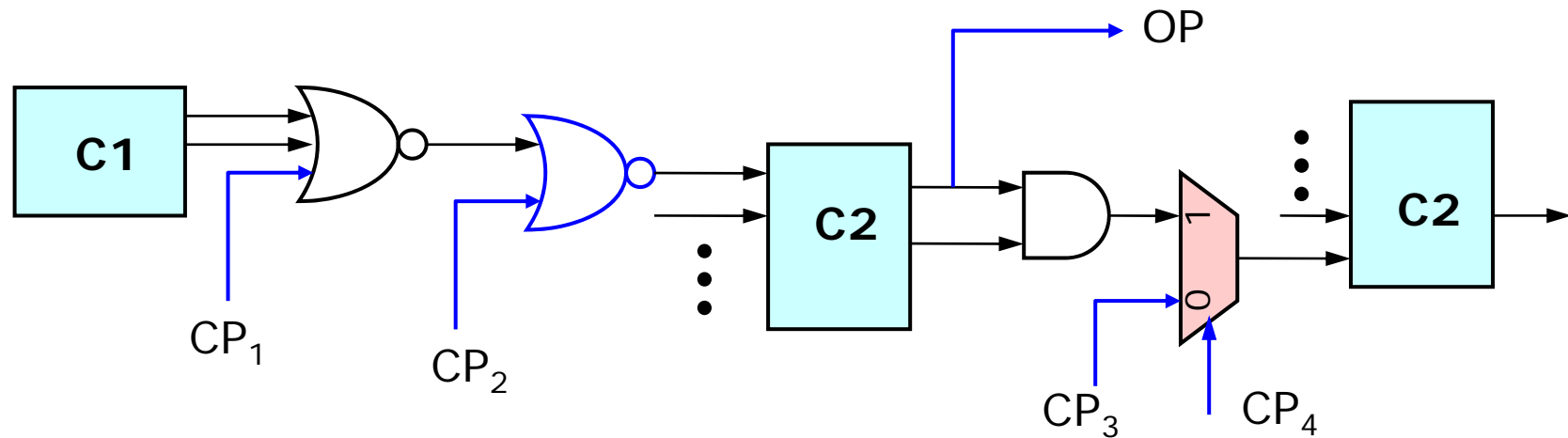
# Ad Hoc DFT Guidelines

---

- Insert test points to enhance controllability & observability
  - Test points: control points & observation points




# Ad Hoc DFT Guidelines

---

- ❑ Design circuits to be easily initializable
- ❑ Provide logic to break global feedback paths
- ❑ Partition large counter into smaller ones
- ❑ Avoid the use of redundant logic
- ❑ Keep analog and digital circuits physically apart
- ❑ Avoid the use of asynchronous logic
- ❑ Consider tester requirements (pin limitation, etc)
- ❑ Etc
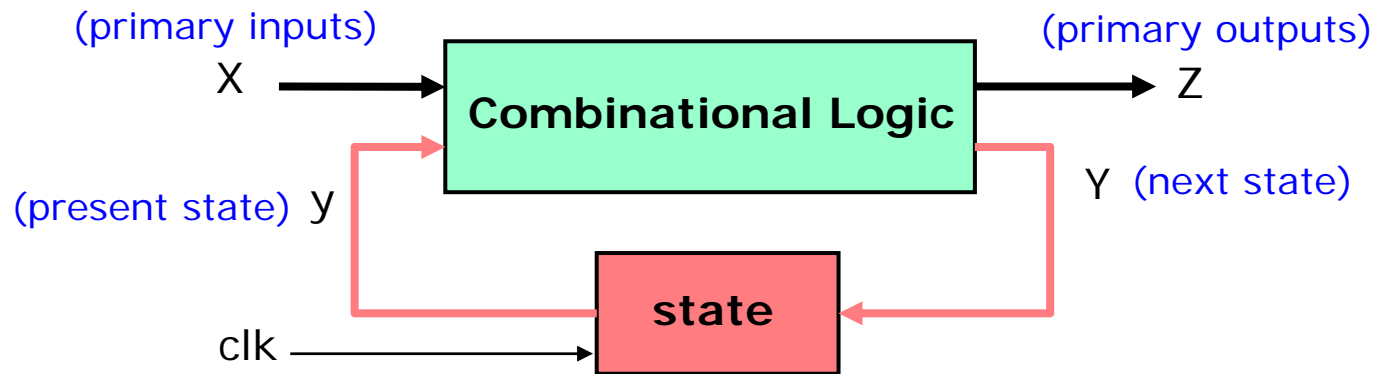
# Scan Design Approaches

- Consider a representation of sequential circuits




- To make elements of state vector controllable and observable, we add
  - A TEST mode pin (T)
  - A SCAN-IN pin (SI)
  - A SCAN-OUT pin (SO)
  - A MUX (switch) in front of each FF (M)



# Adding Scan Structure

---

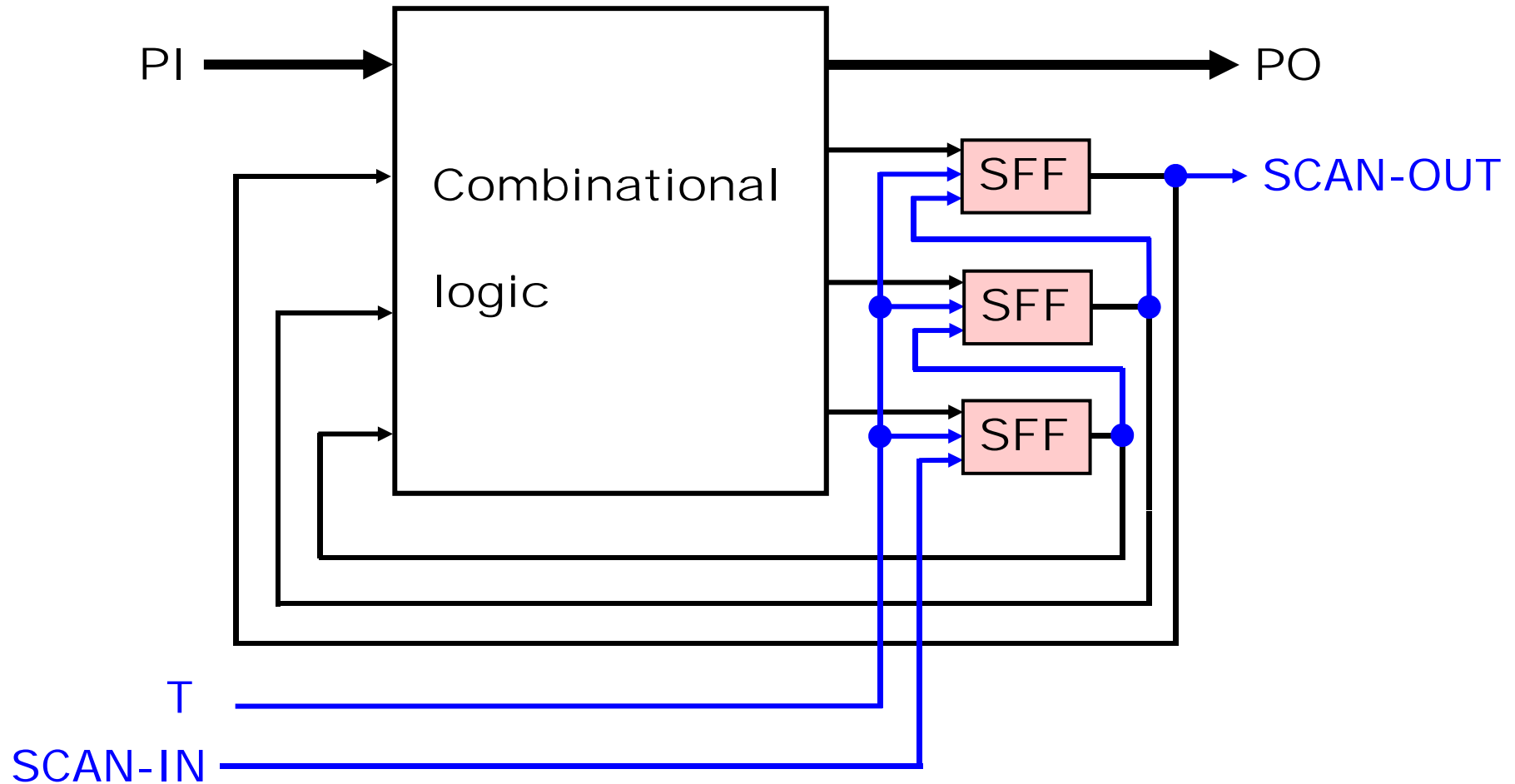

# Scan Test Generation & Design Rules

---


- Test pattern generation
  - Use combinational ATPG to obtain tests for all testable faults in the combinational logic
  - Add shift register tests and convert ATPG tests into scan sequences for use in manufacturing test
- Scan design rules
  - Use only clocked D-type of flip-flops for all state variables
  - At least one PI pin must be available for test; more pins, if available, can be used
  - All clocks must be controlled from PIs
  - Clocks must not feed data inputs of flip-flops

# Scan Test Procedure


---

- ❑ **Step 1:** Switch to the shift-register mode and check the SR operation by shifting in an alternating sequence of 1s and 0s, e.g., 00110 (functional test)
- ❑ **Step 2:** Initialize the SR---load the first pattern
- ❑ **Step 3:** Return to the normal mode and apply the test pattern
- ❑ **Step 4:** Switch to the SR mode and shift out the final state while setting the starting state for the next test. Go to **Step 3**

# Combining Test Vectors

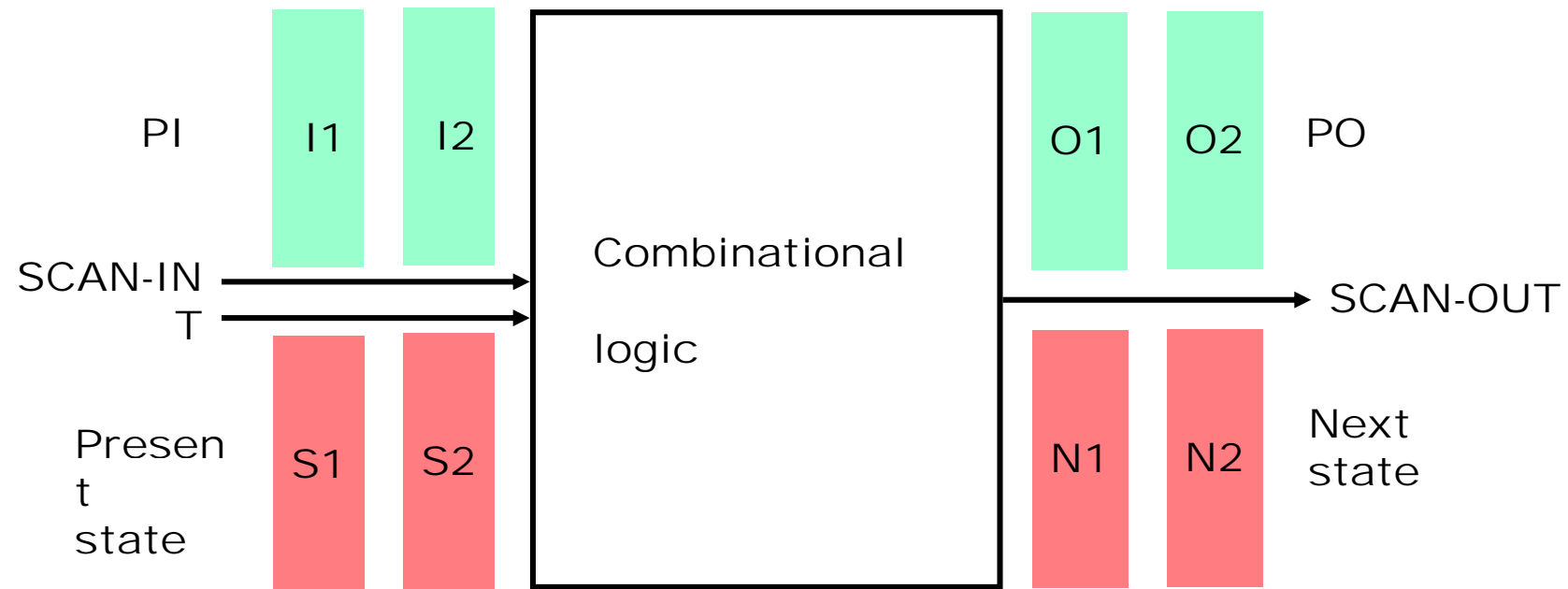

# Combining Test Vectors

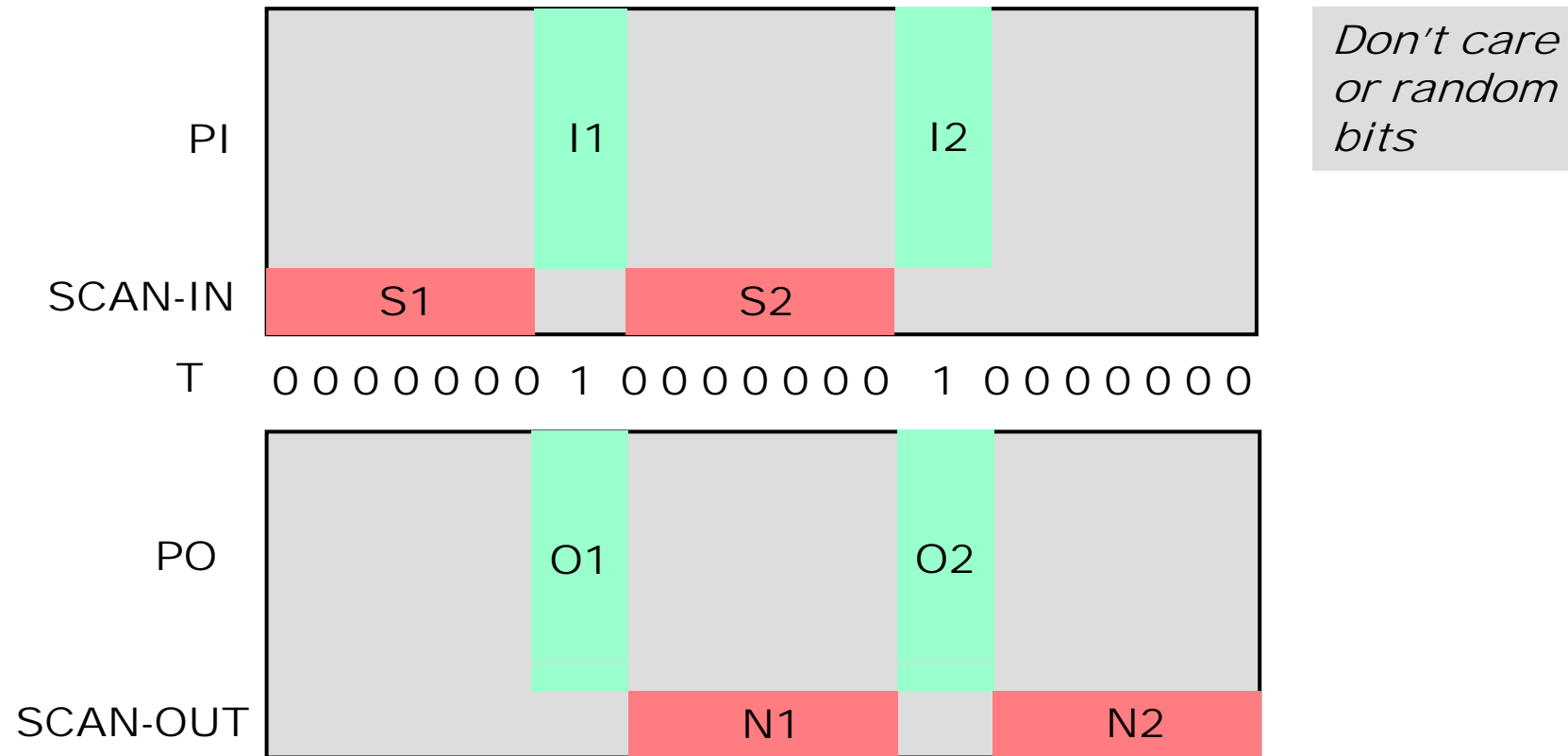

*Sequence length =  $(n_{\text{comb}} + 1) n_{\text{sff}} + n_{\text{comb}}$  clock periods*

$n_{\text{comb}}$  = number of combinational vectors

$n_{\text{sff}}$  = number of scan flip-flops

# Testing Scan Register

---

- Scan register must be tested prior to application of scan test sequences
- A shift sequence 00110011 . . . of length  $n_{\text{sff}} + 4$  in scan mode (TC=0) produces 00, 01, 11 and 10 transitions in all flip-flops and observes the result at SCAN-OUT output
- Total scan test length:  
 $(n_{\text{comb}} + 2)n_{\text{sff}} + n_{\text{comb}} + 4$  *clock periods*
- Example: 2,000 scan flip-flops, 500 comb. vectors, total scan test length  $\sim 10^6$  clocks
- Multiple scan registers reduce test length

# Introduction to Built-In Self-Test

---


- Built-in self-test (BIST):
  - The capability of a circuit (chip/board/system) to test itself
- Advantages of BIST
  - Test patterns generated on-chip → controllability increased
  - (Compressed) response evaluated on-chip → observability increased
  - Test can be on-line (concurrent) or off-line
  - Test can run at circuit speed → more realistic; shorter test time; easier delay testing
  - External test equipment greatly simplified, or even totally eliminated
  - Easily adopting to engineering changes

# Introduction to Built-In Self-Test

---
 
## □ On-line BIST

- Concurrent (EDAC, NMR, totally self-checking checkers, etc.):
  - Coding or modular redundancy techniques (fault tolerance)




- Instantaneous correction of errors caused by temporary or permanent faults
- Nonconcurrent (diagnostic routines):
  - Carried out while a system is in an idle state



# Introduction to Built-In Self-Test

## □ Off-line BIST

- A typical BIST architecture

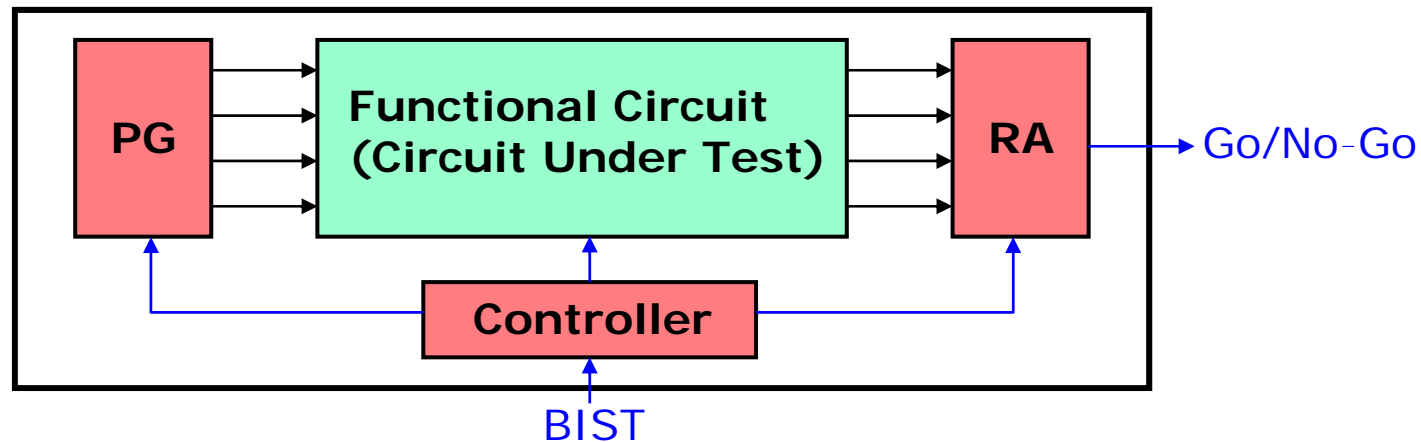

- Test generation

- Prestored TPG, e.g., ROM or shift register
- Exhaustive TPG, e.g., binary counter
- Pseudo-exhaustive TPG, e.g., constant-weight counter, combined LFSR and SR
- Pseudo-random pattern generator, e.g., LFSR


# Introduction to Built-In Self-Test

---

- Response analysis
  - Check-sum
  - Ones counting
  - Transition counting
  - Parity checking
  - Syndrome analysis
  - Etc.
- Linear feedback shift register (LFSR) can be both the test generator and response analyzer
- We need a gold unit to generate the good signature or a simulator


# Structures of LFSR

- Two types of generic standard LFSRs

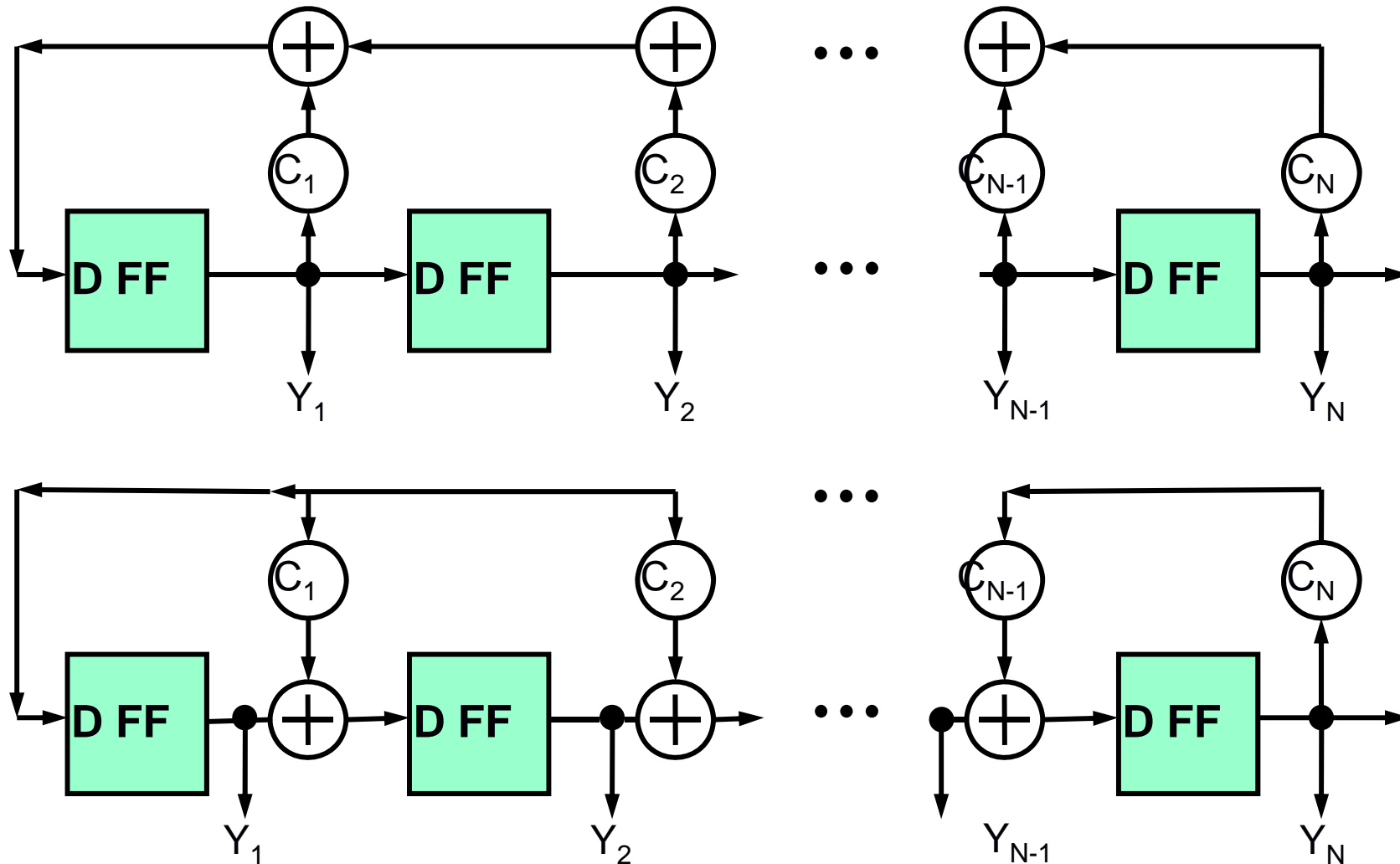

# Pseudorandom Pattern Generator (PRPG)

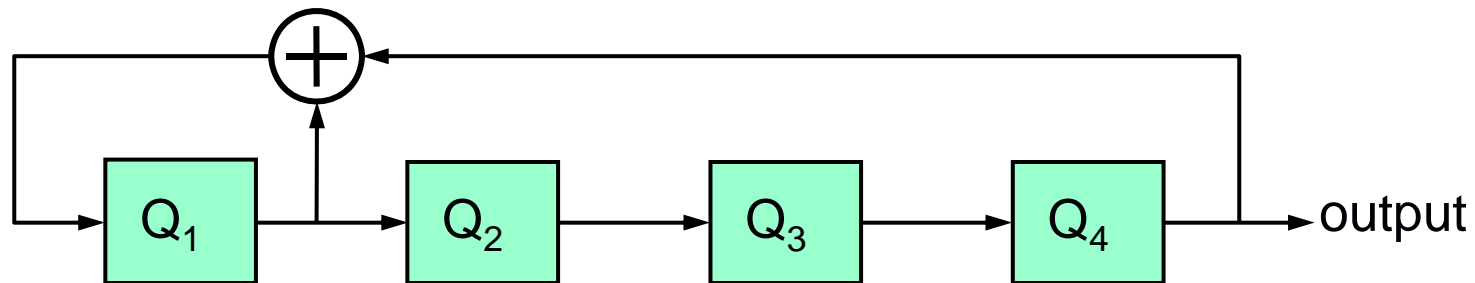- Example: the following ALFSR generates the pseudorandom sequence shown in the table below



State	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15=0
Q <sub>1</sub>	1	1	1	1	0	1	0	1	1	0	0	1	0	0	0	1
Q <sub>2</sub>	0	1	1	1	1	0	1	0	1	1	0	0	1	0	0	0
Q <sub>3</sub>	0	0	1	1	1	1	0	1	0	1	1	0	0	1	0	0
Q <sub>4</sub>	0	0	0	1	1	1	1	0	1	0	1	1	0	0	1	0

- The output sequence is 000111101011001, which repeats after  $15(2^n-1)$  clocks
- Max period for an n-stage ALFSR =  $2^n-1$
- All-0 state of the register cannot occur in the max-length cycle

# STUMPS Architecture

- Logic BIST with STUMPS architecture

