

Chapter 3

VLSI Subsystem Design


Jin-Fu Li

Advanced Reliable Systems (ARES) Laboratory
Department of Electrical Engineering
National Central University
Jhongli, Taiwan

Outline

- ☐ Introduction
- ☐ Datapath Operators
- ☐ Control Structures

System-Level Hierarchy

 

Categories of Components

□ Types of digital component

- Datapath operators
- Memory elements
- Control structures
- I/O cells

□ Tradeoff of selection


- Speed
- Density
- Programmability
- Easy of design
- etc

Datapath – Adder

Adder Truth Table							
C	A	B	A.B(G)	A+B(P)	$A \oplus B$	SUM	CARRY
0	0	0	0	0	0	0	0
0	0	1	0	1	1	1	0
0	1	0	0	1	1	1	0
0	1	1	1	1	0	0	1
1	0	0	0	0	0	1	0
1	0	1	0	1	1	0	1
1	1	0	0	1	1	0	1
1	1	1	1	1	1	1	1

Generate Signal G(A.B): occurs when a carry output (CARRY) is internally generated within the adder .

 Propagate Signal P(A+B): when it is true, the carry in signal C is passed to the carry output (CARRY) when C is true





Datapath – Adder

$$\text{SUM} = A \oplus B \oplus C$$



$$\text{CARRY} = AB + AC + BC$$

Single-bit schematic of SUM

  

Datapath – Adder

Single-bit schematic of CARRY

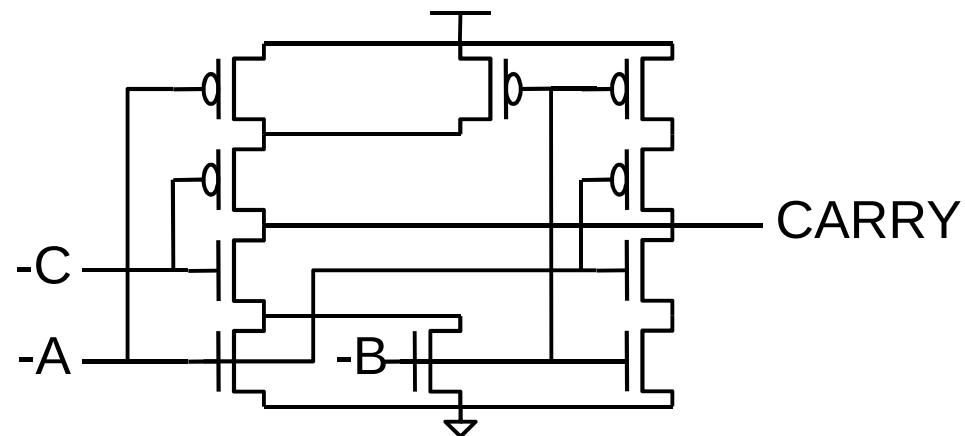 


Datapath – Adder

Optimized combinational adder schematic


$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$
 
$$S_i = (A_i + B_i + C_i) \cdot \overline{C_{i+1}} + A_i B_i C_i$$





Datapath – Adder

 Symmetrical optimized combinational adder schematic




Datapath – Bit-Parallel Adder


Parallel adder implementations

  

Datapath – Bit-Parallel Adder

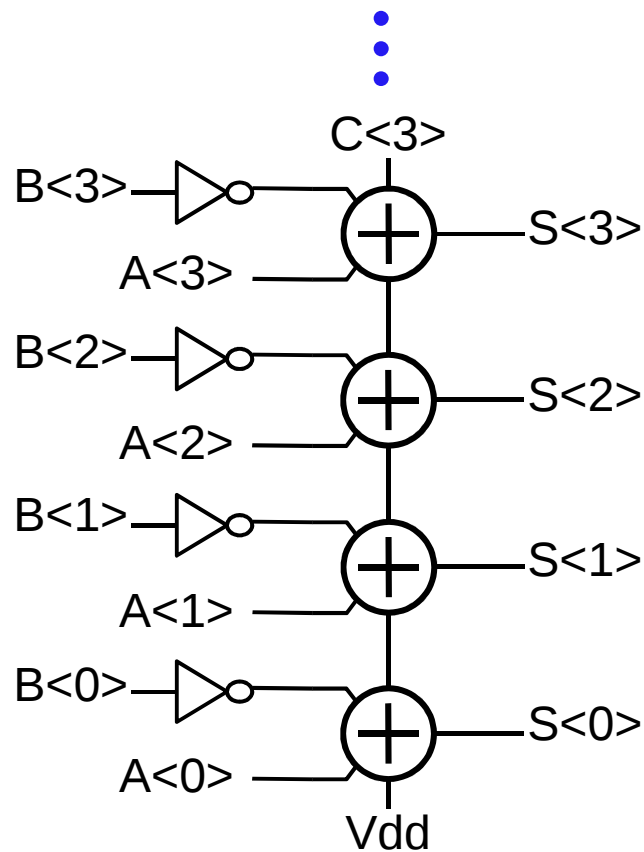


A-B

 

If (Subtract==0)
{S=A+B;}
else
{S=A-B;}

Datapath – *Bit-Serial Adder*

 

Datapath – Carry Look-Ahead Adder (CLA)

□ Objective

- To avoid the linear growth of the carry delay, we use a Carry Look-Ahead Adder (CLA) in which the carries can be generated in parallel

□ Feature

- The Carry of each bit is generated from the propagate and the generate signals as well as the input carry
- The propagate and the generate signals are derived from the operand A_i and B_i by
- $G_i = A_i \cdot B_i$
- $P_i = A_i + B_i$

Datapath – Carry Look-Ahead Adder


$$C_{i+1} = A_i B_i + (A_i + B_i) C_i = G_i + P_i C_i$$

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$



$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$
 
$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$




Datapath – Carry Look-Ahead Adder

CLG1

  

Datapath – Carry Look-Ahead Adder

CLG4

 

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

Datapath – Carry Look-Ahead Adder

Manchester Carry Chain

$$C_{i+1} = G_i + P_i C_i$$


$$G_i = A_i \cdot B_i$$

$$P_i = A_i + B_i$$

Introduce the **carry-kill bit** K_i , this term gets its name from the fact that if $K_i=1$, then $P_i=0$ and $G_i=0$, so that $C_{i+1}=0$; $K_i=1$ thus “kills” the carry-out bit.




$$K_i = \bar{A}_i \cdot \bar{B}_i$$

A_i	B_i	P_i	G_i	K_i
0	0	0	0	1
0	1	1	0	0
1	0	1	0	0
1	1	0	1	0

 

Datapath – Carry Look-Ahead Adder

Manchester circuit styles

   


Datapath – *Carry Look-Ahead Adder*

Extension to wide adders


If we use a brute-force approach for an 8-bit design, then the carry-out bit C_8 would have a term of the form

$$P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0 C_0$$

 Multilevel CLA networks can improve this problem



Datapath – *Carry Look-Ahead Adder*

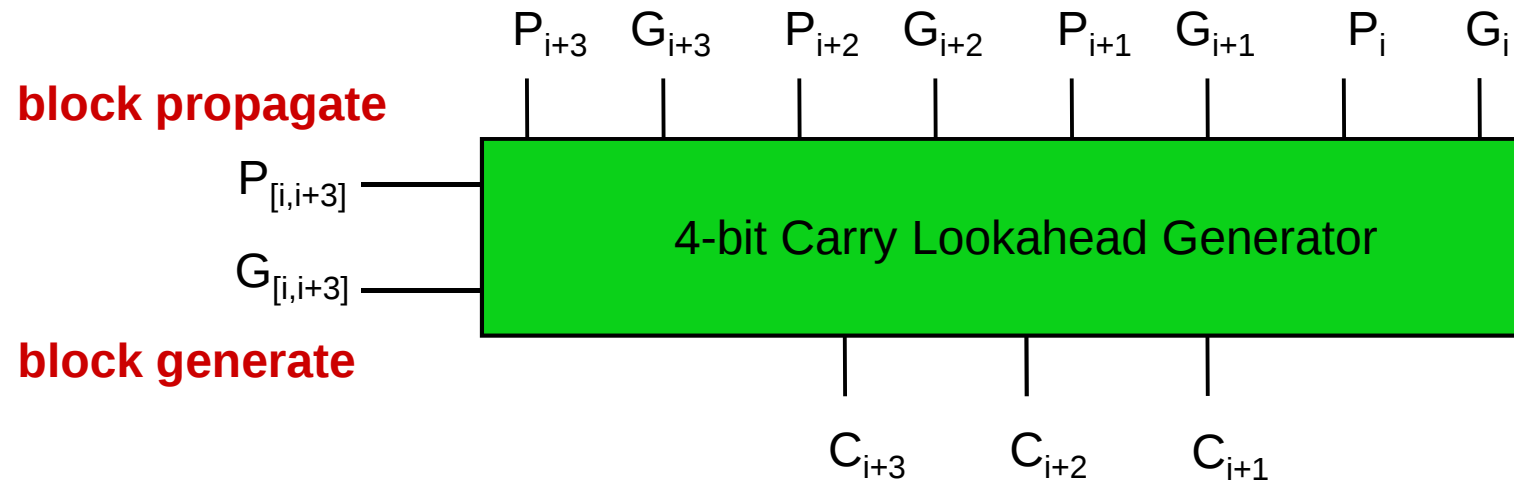


$$G_{[i,i+3]} = G_{i+3} + P_{i+3}G_{i+2} + P_{i+3}P_{i+2}G_{i+1} + P_{i+3}P_{i+2}P_{i+1}G_i$$


$$P_{[i,i+3]} = P_{i+3}P_{i+2}P_{i+1}P_i$$

Datapath – Carry-Skip Adder

 A carry-skip adder is designed to speed up a wide adder by aiding the propagation of a carry bit around a portion of the entire adder.



Carry-skip logic

 


Generalization


$$P_{[i,i+3]} = P_{i+3} P_{i+2} P_{i+1} P_i$$

$$\text{Carry} = C_{i+4} + P_{[i,i+3]} C_i$$


Datapath – Carry-Select Adder

 

Datapath – *Conditional-Sum Adder*

 


Datapath – 8-bit Conditional-Sum Adder

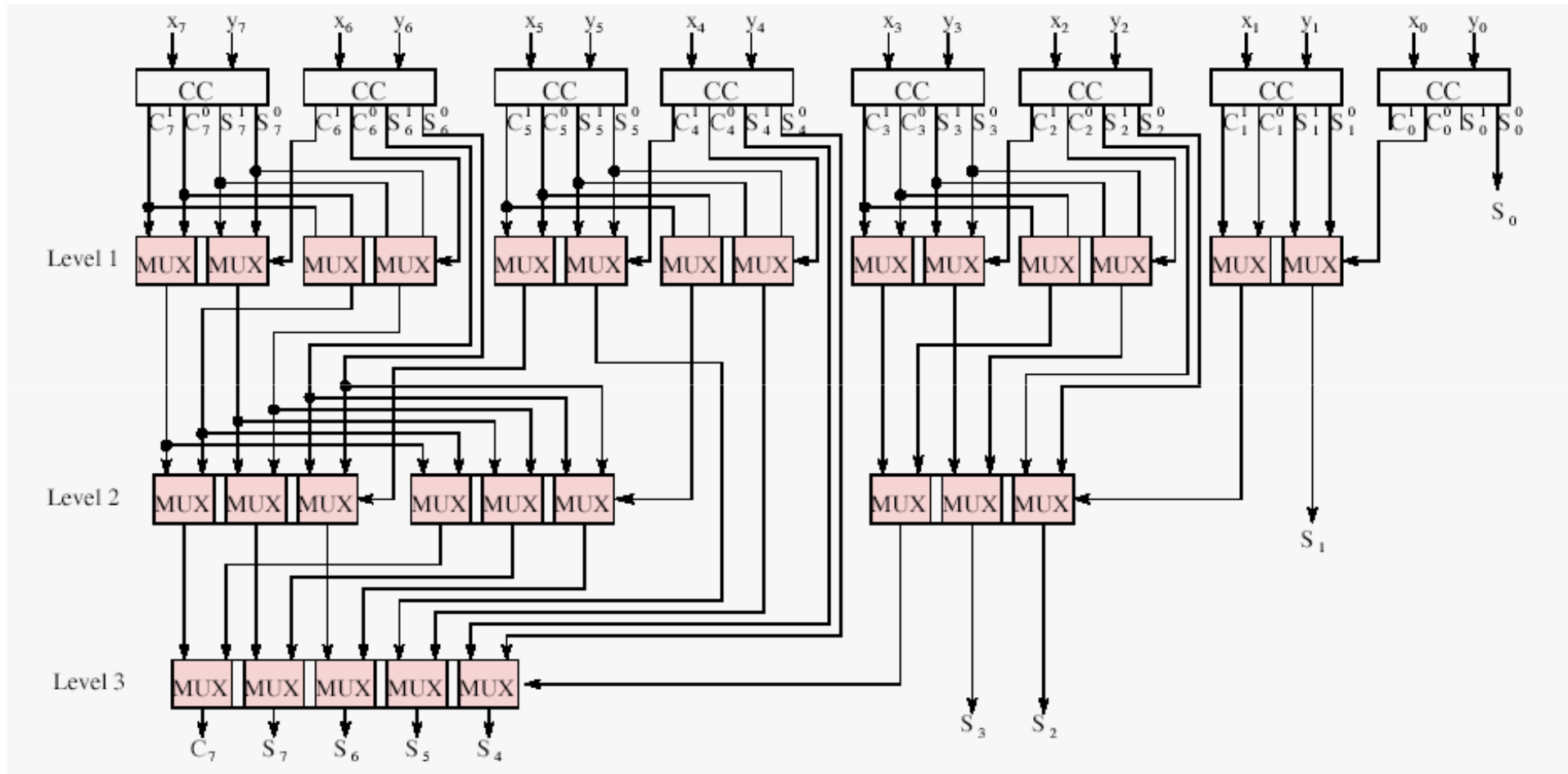


Datapath – *Multipliers*

Bit-level multiplier

a	b	axb
0	0	0
0	1	0
1	0	0
1	1	1

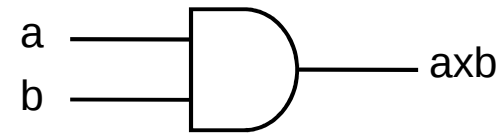

Multiplication of two 4-bit words

 

Datapath – *Multipliers*

The product axb is given by the 8-bit result

$$p = p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0$$

The i th product term p_i can be expressed as


$$p_i = \sum_{j+k=i} a_j b_k + c_{i-1}$$

Alternate view of multiplication process

				a_3	a_2	a_1	a_0	
				b_3	b_2	b_1	b_0	
				$(a_3$	a_2	a_1	$a_0)xb_0$	$(axb_0)2^0$
			$(a_3$	a_2	a_1	$a_0)xb_1$		$(axb_1)2^1$
		$(a_3$	a_2	a_1	$a_0)xb_2$			$(axb_2)2^2$
	$(a_3$	a_2	a_1	$a_0)xb_3$				$(axb_3)2^3$
p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	


Datapath – *Multipliers*

 Using a product register for multiplication




Datapath – Multipliers

Shift-right multiplication sequence

 

Datapath – Register-Based Multiplier

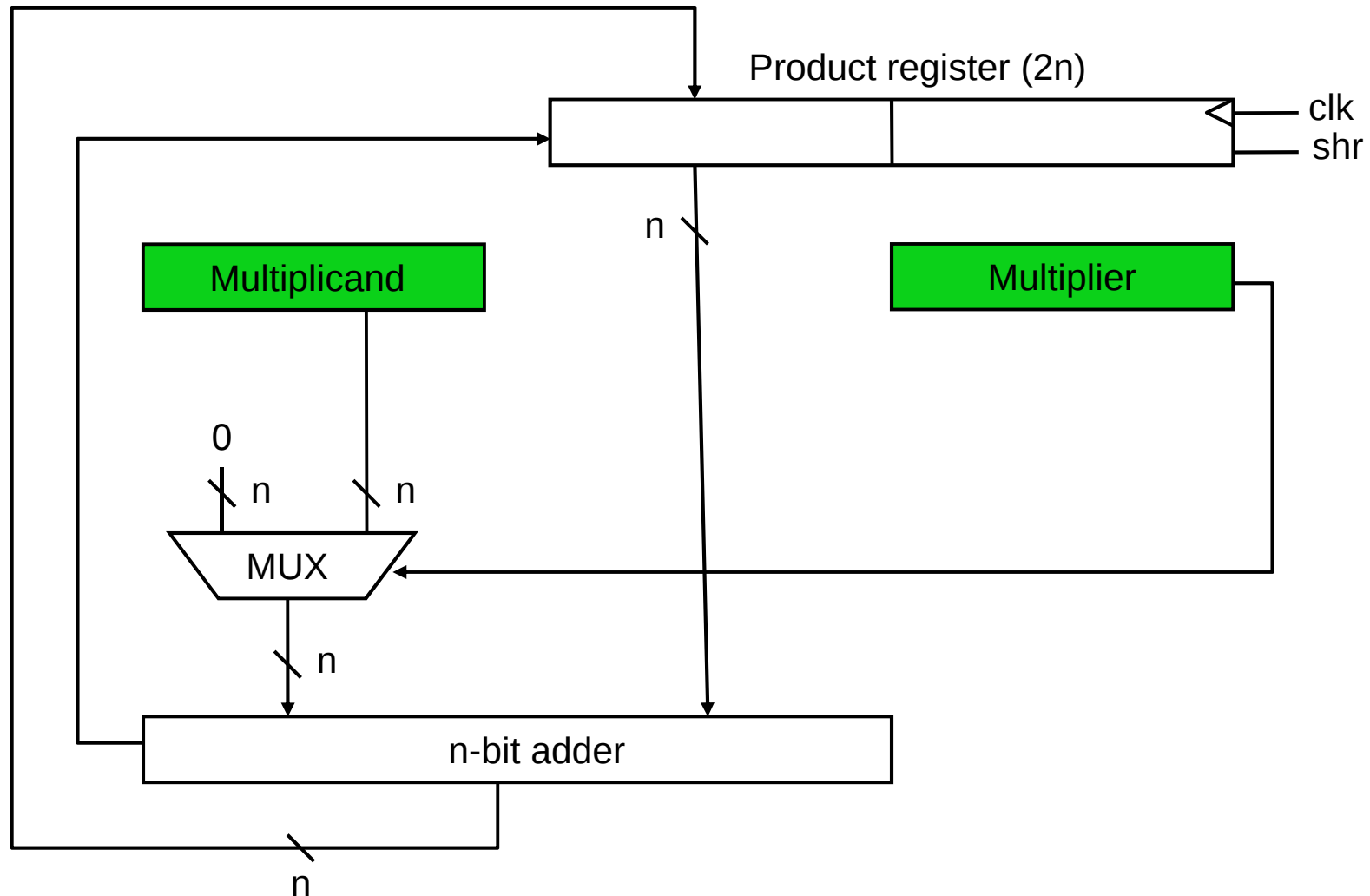


Datapath – *Array Multipliers*

□ Consider two unsigned binary integers X and Y


$$X = \sum_{i=0}^{n-1} X_i 2^i \quad Y = \sum_{j=0}^{n-1} Y_j 2^j$$

$$\begin{aligned} P = X \times Y &= \sum_{i=0}^{n-1} X_i 2^i \cdot \sum_{j=0}^{n-1} Y_j 2^j \\ &= \sum_{i=0}^{n-1} \sum_{j=0}^{n-1} (X_i Y_j) 2^{i+j} \\ &= \sum_{k=0}^{n+n-1} P_k 2^k \end{aligned}$$

Datapath – Array Multipliers

 

Datapath – Array Multipliers

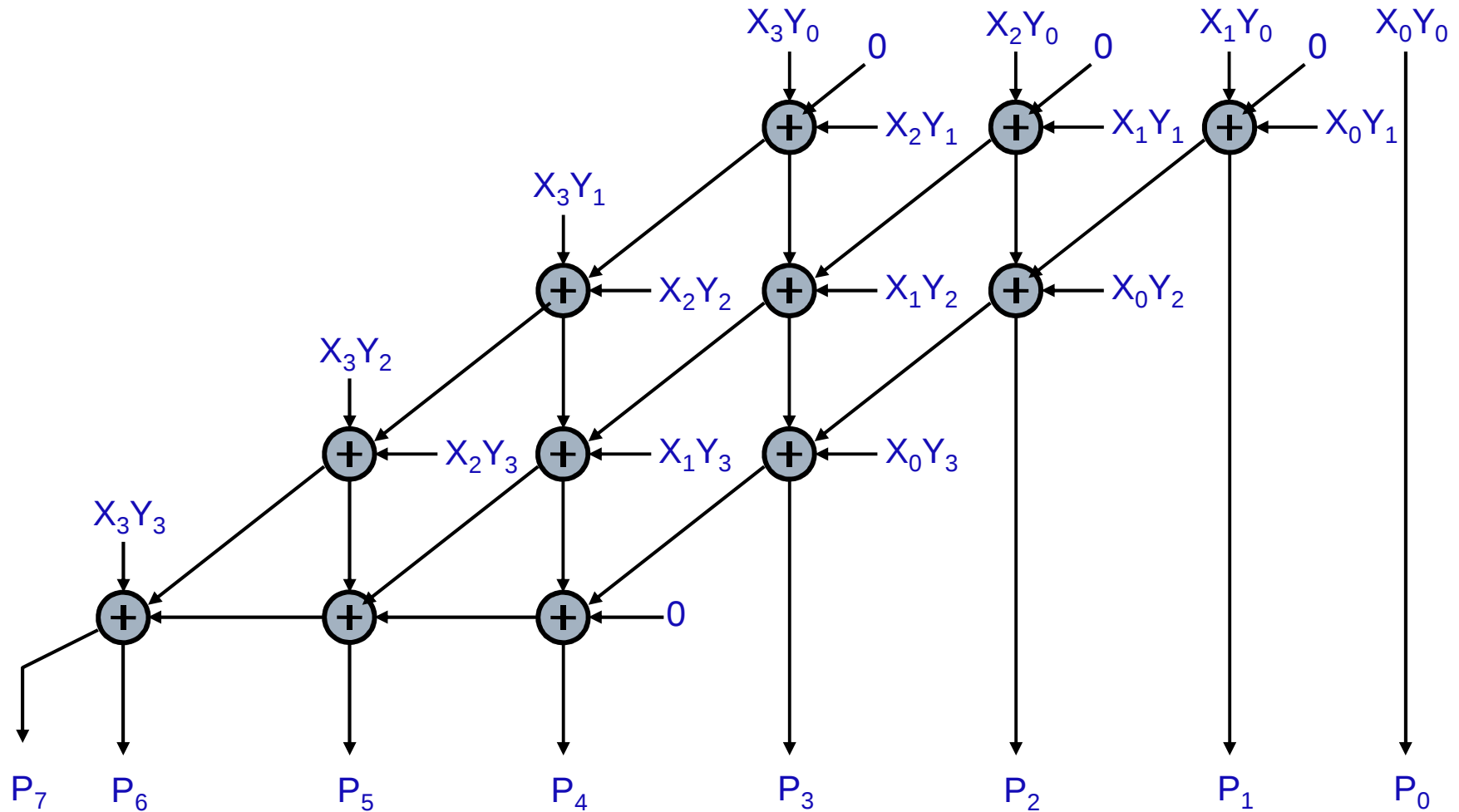

Datapath – Booth Multiplier

- Booth's algorithm takes advantages of the fact that an adder-subtractor is nearly as fast and small as a simple adder
- Consider the two's complement representation of the multiplier y
 - $y = -2^n y_n + 2^{n-1} y_{n-1} + 2^{n-2} y_{n-2} + \dots$
- The representation can be rewritten as
 - $y = 2^n (y_{n-1} - y_n) + 2^{n-1} (y_{n-2} - y_{n-1}) + 2^{n-2} (y_{n-3} - y_{n-2}) + \dots$
- Extract the first two terms
 - $y = 2^n (y_{n-1} - y_n) + 2^{n-1} (y_{n-2} - y_{n-1})$
 - The right-hand term can be used to add x to partial product
 - The left-hand term add $2x$

Datapath – Booth Multiplier

Actions during Booth multiplication


$y_i y_{i-1} y_{i-2}$	Operation
0 0 0	Add 0
0 0 1	Add x
0 1 0	Add x
0 1 1	Add 2x
1 0 0	Sub 2x
1 0 1	Sub x
1 1 0	Sub x
1 1 1	Add 0

For example, $x=011001$ (25_{10}), $y=101110$ (-18_{10})

1. $y_1 y_0 y_{-1}=100$, so $P_1=P_0-2x.1=11111001110$
2. $y_3 y_2 y_1=111$, so $P_2=P_1+0.4=11111001110$
3. $y_5 y_4 y_3=101$, so $P_3=P_2-x.16=11000111110$

Datapath – Booth Multiplier

Structure of a Booth multiplier

 

Datapath – *Wallace Tree Multiplier*

- A Wallace tree is a full adder tree structured specially for a quick addition of the partial products
- Example
 - A 16x16 Booth multiplier
 - 8 partial products are generated
 - Assume that all partial products are negative so all sign extension bits are 1's
 - Sign extension correction vector is 1010101010101011

1111111111111111

1111111111111111

11111111111111

111111111111

11111111

111111

1111

11

1010101010101011

Datapath – *Wallace Tree Multiplier*

Wallace tree multiplication


 


Figure 6

 

Datapath – *Serial Multiplication*


Serial multiplier



1. Require MN clock cycles to produce a product for an N -bit multiplier and a M -bit multiplicand

Datapath – *Serial Multiplication*


Serial/parallel multiplier

 


1. Require $M+N$ clock cycles to produce a product for an N -bit multiplier and a M -bit multiplicand
2. The critical path consists of the adders

Control – *FSM*

Moore

 


Mealy

 

Control – FSM

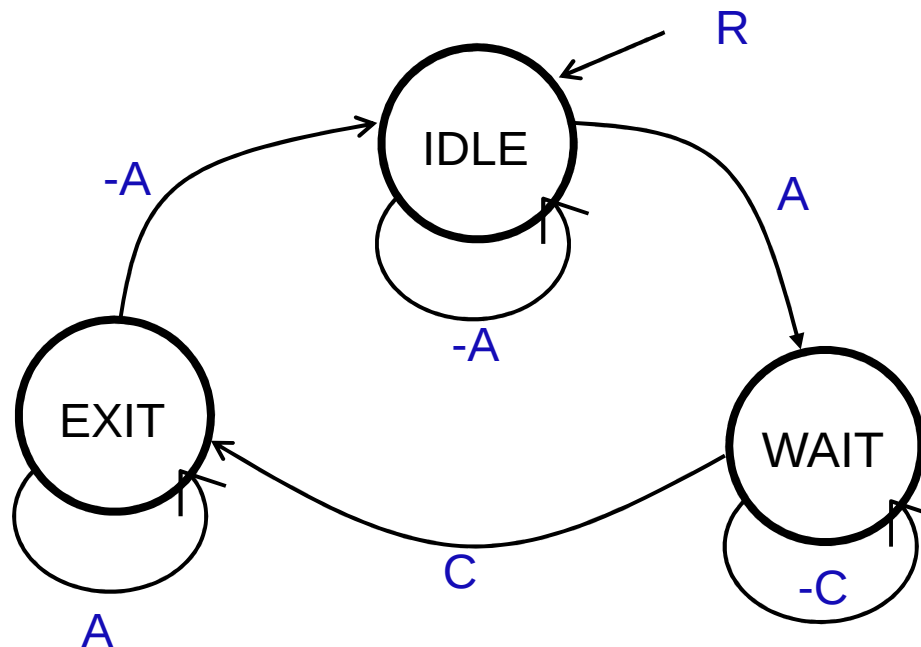- FSM design procedure
 - Draw the state-transition diagram
 - Check the state diagram
 - Write state equations (**Write HDL**)
- An example of state-transition diagram



IDLE: (S1,S0)=(00)

WAIT: (S1,S0)=(01)

EXIT: (S1,S0)=(10)

A: car-in

C: change-ok

R: rst

Control – *FSM*

- Check the state-transition diagram
 - Ensure all states are represented, including the IDLE state
 - Check that the OR of all transitions leaving a state is TRUE. This is a simple method of determining that there is a way out of a state once entered.
 - Verify that the pairwise XOR of all exit transitions is TRUE. This ensures that there are not conflicting conditions that would lead to more than one exit-transition becoming active at any time.
 - Insert loops into any state if it is not guaranteed to otherwise change on each cycle.
- Formal FSM verification method
 - Perform conformance checking


Control – Verilog Coding Style for FSMs

```
module
    toll_booth(clk,rst,car_in,change_ok,green);
input      clk,rst,car_in,change_ok;
output     green;
reg[1:0]   state_reg, next_state;
parameter IDLE = 2'b00;
parameter WAIT = 2'b01;
parameter EXIT = 2'b11;
always @(posedge clk or posedge rst) begin
    if (rst==1'b1) state_reg<=IDLE;
    else state_reg<=next_state;
end
always @(state_reg or car_in or change_ok)
begin
    case(state_reg):
        IDLE: if (car_in==1'b1) begin
            next_state=WAIT;
            green=1'b0;
        end else begin
            next_state>IDEL;
        end
        WAIT: if (change==1'b1) begin
            next_state=EXIT;
            green=1'b1;
        end else begin
            next_state=WAIT;
            green=1'b0;
        end
    end
end
```

```
EXIT: if (car_in==1'b1) begin
    next_state=EXIT;
    green=1'b1;
end else begin
    next_state>IDEL;
    green=1'b0;
end
default: begin
    next_state>IDLE;
    green=1'b0;
end
endcase
end
endmodule
```

Control – PLA

Structure of a PLA

 


A PLA represents an expression of sum-of-product (SOP)

$$f_i = \sum_i m_i(a, b, c, d)$$

$$f_1 = \bar{a} \cdot \bar{b} \cdot c \cdot \bar{d} + \bar{a} \cdot b \cdot c \cdot \bar{d} + a \cdot b \cdot c \cdot d$$

Control – PLA

Fuse-programmable PLA

 

Control – PLA

Logic gate diagram of a PLA

