


Modeling Combinational Circuits with Verilog

Prof. Chien-Nan Liu
TEL: 03-4227151 ext:34534
Email: jimmy@ee.ncu.edu.tw

3-1

Combinational Circuit Design

- Outputs are functions of inputs

 

- Description styles
 - Gate-level
 - Data-flow
 - Behavior
- Some guidelines are given for synthesis

3-2

Sensitivity List

- The sensitivity list must include all inputs of the block
 - All variables in condition statements
 - All variables on the right hand side of procedural assignments
- If not all inputs are listed
 - The changes of inputs may not change outputs immediately
 - May cause functional mismatch in the synthesized circuits
 - The sensitivity list will be skipped during synthesis

Incomplete sensitivity list

```
always@(s1) begin
  if (!s1) q=a;
  else q=b;
end
```

Complete sensitivity list

```
always@(s1 or a or b) begin
  if (!s1) q=a;
  else q=b;
end
```

3-3

Non-Synthesizable Verilog Constructs

Not commonly supported by synthesis tools !!

- initial
- Loops
 - repeat
 - forever
 - while
- Data types
 - event
 - real
 - time
- UDPs
- fork ...join blocks
- procedural assignments
 - assign and deassign
 - force and release
 - disable
- Some operators
 - / and %
 - === and !==

3-4

Inconsistent Results

- The following situations may cause simulation to disagree with synthesis
 - Incomplete sensitivity list
 - Sensitivity list is ignored in synthesis routines
 - Code with delays
 - The specified delay values are also ignored
 - Non-local reference within a function
 - Order dependency of concurrent statements
 - Comparisons to X or Z
- Those cases should be avoided at all

3-5

Non-Local Reference

- Not all inputs are declared in the input list (sensitivity list) of a function


```
function byte_compare;
input [15:0] vector1, vector2;
input [7:0] length;

begin
  if (byte_sel)
    // compare the upper byte
  else
    // compare the lower byte
  end
endmodule
```

non-local variable

3-6

Order Dependency

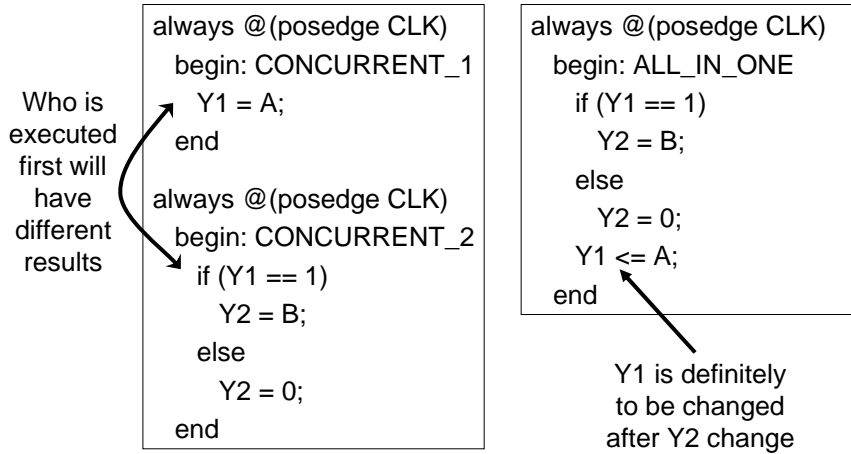

3-7

Comparisons to X or Z

```
always @(A)
begin
  if (A === 1'bx)
    B = 0;
  else
    B = 1;
end
```

Comparisons to a "don't care" are treated as always being false in synthesis routines


3-8

Priority for If Statements

The last "if" has highest priority

```

 always@(a or b or c or d or sel)
begin
  z=0;
  if (sel[0]) z=a;
  if(sel[1]) z=b;
  if(sel[2]) z=c;
  if (sel[3]) z=d;
end
    
```




highest priority

3-9

Late Arriving Data Signal

```

always@(a or b_is_late or c or
d or sel)
begin
  z=0;
  if (sel[0]) z1=a;
  if(sel[2]) z1=c;
  if (sel[3]) z1=d;
  if ( sel[1] & ~sel[2] | sel [3])
    z=b_is_late;
  else
    z=z1;
end
    
```

 

Put the last arriving signal to the last if condition

3-10



Avoid Latch Inference (1/3)

- When if or case statements are used without specifying outputs in all possible condition, a latch will be created

```
always@(enable or data)
  if (enable)
    q =data ;
```

```
always@(enable or data)
begin
  if (enable)
    q =data ;
  else
    q=0;
end
```

Specify all output value

  

3-11

Avoid Latch Inference (2/3)

```
always@(a or b or c)
case(a)
  2'b11 : e = b;
  2'b10 : e = ~c;
end case
```

No latch



```
always@(a or b or c)
case(a)
  2'b11 : e = b;
  2'b10 : e = ~c;
  default : e = 0 ;
end case
```

Add default statement

```
always@(a or b or c)
e =0;
case(a)
  2'b11 : e = b;
  2'b10 : e = ~c;
end case
```

Give initial value



result in a latch

3-12

Avoid Latch Inference (3/3)

Not all possible cases are defined
  
```
always@(a or b or c)
case(a)
  2'b11 : e = b;
  2'b10 : e = ~c;
end case
```




```
always@(a or b or c)
case(a) // synopsys full_case
  2'b11 : e = b;
  2'b10 : e = ~c;
end case
```

- To avoid latch inference and the need for default logic, add case directive :
//synopsys full_case
// ambit synthesis case = full

3-13


If vs. Case (1/2)
 
```
if (A[0] == 0 and A[1] == 0) then
  B = C;
else if (A[0] == 1 and A[1] == 0) then
  B = D;
else if (A[0] == 0 and A[1] == 1) then
  B = E;
else
  B = F;
end if;
```



3-14

If vs. Case (2/2)

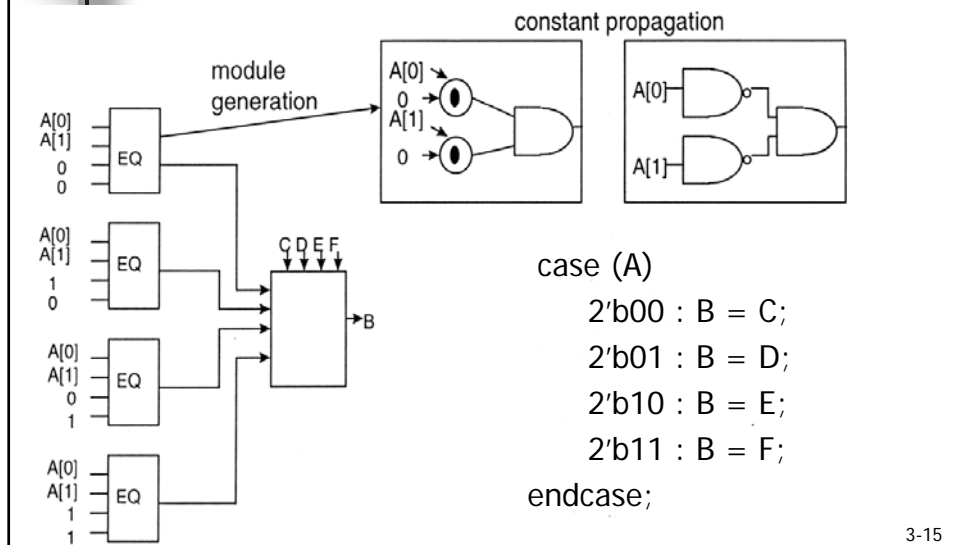

Case Directive

- A non-parallel (overlapped) case statement will generate the logic for a priority encoder
 - The first case item has the highest priority
- If only one case item is executed at a time
 - Force to generate multiplexer logic instead
 - Use // synopsys parallel_case
 - Use //ambit synthesis case = parallel
- The results are unexpected when more than one case items are executed together

3-16

Inferring Multiplexers

- Use directives to force inferring multiplexers

```
//synopsys infer_mux("mux_lab")
always@(SEL or DIN)
begin:mux_lab
case(SEL)
  2'b00:DOUT=DIN[0];
  2'b01:DOUT=DIN[1];
  2'b10:DOUT=DIN[2];
  2'b11:DOUT=DIN[3];
endcase
```

```
always@(SEL or DIN)
begin:mux_lab
case(SEL) //synopsys infer_mux
  2'b00:DOUT=DIN[0];
  2'b01:DOUT=DIN[1];
  2'b10:DOUT=DIN[2];
  2'b11:DOUT=DIN[3];
endcase
```


3-17

Loop Synthesis

- In synthesis, for loops are “unrolled”, and then synthesized

```
integer i;
always@(a or b) begin
  for ( i=0; i<=3; i=i+1)
    out [i]=a[i]&b[3-i];
end
```

unroll

 

```
integer i;
always@(a or b) begin
  out[0]=a[0]&b[3];
  out[1]=a[1]&b[2];
  out[2]=a[2]&b[1];
  out[3]=a[3]&b[0];
end
```

3-18

Non-Static Loops

- Non-static loops are not synthesizable

```

module NonStaticLoop (A, B, R, Y);
  input [7:0] A, B;
  input [2:0] R;
  output [7:0] Y;
  reg [7:0] Y;
  integer i;
  always @(A) begin
    Y = 8'b0;
    for ( i=0; i<R; i=i+1)
      Y[i] = A[i] & B[i];
  end
endmodule
  
```

R is non-static

3-19


Resource Sharing (1/2)

```


always@(a or b or c or d)
  out =(a) ? (b+c):(b+d);
  
```

```

 always@(a or b or c or d)
  if (a) out = b+c;
  else out = b+d ;
  
```



without resource sharing

 

with resource sharing

Keep sharable resource in the

- ✓ same conditional statement
- ✓ same always block
- ✓ same module

3-20

Resource Sharing (2/2)

- The operators that can share resources must be in the mutual exclusive paths

```
if (sel1) out1=a1+b1;
else begin
  out1 = c1+d1 ;
  if ( sel2) out2=a2+b2;
  else out2=c2+d2;
end
```

operator "c1+d1" and
"a2+b2" or "c2+d2" are not
in the mutual exclusive paths

```
if (sel1) out1=a1+b1;
else begin
  out1 = c1+d1 ;
  if ( sel2) out2=a2+b2;
  else out2=c2+d2;
end
```

All operators are in the
mutual exclusive paths

Resource sharing

3-21

Modeling Examples with Verilog for Combinational Circuits

3-22

Code Converter (1/3)

- A code converter transforms one representation of data to another
- Ex: A BCD to excess-3 code converter
 - BCD: Binary Coded Decimal
 - Excess-3 code: the decimal digit plus 3

TABLE 4-2
Truth Table for Code Converter Example

Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

3-23

Code Converter (2/3)



- Equations: (share terms to minimize cost)

$$W = A + BC + BD = A + B(C+D)$$

$$X = \overline{BC} + \overline{BD} + \overline{BCD} = \overline{B}(C+D) + \overline{BCD}$$

$$Y = CD + \overline{CD} = C \oplus D$$

$$Z = D$$

  

3-24

Code Converter (3/3)

- Data-flow style

```
assign W = A|(B&(C|D));
assign X = ~B&(C|D)|(B&~C&~D);
assign Y = ~(C^D);
assign Z = ~D;
```

- Behavior style


```
assign ROM_in = {A, B, C, D};
assign {W, X, Y, Z} = ROM_out;
always @(ROM_in) begin
  case (ROM_in)
    4`b0000: ROM_out = 4`b0011;
    4`b0001: ROM_out = 4`b0100;
    ⋮
    4`b1001: ROM_out = 4`b1100;
    default: ROM_out = 4`b0000;
  endcase
end
```

3-25

Decoder (1/2)

- A decoder is to generate the 2^n (or fewer) minterms of n input variables
- Ex: a 3-to-8 line decoder

Inputs			Outputs							
x	y	z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 

3-26

Decoder (2/2)

■ Behavior style 1

```

input x, y, z;
reg [7:0] D;
always @(x or y or z) begin
  case ({x, y, z})
    3`b000: D = 8`b00000001;
    3`b001: D = 8`b00000010;
    ⋮
    3`b111: D = 8`b10000000;
    default: D = 8`b0;
  endcase
end
end

```

■ Behavior style 2

```

input x, y, z;
wire [2:0] addr;
reg [7:0] D;
assign addr = {x, y, z};

always @(addr) begin
  D = 8`b0;
  D[addr] = 1;
end

```

D is unknown when
addr is unknown

3-27

Encoder (1/2)

- An encoder performs the inverse operation of a decoder
 - Have 2^n (or fewer) input lines and n output lines
 - The output lines generate the binary code of the input positions
- Only one input can be active at any given time
- Ex: a octal-to-binary encoder

Inputs									Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z	
1	0	0	0	0	0	0	0	0	0	0	
0	1	0	0	0	0	0	0	0	0	1	
0	0	1	0	0	0	0	0	0	1	0	
0	0	0	1	0	0	0	0	0	1	1	
0	0	0	0	1	0	0	0	1	0	0	
0	0	0	0	0	1	0	0	1	0	1	
0	0	0	0	0	0	1	0	1	1	0	
0	0	0	0	0	0	0	1	1	1	1	

$$\begin{aligned}
 z &= D_1 + D_3 + D_5 + D_7 \\
 y &= D_2 + D_3 + D_6 + D_7 \\
 x &= D_4 + D_5 + D_6 + D_7
 \end{aligned}$$

3-28

Encoder (2/2)

- Data-flow style

```
assign z = D[1] | D[3] | D[5] | D[7];
assign y = D[2] | D[3] | D[6] | D[7];
assign x = D[4] | D[5] | D[6] | D[7];
```

- Behavior style

```
always @(D) begin
  case (D)
    8`b00000001:
      {x, y, z} = 3`b000;
    8`b00000010:
      {x, y, z} = 3`b001;
      ⋮
    8`b10000000:
      {x, y, z} = 3`b111;
    default: {x, y, z} = 3`b000;
  endcase
end
```


3-29

Priority Encoder (1/2)

- An encoder circuit that includes the priority function
- If two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence

V = 0 : no valid inputs

Inputs				Outputs		
D ₀	D ₁	D ₂	D ₃	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

 

$$\begin{aligned}
 x &= D_2 + D_3 \\
 y &= D_3 + D_1 D_2' \\
 V &= D_0 + D_1 + D_2 + D_3
 \end{aligned}$$

3-30

Priority Encoder (2/2)

- Data-flow style

```
assign x = D[2] | D[3];
assign y = D[3] | (~D[2] & D[1]);
assign V = D[0] | D[1] | D[2] | D[3];
```


- Behavior style

```
always @(D) begin
    V = 1;
    case (D)
        4`b1???: {x, y} = 2`b11;
        4`b01??: {x, y} = 2`b10;
        4`b001?: {x, y} = 2`b01;
        4`b0001: {x, y} = 2`b00;
        default: begin
            {x, y} = 2`bx;
            V = 0;
        end
    endcase
end
```

3-31

Multiplexer (1/2)

 - A multiplexer uses n selection bits to choose binary info. from a maximum of 2^n unique input lines
- Like a decoder, it decodes all minterms internally
- Unlike a decoder, it has only one output line



s_1	s_0	Y
0	0	i_0
0	1	i_1
1	0	i_2
1	1	i_3

(b) Function table

3-32

Multiplexer (2/2)

- Behavior style 1

```

input [1:0] S;
input [3:0] I;
output Y;
always @(S or I) begin
  case (S)
    2`b00: Y = I[0];
    2`b01: Y = I[1];
    2`b10: Y = I[2];
    2`b11: Y = I[3];
    default: Y = 0;
  endcase
end

```

- Behavior style 2

```

input [1:0] S;
input [3:0] I;
output Y;
always @(S or I) begin
  Y = I[S];
end


```

suitable for the cases
that inputs are not coded
(ex: A, B, C, ...)

3-33

Demultiplexer (1/2)

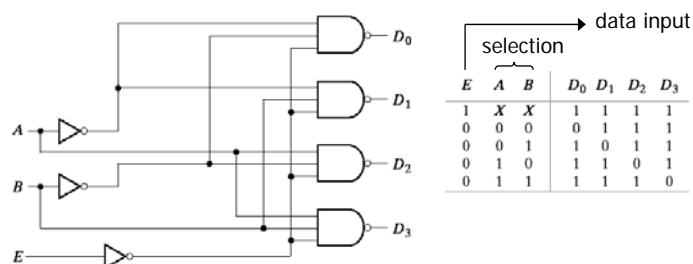- It performs the inverse function of a multiplexer
- It receives info from a single line and transmits it to one of 2^n possible output lines
- A decoder with enable input can function as a demultiplexer
 - Often referred to as a *decoder/demultiplexer*



3-34

Demultiplexer (2/2)

■ Behavior style 1

```

input A, B, E;
reg [3:0] D;
always @(A or B or E) begin
    D = 4`b1111;
    case ({A, B})
        2`b00: D[0] = E;
        2`b01: D[1] = E;
        2`b10: D[2] = E;
        2`b11: D[3] = E;
        default: D = 4`b0;
    endcase
end
    
```

■ Behavior style 2

```

input A, B, E;
wire [1:0] S;
reg [3:0] D;
assign S = {A, B};
always @(S or E) begin
    D = 4`b1;
    D[S] = E;
end
    
```

3-35

Binary Adder Cell (1/2)

□ TABLE 3-7
Truth Table of Half Adder

Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Table 3-7 Truth Table of Half Adder

 


Fig. 3-25 Logic Diagram of Half Adder

□ TABLE 3-8
Truth Table of Full Adder

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Table 3-8 Truth Table of Full Adder

 


Fig. 3-27 Logic Diagram of Full Adder

3-36

Binary Adder Cell (2/2)

- Half adder

```
assign {C, S} = X + Y;
```

```
assign C = X & Y;
```

```
assign S = X ^ Y;
```

preferred writing style
that can tell synthesizer
the existence of an adder

- Full adder


```
assign {C, S} = X+Y+Z;
```

```
assign C = (X&Y) | Z&(X^Y);
```

```
assign S = X ^ Y ^ Z;
```

3-37

Ripple Carry Adder

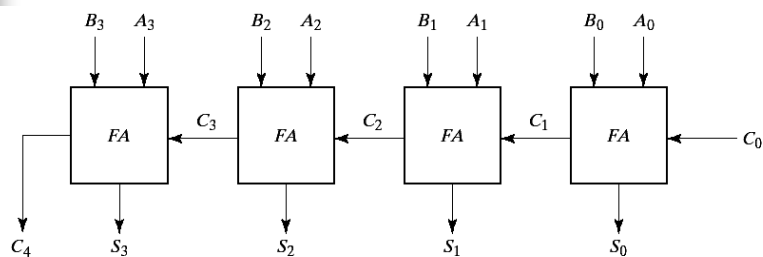

```
module FA4 (S, C4, A, B, C0);
```

```
input [3:0] A, B;
```

```
input C0;
```

```
output [3:0] S;
```

```
output C4;
```

```
FA1 U0(S[0], C1, A[0], B[0], C0);
```

```
FA1 U1(S[1], C2, A[1], B[1], C1);
```

```
FA1 U2(S[2], C3, A[2], B[2], C2);
```

```
FA1 U3(S[3], C4, A[3], B[3], C3);
```

```
endmodule
```


3-38

Carry Propagation

- The **carry propagation time** is a limiting factor on the speed with which two numbers are added
- All other arithmetic operations are implemented by successive additions
 - The time consumed during the addition is very critical
- To reduce the carry propagation delay
 - Employ faster gates with reduced delays
 - Increase the equipment complexity
- Several techniques for reducing the carry propagation time in a parallel adder
 - The most widely used technique employs the principle of **carry lookahead**

3-39

Carry Lookahead Adder

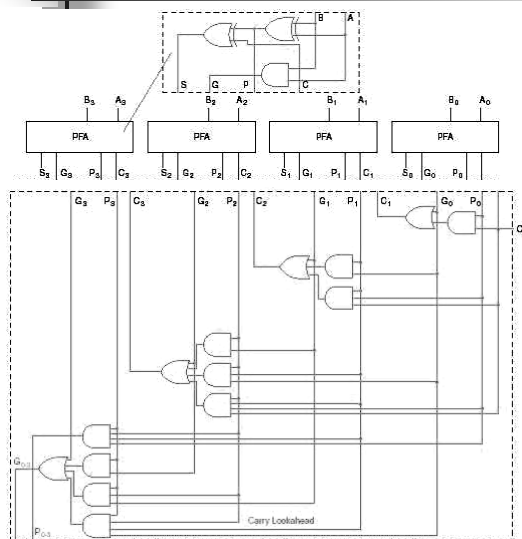


- The critical path “carry” is calculated separately to reduce delay
- $G_n = A_n B_n$
 $P_n = A_n \wedge B_n$
 $S_n = P_n \wedge C_n$
 $C_n = G_{n-1} + P_{n-1} C_{n-1}$
- $C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$
- Gate-level descriptions are often used

3-40


Hierarchical CLA

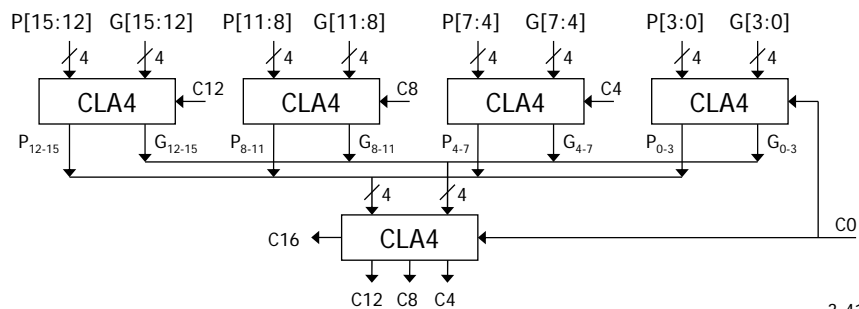- $C_n = G_{n-1} + P_{n-1}C_{n-1}$
- $C_4 = (G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0) + (P_3P_2P_1P_0)C_0$
- ☞ $P_{0-3} = P_3P_2P_1P_0$
- $G_{0-3} = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0$




Carry Skip Adder

 - Looks for the cases in which the carry out is identical to carry in
 - All propagation
 - The most time-consuming path
- For such cases, **bypass** the original carry path
 - Generate carry out directly ($C_{out} = C_{in}$)
 - Use a MUX to select



Carry Select Adder

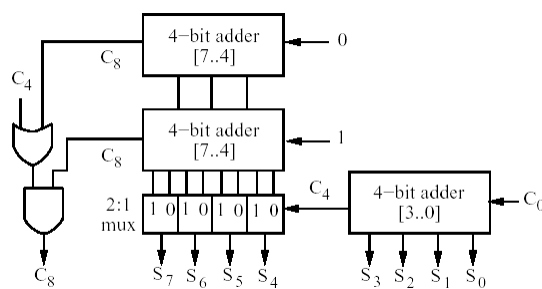- Compute two results in parallel, each for different carry assumptions
- Use actual carry in to select correct results
- Reduce delay to a multiplexer



3-43

Comparison of Adders


- Make comparison between Time (*speed*) and Space (*area*)
- Empirical average power consumption of 16-bit adders

Adder	Time	Space	Power (mW)
Ripple carry adder	$O(n)$	$O(n)$	0.117
Carry look-ahead adder	$O(\lg n)$	$O(n \lg n)$	0.171
Carry skip adder	$O(\sqrt{n})$	$O(n)$	0.109
Carry select adder	$O(\sqrt{n})$	$O(n)$	0.216

3-44

Binary Adder-Subtractor (1/2)

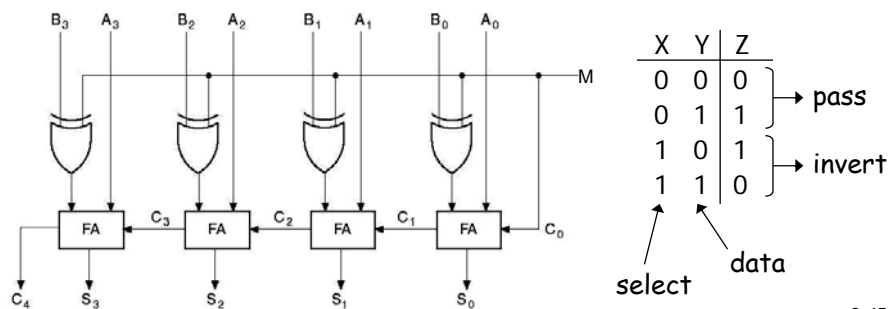- Subtraction can be achieved by adding 2's complement
 - $A - B = A + (-B)$
 - Complement each bit of B then add 1 to the result
- $M = 0$: addition
- $M = 1$: supply the additional "1" in subtraction



3-45

Binary Adder-Subtractor (2/2)


```

module Add_Sub (S, C4, A, B, M);
    input [3:0] A, B;
    input M; // 0: Add, 1: Sub
    output [3:0] S;
    output C4;
    wire [3:0] K;
    assign K = B ^ {4{M}};
    FA1 U0(S[0], C1, A[0], K[0], M);
    FA1 U1(S[1], C2, A[1], K[1], C1);
    FA1 U2(S[2], C3, A[2], K[2], C2);
    FA1 U3(S[3], C4, A[3], K[3], C3);
endmodule
    
```

3-46

Signed Adder-Subtractor

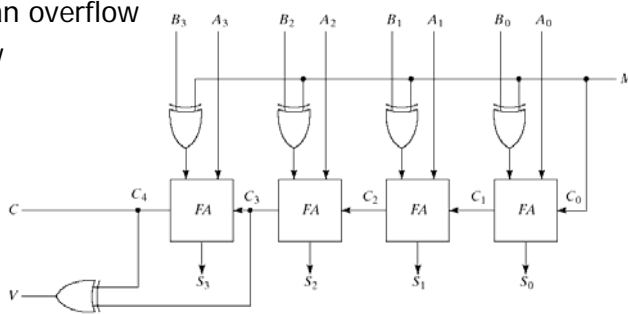- Unsigned
 - C detects a **carry** after addition or a **borrow** after subtraction
- Signed
 - V bit detects an overflow
 - 0: no overflow
 - 1: overflow




3-47

BCD Adder (1/2)

C detects whether the binary sum is greater than 9(1001)

$$C = K + Z_8 Z_4 + Z_8 Z_2$$

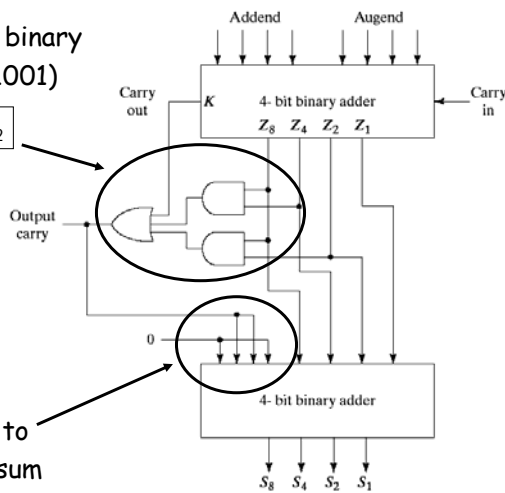

If C=1, it is necessary to add 6(0110) to binary sum

3-48

BCD Adder (2/2)

```

module bcd_add (S, Cout, A, B, Cin);
  input [3:0] A, B;
  input Cin;
  output [3:0] S;
  output Cout;
  reg [3:0] S;
  reg Cout;
  always @(A or B or Cin) begin
    {Cout, S} = A + B + Cin;
    if (Cout != 0 || S > 9) begin
      S = S + 6;
      Cout = 1;
    end
  end
end
endmodule

```


3-49

Binary Multiplier

- Ex: 2 x 2 multiplier


$$\begin{array}{r}
 \begin{array}{cc}
 B_1 & B_0 \\
 A_1 & A_0 \\
 \hline
 A_0B_1 & A_0B_0 \\
 A_1B_1 & A_1B_0 \\
 \hline
 C_3 & C_2 & C_1 & C_0
 \end{array}
 \end{array}$$

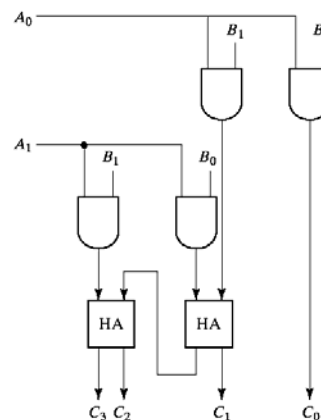- Compute partial products, and justify the sum of those partial products
- $m \times n$ digit multiplication generates up to an $(m+n)$ digit result
- Can be described using * (not recommended)




3-50

4-Bit By 3-Bit Binary Multiplier

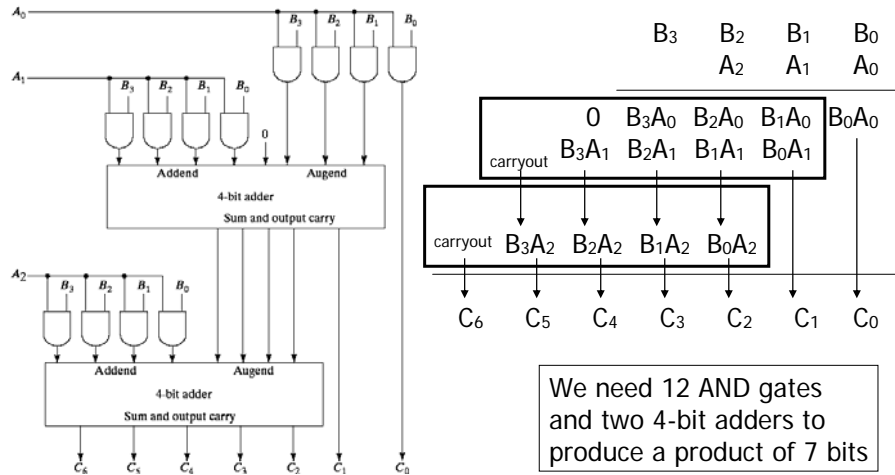

3-51


General Multiplier Architecture

 

3-52

Column Compression Tree

 - Also called *Wallace Tree*
- Use “carry in” to add three components at a time
- “carry out” is added in next column



3-53

Signed Multiplication

- Case: negative multiplicand, positive multiplier
→ sign extension works

$$\begin{array}{r}
 11010 \quad (-6) \\
 \times 01101 \quad (+13) \\
 \hline
 11111111010 \\
 00000000000 \\
 111111010 \\
 11111010 \\
 0000000 \\
 \hline
 1110110010 \quad (-78)
 \end{array}$$

sign extension {

- Other cases can be handled by applying 2's complement to appropriate numbers

3-54