

Modeling Digital Systems with Verilog

Prof. Chien-Nan Liu
TEL: 03-4227151 ext:34534
Email: jimmy@ee.ncu.edu.tw

6-1

Composition of Digital Systems

- Most digital systems can be partitioned into two types of modules:
 - Datapath: perform data-processing operations between registers
 - Controller: determine the sequence of those operations


 


Fig. 8-2 Control and Datapath Interaction

6-2

Register Transfer Operations

 
- The movement of the data stored in registers and the processing performed on the data are referred to as **register transfer operations**
- Ex: If $(K1 = 1)$ then $(R2 \leftarrow R1)$



6-3

Multiplexer-Based Transfer

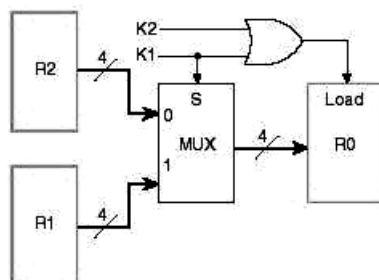- When a register receives data from two or more different sources at different times, a **multiplexer** can be used
- Ex: If $(K1 = 1)$ then $(R0 \leftarrow R1)$
 else if $(K2 = 1)$ then $(R0 \leftarrow R2)$



6-4

Bus-Based Transfer

- Each register has its own multiplexers
 - May be too complex for large systems
- Use shared transfer path instead
 - Often called a **bus**
 - Can have only one source but multiple destinations at a time
 - More hardware-efficient


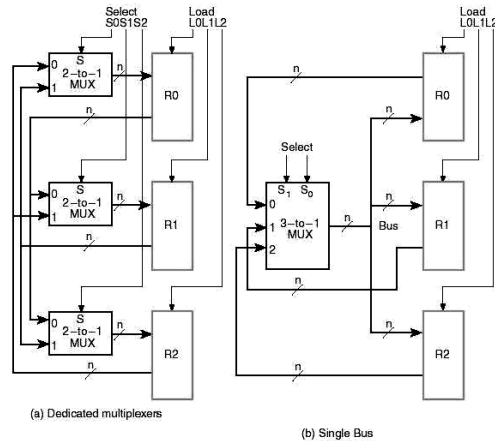


Fig. 7-6 Single Bus versus Dedicated Multiplexers

6-5

Three-State Bus

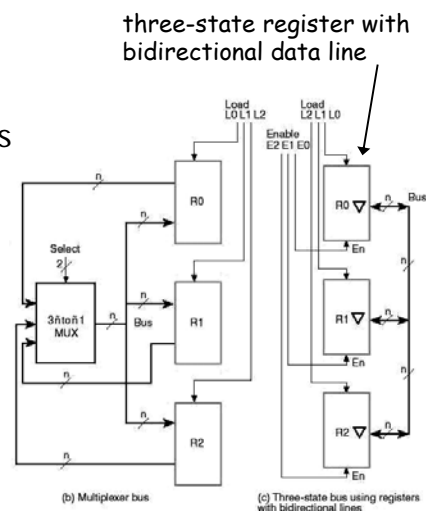
- A bus can be constructed with the three-state buffers
- Many three-state buffer outputs can be connected together
 - Avoid the high-fanin OR in multiplexers
 - Delay time and logic complexity can be reduced
- The signals can travel in two directions on a three-state bus
 - EN=1: output, EN=0: input
 - Simplify the interconnections



6-6

Disadv. of Three-State Bus

 - Bus connection problems
 - May reduce reliability
 - One and only one active bus driver at a time
 - Limited driving strength
- Bus floating problems
 - Floating nets with ambiguous logic values
 - Solution: **bus keeper** or pull up/down resistances
- ATPG problem
- FPGA prototyping problem



6-7

Modeling Three-State Registers

- To declare a bidirectional data port, *inout* type is used instead of *input* or *output*


- EX:

```
module TriReg(CLK, Rst, EN, Load, Data);
    input CLK, Rst, EN, Load;
    inout Data;
    reg int_data, Data;
```

separated to ensure correct circuits

```
    always @(posedge CLK) begin
        if (Rst) int_data = 0;
        else if (Load) int_data = Data;
    end
```
 
```
    always @(int_data or EN) begin
        if (EN) Data = int_data;
        else Data = 1`bz;
    end
endmodule
```



three-state control

6-8

HDL Modeling for Buses


- To model the behavior of a three-state bus, *tri* type is used instead of *wire*
 - *tri*: has the same properties of *wire* but indicates more than one drivers may connect to it
- Ex:

```

module TriBus(CLK, Rst, E2, E1, E0, L2, L1, L0);
input CLK, Rst, E2, E1, E0, L2, L1, L0;
tri databus;

TriReg R0(CLK, Rst, E0, L0, databus);
TriReg R1(CLK, Rst, E1, L1, databus);
TriReg R2(CLK, Rst, E2, L2, databus);
endmodule
    
```

all connected together

 


6-9

Datapaths

- A typical datapath often consists of:
 - Register file
 - Arithmetic/logic unit (ALU)
 - Shifter (may be implemented in ALU)
 - Status signals that feedback to controller

status bits

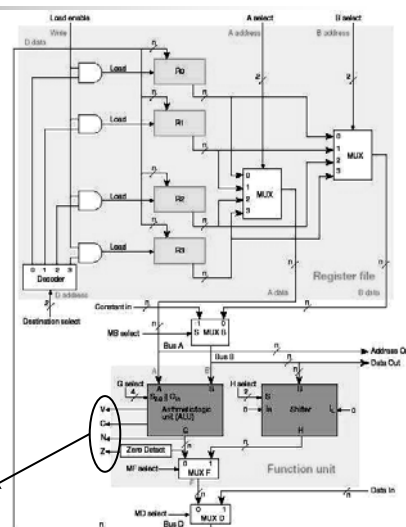

6-10

Arithmetic/Logic Unit

ALU =
Arithmetic Circuit
+ Logic Circuit

 


Fig. 7-15 One Stage of ALU

TABLE 7-8
Function Table for ALU

Operation Select				Operation	Function
S ₂	S ₁	S ₀	C _{in}		
0	0	0	0	$G = A$	Transfer A
0	0	0	1	$G = A + 1$	Increment A
0	0	1	0	$G = A + B$	Addition
0	0	1	1	$G = A + B + 1$	Add with carry input of 1
0	1	0	0	$G = A + \bar{B}$	A plus 1's complement of B
0	1	0	1	$G = A + \bar{B} + 1$	Subtraction
0	1	1	0	$G = A - 1$	Decrement A
0	1	1	1	$G = A$	Transfer A
1	0	0	X	$G = A \wedge B$	AND
1	0	1	X	$G = A \vee B$	OR
1	1	0	X	$G = A \oplus B$	XOR
1	1	1	X	$G = \bar{A}$	NOT (1's complement)

6-11

Arithmetic Circuit

Eight arithmetic functions can be performed by setting the three control signals: S₁, S₀, C_{in}.

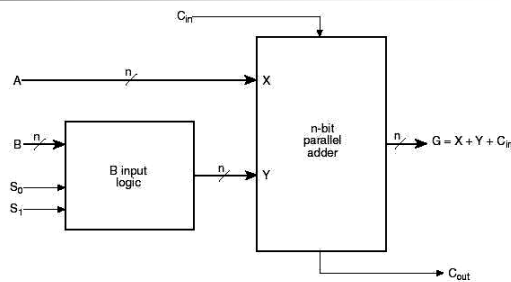


Fig. 7-11 Block Diagram of an Arithmetic Circuit

TABLE 7-7
Function Table for Arithmetic Circuit

Select		Input	$G = A + Y + C_{in}$	
S ₁	S ₀	Y	C _{in} = 0	C _{in} = 1
0	0	all 0's	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	B	$G = A + B$ (add)	$G = A + B + 1$
1	0	\bar{B}	$G = A + \bar{B}$	$G = A + \bar{B} + 1$ (subtract)
1	1	all 1's	$G = A - 1$ (decrement)	$G = A$ (transfer)

6-12

Logic Circuit

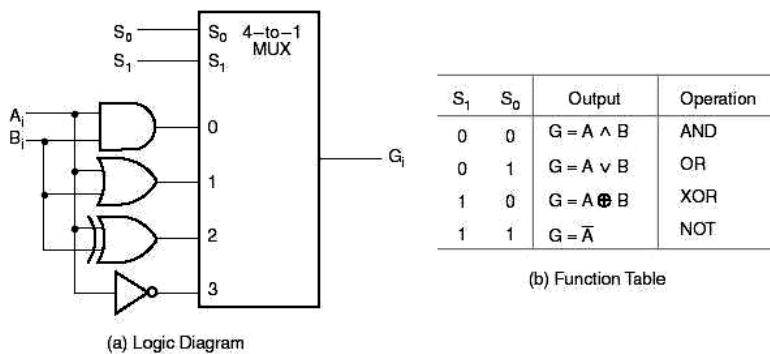



Fig. 7-14 One Stage of Logic Circuit

6-13

The Shifter

- A bidirectional shift register can meet the basic requirement for the shift operations
 - Shift left and shift right
- One shift operation per clock cycle for shift registers
 - A faster method is often required
- Combinational shifter can be used instead

 S=00 : keep unchanged
 S=01 : shift right
 S=10 : shift left
 S=11 : undefined



6-14

Barrel Shifter

- In some datapaths, the data must be shifted more than one bit position in a single clock cycle
 - Barrel shifter is used
- A barrel shifter with 2^n input and output lines requires 2^n multiplexers and n selection inputs

 



TABLE 7-9
Function Table for 4-Bit Barrel Shifter

Select		Output				Operation
S_1	S_0	Y_3	Y_2	Y_1	Y_0	
0	0	D_3	D_2	D_1	D_0	No rotation
0	1	D_2	D_1	D_0	D_3	Rotate one position
1	0	D_1	D_0	D_3	D_2	Rotate two positions
1	1	D_0	D_3	D_2	D_1	Rotate three positions

6-15

Modeling the Barrel Shifter

 - Describe one by one case (select)
 - 2^0 b00:
 $Y = D;$
 - 2^0 b01:
 $Y = \{D[2:0], D[3]\};$
 - 2^0 b10:
 $Y = \{D[1:0], D[3:2]\};$
 - 2^0 b11:
 $Y = \{D[0], D[3:1]\};$
- Incorrect description case (select)
 - 2^0 b00:
 $Y = D;$
 - 2^0 b01:
 $Y = D \ll 1;$
 -
 - endcase



the vacated bits are filled with 0, not really rotate

6-16

The Control Unit

- Two primary types of control units:
 - Programmable
 - Determine the performed operations according to the pre-stored *instructions* and associated operands
 - Non-programmable
 - Determine the performed operations and their sequence by only its inputs and the status bits

6-17


Design of Control Unit

- Design of control unit: the most challenging and creative part of digital design
 - Formulate hardware algorithms for achieving required objectives
- A special flowchart, *algorithmic state machine* (ASM), is often used to define hardware algorithms
 - Convenient to specify the procedural steps and decision paths with timing relationship
 - Easier to understand
 - Lead directly to hardware realization

6-18


Basic Elements of ASM Chart (1/2)

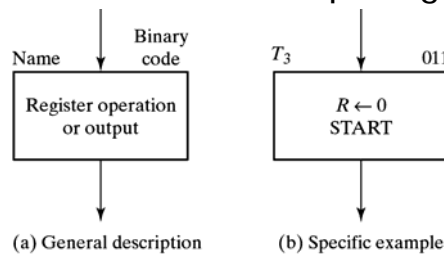- The ASM chart contains three basic elements:
 - State box (rectangle shape)
 - Decision box (diamond shape)
 - Conditional output box (oval shape)
- State box: containing register transfer operations or activated output signals



6-19



Basic Elements of ASM Chart (2/2)

 

- Decision box: describe the effect of inputs on the control
 - Two exit paths (true & false)

- Conditional output box: similar to state box but describe the operations after a condition is satisfied

From exit path of decision box

  

6-20

An Example of ASM Block

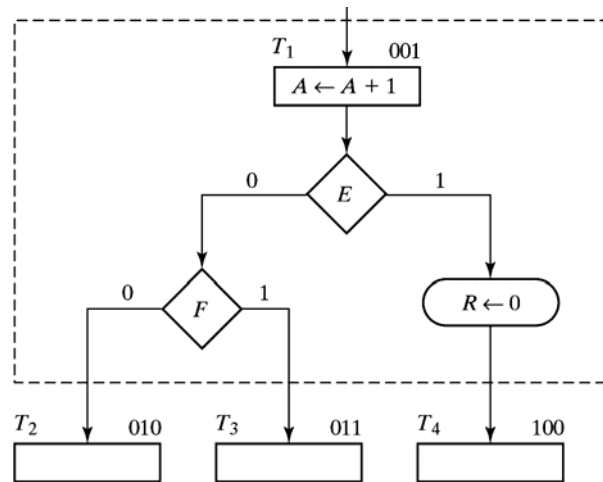


Fig. 8-6 ASM Block


6-21

ASM Block


- ASM chart is constructed from ASM blocks
- Contains exactly one state box
- One entrance path
- n exit paths
- Every valid input combination defines one exit path
- No internal feedback

6-22

ASM Block with Feedback

 


(a) Incorrect

 


(b) Correct

6-23

STG to ASM Chart

 

equivalent ASM chart

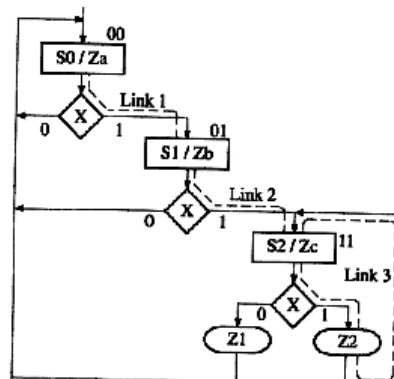

6-24

Timing Considerations

- Assume positive-edge triggering of all flip-flops in Fig. 8-6
- The ASM chart considers the entire block as one unit
 - All operations in the block must occur in the same clock cycle
- The following operations occur simultaneously after T1
 - Register A is incremented
 - If E=1, register R is cleared
 - Control transfer to the next state as specified in Fig. 8-7

 


Figure 8-7

 


Fig. 8-8 Transition Between States

6-25

Binary Multiplication

23	10111	Multiplicand
<u>19</u>	<u>10011</u>	Multiplier
	00000	Initial partial product
	<u>10111</u>	Add multiplicand, since multiplier bit is 1
	10111	Partial product after add and before shift
	010111	Partial product after shift
	<u>10111</u>	Add multiplicand, since multiplier bit is 1
	1000101	Partial product after add and before shift ^a
	1000101	Partial product after shift
	01000101	Partial product after shift
	001000101	Partial product after shift
	<u>10111</u>	Add multiplicand, since multiplier bit is 1
	110110101	Partial product after add and before shift
437	0110110101	Product after final shift

a. Note that overflow temporarily occurred.

6-26

Serial Binary Multiplier


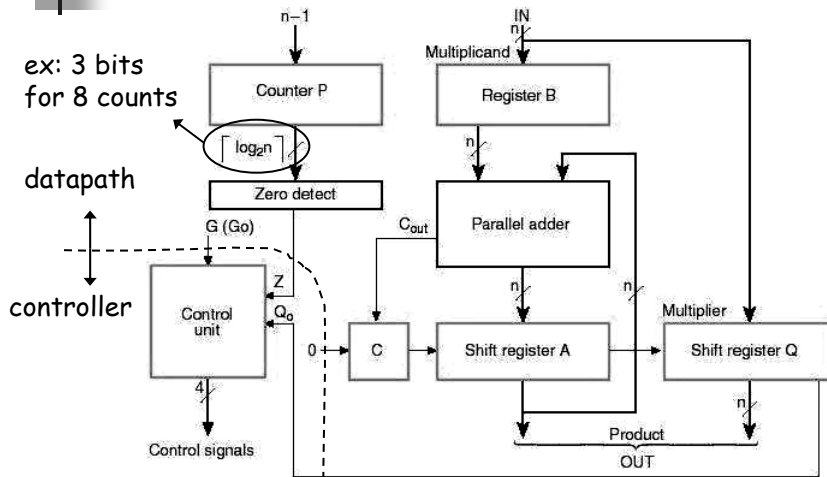


Fig. 8-6 Block Diagram for Binary Multiplier

6-27

ASM Chart for Multiplier

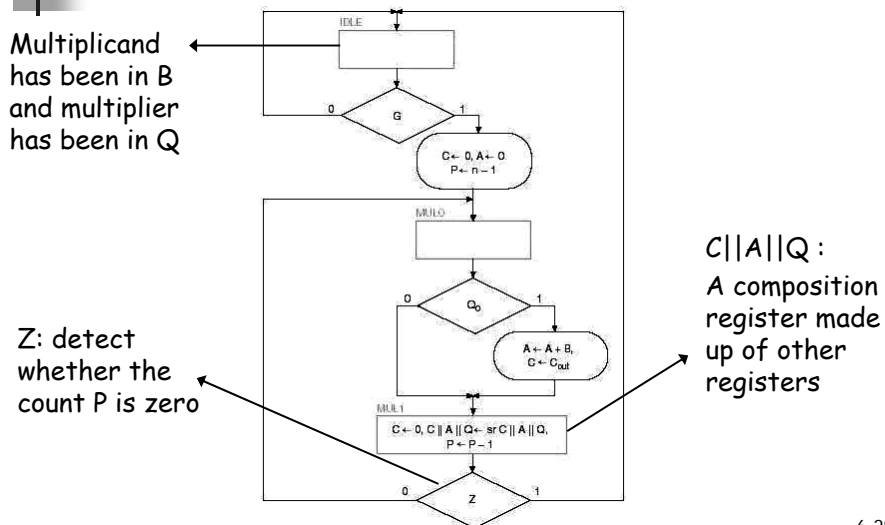

6-28

ASM Chart to Control Circuits

- Two design approaches are introduced for the control unit:
 - Hardwired control: dedicated circuits for generating the control signals
 - Sequence register and decoder approach
 - One flip-flop per state approach
 - Microprogrammed control: store its binary control values as words in memory
 - Execute the pre-stored *microprogram* according to the current control address

6-29

Hardwired Control

- Two primary parts:
 - Generate the control signals
 - Determine what happens next
- Analyze the required control signals:


□ TABLE 8-1
Control Signals for Binary Multiplier

Block Diagram Module	Microoperation	Control Signal Name	Control Expression
Register A:	$A \leftarrow 0$ $A \leftarrow A + B$ $C \ll A \ll Q \leftarrow sr \ C \ll A \ll Q$	Initialize Load Shift_dec	IDLE · G MUL0 · Q ₀ MUL1
Register B:	$B \leftarrow IN$	Load_B	LOADB
Flip-Flop C:	$C \leftarrow 0$ $C \leftarrow C_{out}$	Clear_C Load	IDLE · G + MUL1 —
Register Q:	$Q \leftarrow IN$ $C \ll A \ll Q \leftarrow sr \ C \ll A \ll Q$	Load_Q Shift_dec	LOADQ —
Counter P:	$P \leftarrow n - 1$ $P \leftarrow P - 1$	Initialize Shift_dec	— —

6-30

The Execution Sequence

 - Determine the execution sequence by removing
 - The information of microoperations
 - All conditional output boxes
 - The decision boxes not affecting the next state
- This simplified ASM chart is similar to the traditional state diagram



6-31

Sequence Register and Decoder

- A sequence register to determine the next states
 - Designed from the simplified ASM chart
- A decoder to generate required control signals for each state

TABLE 8-2
State Table for Sequence Register and Decoder Part
of Multiplier Control Unit

Present state	Inputs				Next state		Decoder Outputs			
	Name	M ₁	M ₀	G	Z	M ₁	M ₀	IDLE	MUL0	MUL1
IDLE	0	0	0	×	0	0	1	0	0	
	0	0	1	×	0	1	1	0	0	
MUL0	0	1	×	×	1	0	0	1	0	
MUL1	1	0	×	0	0	1	0	0	0	1
	1	0	×	1	0	0	0	0	0	1
—	1	1	×	×	×	×	×	×	×	×

6-32

The Final Circuits

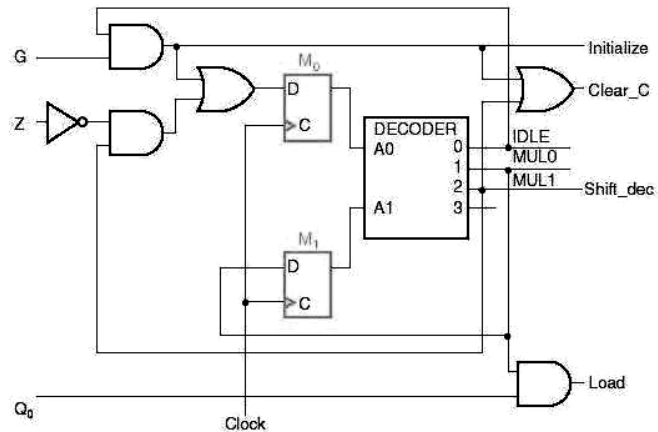


Fig. 8-9 Control Unit for Binary Multiplier Using a Sequence Register and a Decoder

6-33

Design with Multiplexers

- The sequence register and decoder control consists of three components:
 - Flip-flops: hold the binary value
 - Decoder: generates the control outputs
 - Some gates: determine the next state and the values of output signals
 - Can be replaced by multiplexers !!
- Using multiplexers results in a regular pattern of three levels of components
 - MUXs → flip-flops → decoder

6-34

ASM Chart for the Example

Inputs = (Next State) & (Input Conditions)

Table 8-7
Multiplexer Input Conditions

Present State		Next State		Input Conditions	Inputs	
G_1	G_0	G_1	G_0		MUX1	MUX2
0	0	0	0	w'		
0	0	0	1	w	0	w
0	1	1	0	x		
0	1	1	1	x'	1	x'
1	0	0	0	y'		
1	0	1	0	yz'	$yz' + yz = y$	yz
1	0	1	1	yz		
1	1	0	1	$y'z$		
1	1	1	0	y		
1	1	1	1	$y'z'$	$y + y'z' = y + z'$	$y'z + y'z' = y'$

used as MUX selection

required conditions to enable this transition

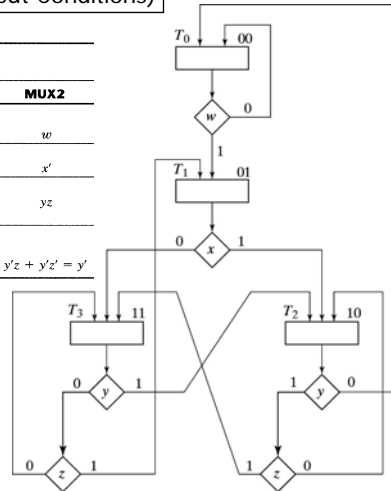


Fig. 8-19 Example of ASM Chart with Four Control Inputs 6-35

Implementation with MUXs

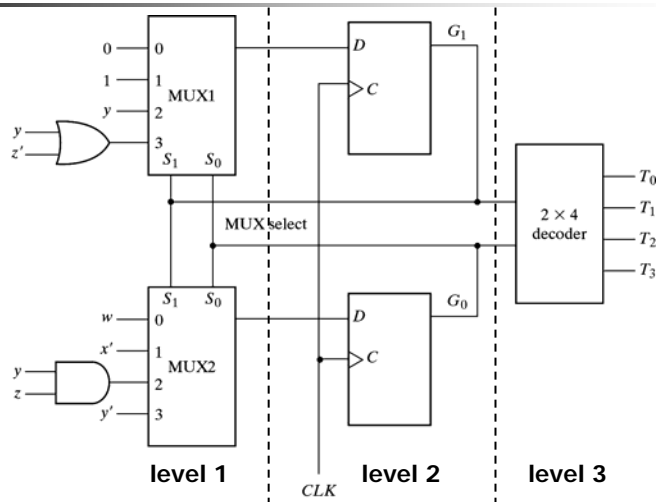


Fig. 8-20 Control Implementation with Multiplexers

6-36


One Flip-Flop per State

- Each state is assigned a different flip-flop
 - Flip-flop is 1: currently in its corresponding state
- Only one flip-flop contains a 1 at any time
 - The single 1 propagates from one flip-flop to another under the control of decision logic
- Maximum number of flip-flops are used
 - n vs. $\log_2 n$
- Simplify the decision logic and design procedure
 - Can be directly transformed from the ASM chart

6-37

Transformation Rules (1/2)

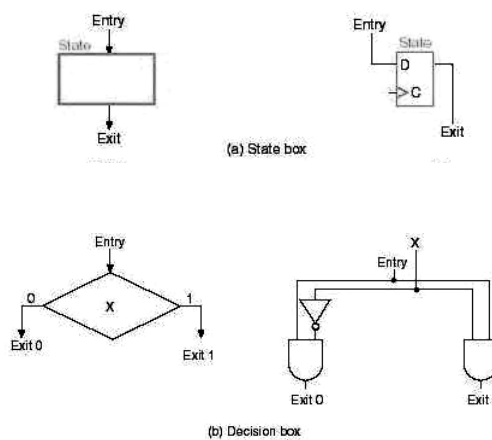- State box
 - Entry = 1:
going into the state
 - Exit = 1:
currently in the state
- Decision box
 - $X = 0$: send signal to the exit 0
 - $X = 1$: send signal to the exit 1




6-38

Transformation Rules (2/2)


- Junction

 - Wired-OR in nature
- OR all input signals



- Conditional output box

 
- Replaced by a connection only
- Attached a control line to trigger the output actions



6-39

The Final Circuit

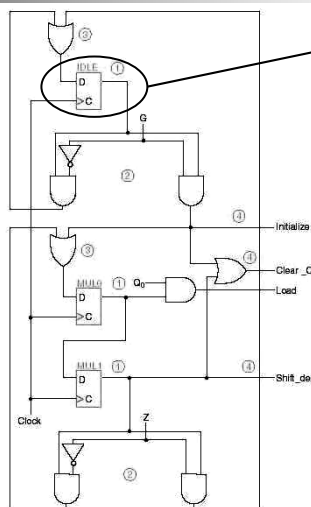- ① : state box
- ② : decision box
- ③ : junction
- ④ : conditional output



should be 1 at initialization

Solutions:

1. Use flip-flop with PRESET
2. Add inverters at both its input and output

Fig. 8-11 Control Unit with One Flip-Flop per State for the Binary Multiplier

6-40

Verilog Modeling (1/2)

```
// Binary Multiplier with n = 4: Verilog Description
// See Figures 8-6 and 8-7 for block diagram and ASM Chart

module binary_multiplier_v (CLK, RESET, G, LOADB, LOADQ,
    MULT_IN, MULT_OUT);
input CLK, RESET, G, LOADB, LOADQ;
input [3:0] MULT_IN;
output [7:0] MULT_OUT;
reg [1:0] state, next_state, P;
parameter IDLE = 2'b00, MULO = 2'b01, MULL = 2'b10;
reg [3:0] A, B, Q;
reg C;
wire Z;

assign Z = ~| P;
assign MULT_OUT = {A,Q};

//state register
always@(posedge CLK or posedge RESET)
begin
    if (RESET == 1)
        state <= IDLE;
    else
        state <= next_state;
end

end
```

6-41

Verilog Modeling (2/2)


```
//next state function
always@(G or Z or state)
begin
    case (state)
        IDLE:
            if (G == 1)
                next_state <= MULO;
            else
                next_state <= IDLE;
        MULO:
            next_state <= MULL;
        MULL:
            if (Z == 1)
                next_state <= IDLE;
            else
                next_state <= MULO;
    endcase
end

//datapath function
always@(posedge CLK)
```

```
begin
    if (LOADB == 1)
        B <= MULT_IN;
    if (LOADQ == 1)
        Q <= MULT_IN;
    case (state)
        IDLE:
            if (G == 1)
                begin
                    C <= 0;
                    A <= 4'b0000;
                    P <= 2'b11;
                end
            MULO:
                if (Q[0] == 1)
                    {C, A} = A + B;
            MULL:
                begin
                    C <= 1'b0;
                    A <= {C, A[3:1]};
                    Q <= {A[0], Q[3:1]};
                    P <= P - 2'b01;
                end
    endcase
end
endmodule
```

6-42

Microprogrammed Control

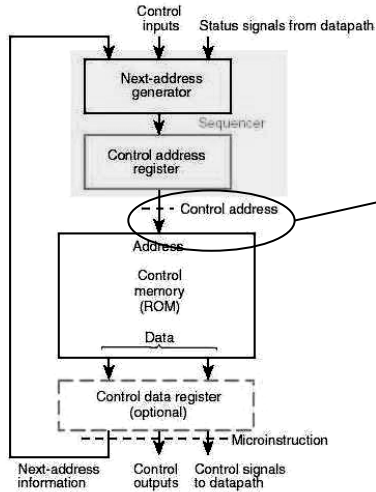


Determine the output actions by only state information (Moore type)

Fig. 8-16 Microprogrammed Control Unit Organization

6-43

Modify the ASM Chart

 

No conditional output boxes are allowed !! (replaced by a state box)

Fig. 8-17 ASM Chart for Microprogrammed Binary Multiplier Control Unit

6-44

Control Signal Analysis


TABLE 8-3
Control Signals for Microprogrammed Multiplier Control

Control Signal	Register Transfers	States in Which Signal is Active	Micro-instruction Bit Position	Symbolic Notation
Initialize	$A \leftarrow 0, P \leftarrow n-1$	INIT	0	IT
Load	$A \leftarrow A+B, C \leftarrow C_{out}$	ADD	1	LD
Clear_C	$C \leftarrow 0$	INIT, MUL1	2	CC
Shift_dec	$C[A]Q \leftarrow sr C[A]Q, P \leftarrow P-1$	MUL1	3	SD

6-45

Microinstruction Format

total: 12 bits

 

next address for FALSE

next address for TRUE

5 possible states require 3 bits for an address

the four control signals

TABLE 8-4
SEL Field Definition for Binary Multiplier Control Sequencing

SEL		
Symbolic notation	Binary Code	Sequencing Microoperations
NXT	00	$CAR \leftarrow NXTADD0$
DG	01	$\bar{G}: CAR \leftarrow NXTADD0$ $G: CAR \leftarrow NXTADD1$
DQ	10	$\bar{Q}_0: CAR \leftarrow NXTADD0$ $Q_0: CAR \leftarrow NXTADD1$
DZ	11	$\bar{Z}: CAR \leftarrow NXTADD0$ $Z: CAR \leftarrow NXTADD1$

6-46

The Final Circuit

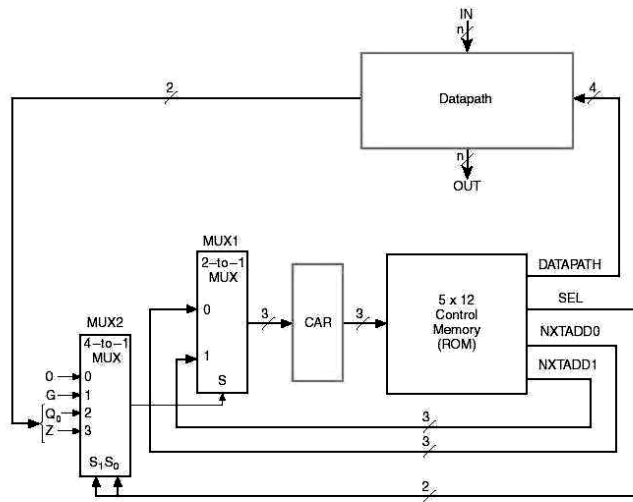


Fig. 8-19 Microprogrammed Control Unit for Multiplier

6-47

Microprogram Design

TABLE 8-5
Register Transfer Description of Binary Multiplier Microprogram

Address	Symbolic transfer statement
IDLE	$G: CAR \leftarrow INIT, \bar{G}: CAR \leftarrow IDLE$
INIT	$C \leftarrow 0, A \leftarrow 0, P \leftarrow n-1, CAR \leftarrow MUL0$
MUL0	$Q_0: CAR \leftarrow ADD, \bar{Q}_0: CAR \leftarrow MUL1$
ADD	$A \leftarrow A + B, C \leftarrow C_{out}, CAR \leftarrow MUL1$
MUL1	$C \leftarrow 0, C[A]Q \leftarrow sr C[A]Q, Z: CAR \leftarrow IDLE, \bar{Z}: CAR \leftarrow MUL0, P \leftarrow P-1$

TABLE 8-6
Symbolic Microprogram and Binary Microprogram for Multiplier

Address	NXTADD1	NXTADD0	SEL	DATAPATH	Address	NXTADD1	NXTADD0	SEL	DATAPATH
IDLE	INIT	IDLE	DG	None	000	001	000	01	0000
INIT	—	MUL0	NXT	IT, CC	001	000	010	00	0101
MUL0	ADD	MUL1	DQ	None	010	011	100	10	0000
ADD	—	MUL1	NXT	LD	011	000	100	00	0010
MUL1	IDLE	MUL0	DZ	CC, SD	100	000	010	11	1100

6-48

Why Pipelined System ?

- Conventional:
 - Max delay = 12ns
 - Clock rate = 83.3 MHz
 - Required 1 clock cycle to finish a operation
- Pipelined:
 - Max delay = 5ns
 - Clock rate = 200 MHz
 - Required 3 clock cycles (15ns) for a operation
 - Longer latency but higher throughput

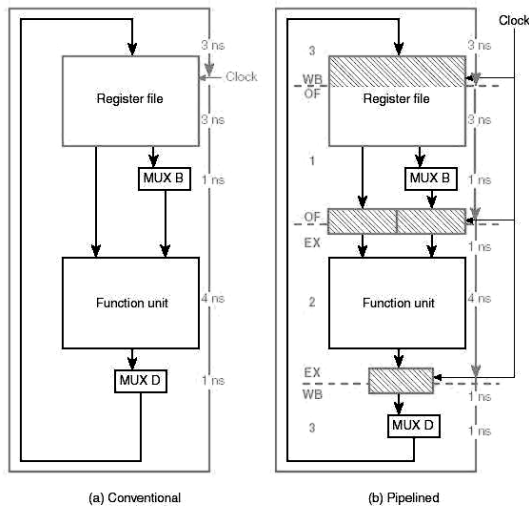


Fig. 7-21 Datapath Timing

Analogy to Pipelined Operations

- Can process next operation when current operation is sent to another stage
 - Every worker only finish a part of the product in the assembly line
- Can have almost n times improvements on total speed if multiple operations are processed


 


Fig. 7-22 Assembly Line Analogy to Datapath Pipeline

6-50

Pipelined Datapath Design

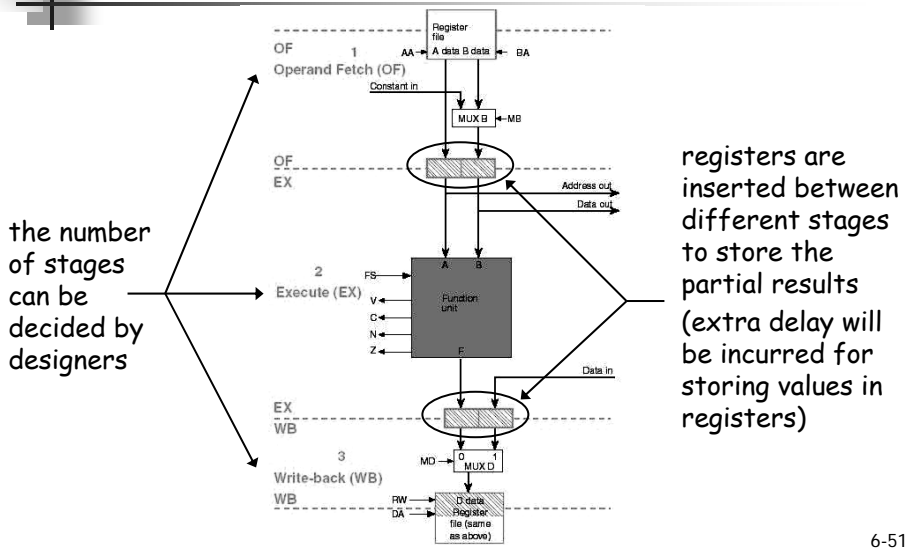

Execution in Pipelined Datapath

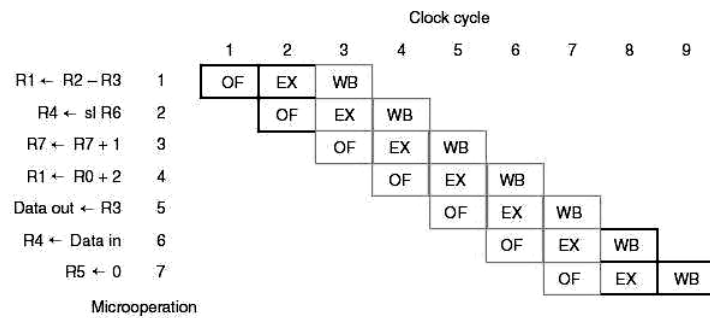


Fig. 7-24 Pipeline Execution Pattern for Microoperation Sequence in Table 7-13

Controller design for pipelined datapath will be more complex !!

Pipelined Control

store the fetched instruction

store the control signals

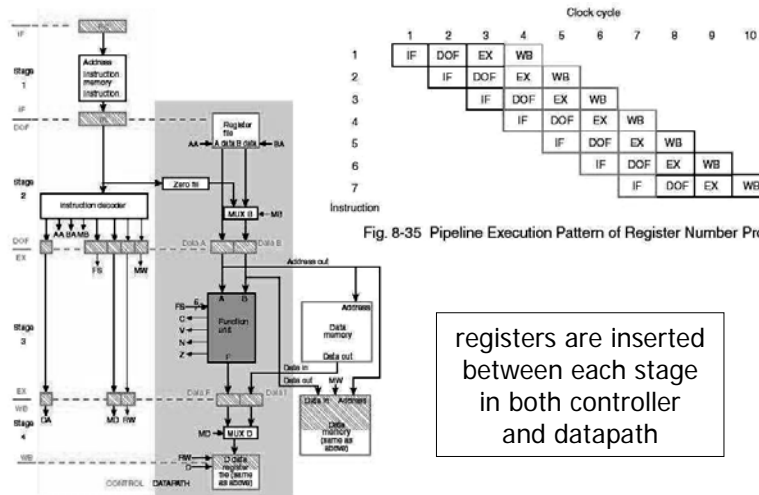


Fig. 8-35 Pipeline Execution Pattern of Register Number Program

registers are inserted between each stage in both controller and datapath

Fig. 8-34 Block Diagram of Pipelined Computer