

# Introduction to HDL Synthesis

---

Prof. Chien-Nan Liu  
TEL: 03-4227151 ext:34534  
Email: jimmy@ee.ncu.edu.tw

7-1


## Outline

---

- Synthesis overview
- RTL synthesis
  - Combinational circuit generation
  - Special element inferences
- Logic optimization
  - Two-level optimization
  - Multi-level optimization
- Modeling for synthesis

7-2

# Levels of Design

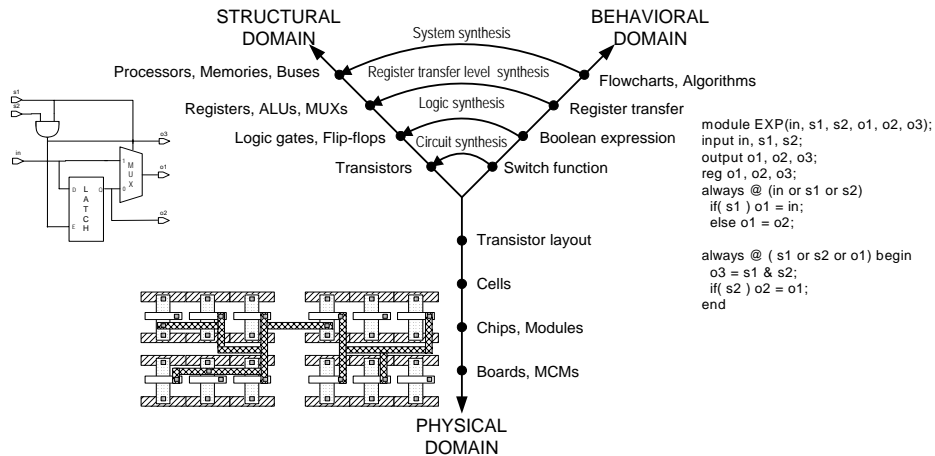

7-3


# Synthesis

- Transform HDL descriptions into logic gate networks (structural domain) in a particular library
- Advantages
  - Reduce time to generate netlists
  - Easier to retarget designs from one technology to another
  - Reduce debugging effort
- Requirement
  - **Robust HDL synthesizers**

7-4


# HDL Synthesis

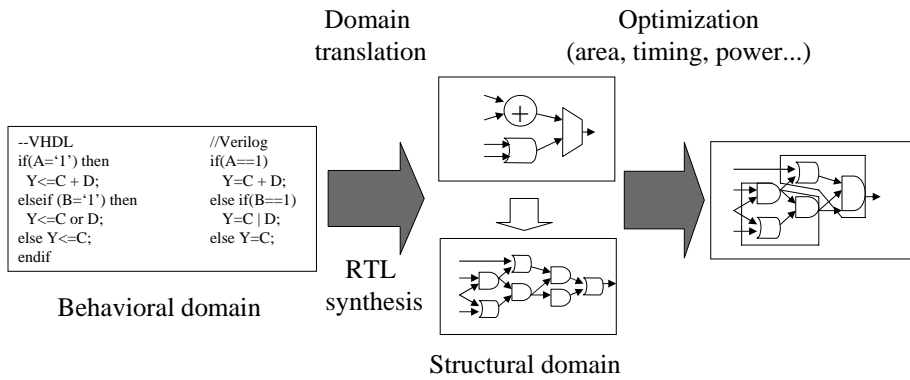**Synthesis = Domain Translation + Optimization**



7-5

# Domain Translation

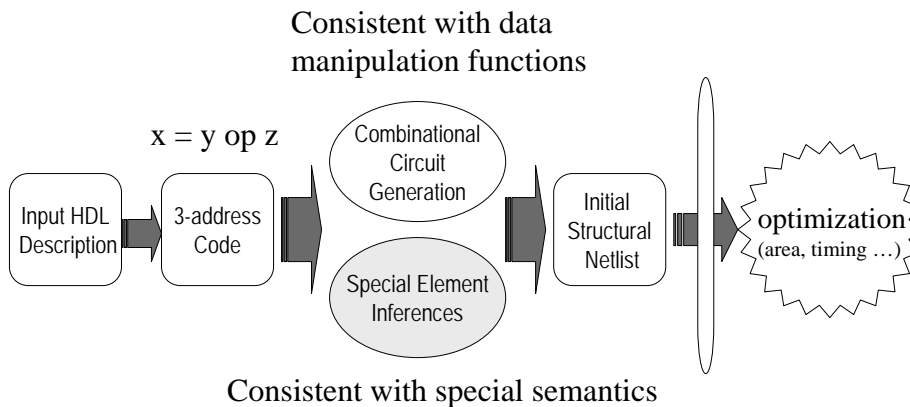

7-6

## Two-Level Logic Optimization

- Two-level logic representations
  - Sum-of-product form
  - Product-of-sum form
- Two-level logic optimization
  - Key technique in logic optimization
  - Many efficient algorithms to find a near minimal representation in a practical amount of time
  - In commercial use for several years
  - Minimization criteria: **number of product terms**
- Example:  $F = XYZ + \overline{X}\overline{Y}\overline{Z} + \overline{X}YZ + X\overline{Y}\overline{Z} + XY\overline{Y}\overline{Z}$



$$F = X\overline{Y} + YZ$$

7-7

## Multi-Level Logic Optimization

- Transforms a combinational circuit to meet performance or area constraints
  - Two-level minimization
  - Common factors or kernel extraction
  - Common expression resubstitution
- In commercial use for several years
- Example:

$$\begin{array}{l}
 f1 = abcd + abce + \overline{a}\overline{b}\overline{c}\overline{d} + \overline{a}\overline{b}\overline{c}\overline{d} + \\
 \quad \overline{a}c + cdf + \overline{a}bcde + \overline{a}bcdf \\
 f2 = bdg + \overline{b}dfg + \overline{b}dg + \overline{b}deg
 \end{array}
 \quad \longrightarrow \quad
 \begin{array}{l}
 f1 = c(\overline{a} + x) + \overline{a}\overline{c}\overline{x} \\
 f2 = gx \\
 x = d(b + f) + \overline{d}(\overline{b} + e)
 \end{array}$$

7-8


## Outline

- Synthesis overview
- **RTL synthesis**
  - Combinational circuit generation
  - Special element inferences
- Logic optimization
  - Two-level optimization
  - Multi-level optimization
- Modeling for synthesis

7-9
 
## Typical Domain Translation Flow

- Translate original HDL code into 3-address format
- Conduct special element inferences before combinational circuit generation
- Conduct special element inferences process by process (local view)



7-10


## Combinational Circuit Generation

- Functional unit allocation
  - Straightforward mapping with 3-address code
- Interconnection binding
  - Using control/data flow analysis

7-11
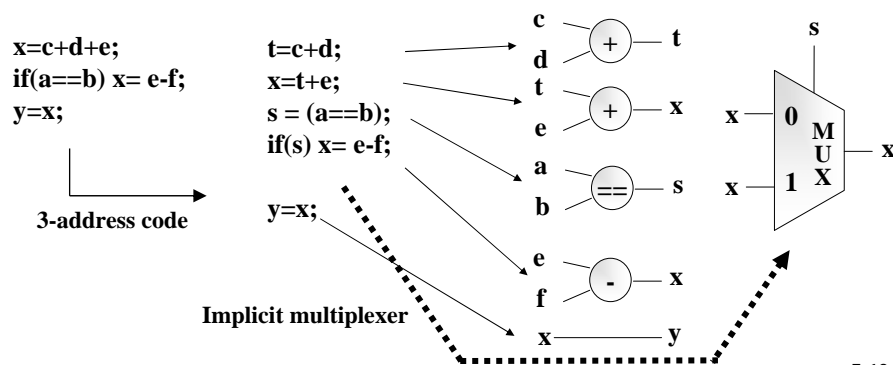
## Functional Unit Allocation

- 3-address code
  - $x = y \text{ op } z$  in general form
  - Function unit op with inputs y and z and output x



7-12


## Interconnection Binding

- Need the dependency information among functional units
  - Using **control/data flow analysis**
  - A traditional technique used in compiler design for a variety of code optimizations
  - Statically analyze and compute the set of assignments reaching a particular point in a program

7-13
 
## Control/Data Flow Analysis

```
/*d1*/ x = a;
  if(s) begin
/*d2*/   x = b;
/*d3*/   y = x + a;
  end
/*d4*/ y = x;
```



- Terminology
  - A **definition** of a variable x
    - An assignment assigns a value to the variable x
    - d1 can reach d4 but cannot reach d3
    - d1 is killed by d2 before reaching d3
  - A definition can only be affected by those definitions being able to reach it
  - Use a set of data flow equations to compute which assignments can reach a target assignment

7-14

# Combinational Circuit Generation

```

always @ ( x or a or b or c or d or s )
begin
/*d1*/ x = a + b;
/*d2*/ if ( s ) x = c - d;
/*d3*/ else x = x;
/*d4*/ y = x;
end
    
```




**Input HDL**

```


always @ ( x or a or b or c or d or s )
begin
/*d1*/ x = a + b;
/*d2*/ if ( s ) x = c - d;
/*d3*/ else x = x;
/*d4*/ x = s mux x;
/*d5*/ y = x;
end
    
```

**Modified 3-address code**


**Functional unit allocation**

   

 **computed by control/ data flow analysis**



**Interconnection binding**

 

**Final result**

7-15

# Special Element Inferences

- Given a HDL code at RTL, three special elements need to be inferred to keep the special semantics
  - Latch (D-type) inference
  - Flip-Flop (D-type) inference
  - Tri-state buffer inference
- Some simple rules are used in typical approaches

```

reg Q;
always@(D or en)
if(en) Q = D;
    
```

**Latch inferred!!**

```

reg Q;
always@(posedge clk)
Q = D;
    
```

**Flip-flop inferred!!**

```

reg Q;
always@(D or en)
if(en) Q = D;
else Q = 1'bz;
    
```

**Tri-state buffer inferred!!**

7-16

## Preliminaries

- Sequential section
  - Edge triggered always statement
- Combinational section
  - All signals whose values are used in the always statement are included in the sensitivity list

```
reg Q;  
always@(posedge clk)  
  Q = D;
```

**Sequential section**  
Conduct flip-flop inference

```
reg Q;  
always@(in or en)  
  if(en) Q=in;
```


**Combinational section**  
Conduct latch inference

7-17

## Rules of Latch Inference

- Condition 1: There is no branch associated with the output of a conditional assignment for a value of the selector
  - Output depends on its previous value implicitly

```
always@(s or a)  
if(s) Q=a;
```

 

Q depends on its  
previous value  
at this branch


7-18

## Rules of Latch Inference

- Condition 2: The output value of a conditional assignment depends on its previous value explicitly

always@(s or z or y or a)
 
```
begin
  z = y;
  if(s) y=a;
  else y=z;
end
```



y depends on its previous value at this branch via the assignment z=y;

7-19

## Typical Latch Inference

- Conditional assignments are not completely specified
  - Check if the *else-clause* exists
- Outputs conditionally assigned in an if-statement are not assigned before entering or after leaving the if-statement

always@(D or S)

```
if(S) Q = D;
```

↳ Infer latch for Q

always@(S or A or B)

```
begin
```

```
  Q = A;
```

```
  if(S) Q = B;
```


```
end
```

→ Do not infer latch for Q


7-20

## Typical Coding Style Limitation

```
always@(a or en)
  if(en) x=a;
```

 
 
```
always@(a or en)
  if(en) x=a;
  else x=x;
```



Latch description

7-21


## Typical Coding Style Limitation

- Process by process
  - No consideration on the dependencies across processes
  - No warrantee on the consistency of memory semantics

```
module EXP(in, s1, s2, o1, o2, o3);
  input in, s1, s2;
  output o1,o2,o3;
  reg o1, o2, o3;
  always@(in or s1 or o2)
    /*d1*/ if(s1) o1=in;
    /*d2*/ else o1=o2;
  always@( s1 or s2 or o1) begin
    /*d3*/ o3=s1&s2;
    /*d4*/ if(s2) o2=o1;
  end
endmodule
```

**o1 depends on its value via o2 at d4**

**Infer a latch for o2**

 

**Asynchronous feedback loop**

7-22


## Terminology

- Clocked statement: edge-triggered always statement
  - Simple clocked statement
    - e.g., **always @ (posedge clock)**
  - Complex clocked statement
    - e.g., **always @ (posedge clock or posedge reset)**
- **Flip-flop inference** must be conducted only when synthesizing the **clocked statements**

7-23
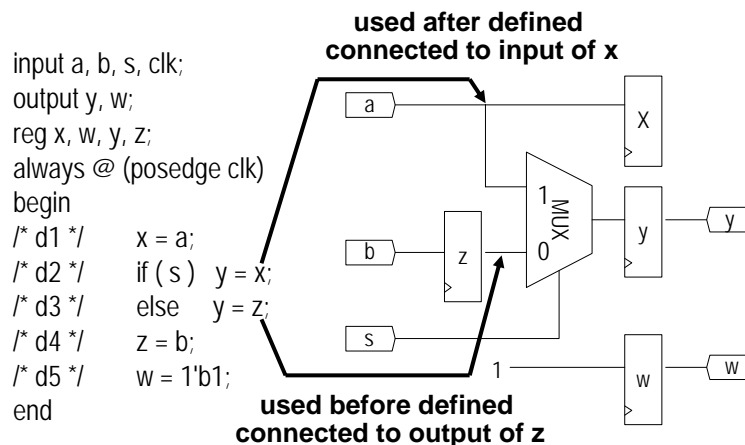
## Infer FF for Simple Clocked Statements


- Infer a flip-flop for **each variable** being assigned in the simple clocked statement



7-24
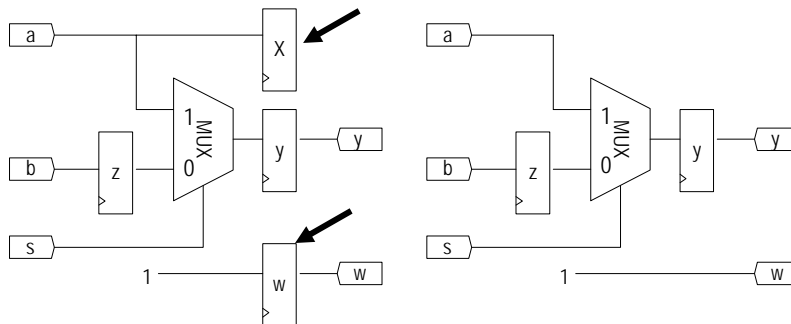
## Infer FF for Simple Clocked Statements

- Two post-processes
  - Propagating constants
  - Removing the flip-flops without fanouts



7-25

## Infer FF for Complex Clocked Statements

- Require the following syntactic template
  - An if-statement immediately follows the always statement
  - Each variable in the event list except the *clock signal* must be a selective signal of the if-statements
  - Assignments in the blocks B1 and B2 must be constant assignments (e.g., x=1, etc.)

**always @ (posedge clock or posedge reset or negedge set)**


```

if(reset) begin B1 end
else if ( !set) begin B2 end
else begin B3 end
    
```

7-26
 
## Typical Coding Style Limitation

```
always @ (posedge clk or posedge R)
if(R) Q = 0;
else Q = D;
```



```
always @ (posedge clk or posedge R)
begin
Q = D;
if(R) Q = 0;
end
```




7-27

 
## Typical Tri-State Buffer Inference

- If a data object Q is assigned a high impedance value 'Z' in a multi-way branch statement (if, case, ?:)
  - Associated Q with a tri-state buffer
- If Q associated with a tri-state buffer has also a memory attribute (latch, flip-flop)
  - Have **Hi-Z propagation problem**
    - Real hardware cannot propagate Hi-Z value
  - Require two memory elements for the control and the data inputs of tri-state buffer

```
reg Q;
always @ (En or D)
if(En) Q = D;
else Q = 1'bz;
```


 
```
reg Q;
always @ (posedge clk)
if(En) Q = D;
else Q = 1'bz;
```




7-28

## Typical Tri-state Buffer Inference

- It may suffer from mismatches between synthesis and simulation
  - Process by process
  - May incur the Hi-Z propagation problem

```
reg QA, QB;  
always @ (En or D)  
if(En) QA = D;  
else QA = 1'bz;
```
 
```
always @ (posedge clk)  
QB = QA;
```



7-29

## Comments on Special Element Inference

- Typical synthesizers
  - Use ad hoc methods to solve latch inference, flip-flop inference and tri-state buffer inference
  - Incur extra limitations on coding style
  - Do not consider the dependencies across processes
  - Suffer from synthesis/simulation mismatches
- A lot of efforts can be done to enhance the synthesis capabilities
  - It may require more computation time
  - Users' acceptance is another problem

7-30

## Outline

- Synthesis overview
- RTL synthesis
  - Combinational circuit generation
  - Special element inferences
- **Logic optimization**
  - Two-level optimization
  - Multi-level optimization
- Modeling for synthesis

7-31

## Two-Level Logic Optimization

**Basic idea:** Boolean law  $x+x'=1$  allows for grouping  $x_1x_2+x_1x_2' = x_1$

Approaches to simplify logic functions:


- Karnaugh maps [Kar53]
- Quine-McCluskey [McC56]

7-32

# 3-Variable Karnaugh Maps


## ■ Example

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

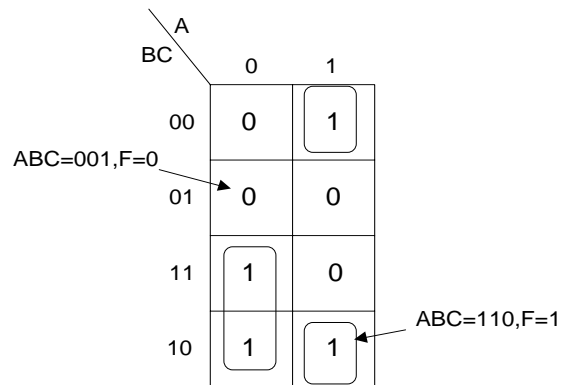

7-33

# Implicant

 

7-34


## Minimum Form

- A sum-of-products expression containing a non-prime implicant cannot be minimum
  - Could be simplified by combining the nonprime term with additional minterm
- To find the minimum sum-of-products
  - Find a minimum number of prime implicants which cover all of the 1's
  - Not every prime implicant is needed
  - If prime implicants are selected in the wrong order, a nonminimum solution may result

7-35
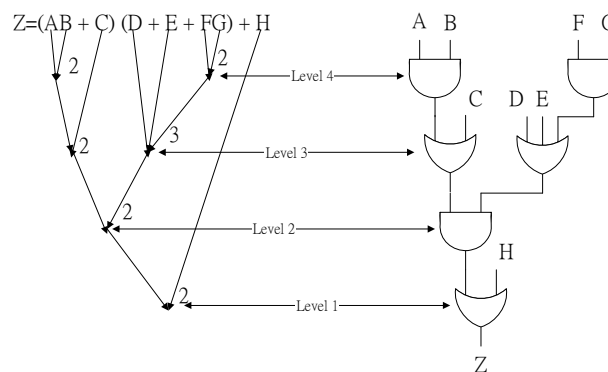
## Multi-Level Logic

- Multi-level logic:
  - A set of logic equations with no cyclic dependencies
- Example:  $Z = (AB + C)(D + E + FG) + H$ 
  - 4-level, 6 gates, 13 gate inputs



7-36

## Multi-Level v.s. Two-Level

- Two-level:
  - Often used in control logic design
$$f_1 = x_1x_2 + x_1x_3 + x_1x_4$$
$$f_2 = x_1'x_2 + x_1'x_3 + x_1x_4$$
  - Only  $x_1x_4$  shared
  - Sharing restricted to common cube

7-37

## Multi-Level v.s. Two-Level

- Multi-level:
  - Datapath or control logic design
  - Can share  $x_2 + x_3$  between the two expressions
  - Can use complex gates
$$g_1 = x_2 + x_3$$
$$g_2 = x_2x_4$$
$$f_1 = x_1y_1 + y_2$$
$$f_2 = x_1'y_1 + y_2$$

( $y_i$  is the output of gate  $g_i$ )

7-38

## Multi-Level Logic Optimization

- Technology independent
  - Decomposition/Restructuring
    - Algebraic
    - Functional
  - Node Optimization
    - Two-level logic optimization techniques are used

7-39

## Basic Operations

### 1. decomposition

(single function)

$$f = abc + abd + (ac)'d' + b'c'd'$$



$$\begin{aligned} f &= xy + (xy)' \\ x &= ab \\ y &= c + d \end{aligned}$$

### 2. extraction

(multiple functions)

$$\begin{aligned} f &= (az + bz')cd + e \\ g &= (az + bz')e' \\ h &= cde \end{aligned}$$



$$\begin{aligned} f &= xy + e \\ g &= xe' \\ h &= ye \\ x &= az + bz' \\ y &= cd \end{aligned}$$

7-40

## Basic Operations

### 3. factoring

(series-parallel decomposition)

$$f = ac + ad + bc + bd + e$$



$$f = (a + b)(c + d) + e$$

### 4. substitution

(with complement)

$$g = a + b$$

$$f = a + bc + b'c'$$




$$f = g(a + c) + g'c'$$

### 5. elimination

$$f = ga + g'b$$

$$g = c + d$$

 

$$f = ac + ad + bc'd'$$

$$g = c + d$$

**“Division” plays  
a key role !!**

7-41

## Division

- Division:  $p$  is a Boolean divisor of  $f$  if  $q \neq \phi$  and  $r$  exist such that  $f = pq + r$ 
  - $p$  is said to be a factor of  $f$  if in addition  $r = \phi$  :
 
$$f = pq$$
    - $q$  is called the **quotient**
    - $r$  is called the **remainder**
    - $q$  and  $r$  are **not unique**
  - **Weak division**: the unique algebraic division such that  $r$  has as few cubes as possible
    - The quotient  $q$  resulting from weak division is denoted by  $f / p$  (it is **unique**)

7-42

## Weak Division Algorithm

Weak\_div( $f, p$ ):

$U =$  Set  $\{u_j\}$  of cubes in  $f$  with literals not in  $p$  deleted

$V =$  Set  $\{v_j\}$  of cubes in  $f$  with literals in  $p$  deleted

*/\* note that  $u_j v_j$  is the  $j$ -th cube of  $f$  \*/*

$V^i = \{v_j \in V : u_j = p_j\}$

$q = \cap V^i$

$r = f - pq$

return( $q, r$ )

7-43

## Weak Division Algorithm

### ■ Example

common expressions

$$f = \boxed{acg + adg} + ae + \boxed{bc + bd + be + a'b}$$

$$p = ag + b$$

$$U = \boxed{ag + ag} + a + \boxed{b + b + b + b}$$

$$V = \boxed{c + d} + e + \boxed{c + d + e + a'}$$

$$V^{ag} = \boxed{c + d}$$

$$V^b = \boxed{c + d} + e + a'$$

$$q = c + d = f/p$$

7-44

## Outline

- Synthesis overview
- RTL synthesis
  - Combinational circuit generation
  - Special element inferences
- Logic optimization
  - Two-level optimization
  - Multi-level optimization
- Modeling for synthesis

7-45

## Non-Synthesizable Verilog Constructs

Not commonly supported by synthesis tools !!

- initial
- Loops
  - repeat
  - forever
  - while
- Data types
  - event
  - real
  - time
- UDPs
- fork ...join blocks
- procedural assignments
  - assign and deassign
  - force and release
  - disable
- Some operators
  - / and %
  - === and !==

7-46

## Typical HDL Synthesizer Directives

- Directives : special case of regular comments
  - Ignored by the simulator
  - Affect the synthesis results
- Turn translator off by using

```
// synopsys translate_off
/* synopsys translate_off */
```
- Turn translator on by using

```
// synopsys translate_on
/* synopsys translate_on */
```

7-47

## case

- The first case-item that evaluates to true determines the path
- Full case
  - HDL compiler directive
  - Use “ synopsys full\_case ”
- Parallel case
  - if HDL Compiler can statically determine or
  - Use “ synopsys parallel\_case ”

7-48

## case Examples

- full and parallel

```
input [1:0] a;
always @ (a or w or x or
y or z)
begin
  case (a)
    2'b11: b = w ;
    2'b10: b = x ;
    2'b01: b = y;
    2'b00: b = z;
  endcase
end
```

- parallel but not full

```
input [1:0] a;
always @ (a or w or z)
begin
  case (a)
    2'b11: b = w;
    2'b00: b = z;
  endcase
end
```

7-49

## case Examples (cont'd)

- Not full nor parallel

```
always @ (w or x) begin
  case (2'b11)
    w:
      b=10;
    x:
      b=01;
  endcase
end
```

7-50

## parallel\_case

- //synopsys parallel\_case
  - Affect the way logic is generated for the case statement
  - Generate mux logic instead of priority encoder
  - Used when only one case-item is executed

```
reg [3:0] current_state,next_state;
parameter state1 = 4'b0001, state2 = 4'b0010,
           state3 = 4'b0100, state4 = 4'b1000;
case (1) //synopsys parallel_case
  current_state[0] : next_state = state2;
  current_state[1] : next_state = state3;
  current_state[2] : next_state = state4;
  current_state[3] : next_state = state1;
endcase
```

7-51

## full\_case

- //synopsys full\_case
  - Asserts all possible clauses of a case statement have been covered
  - Can avoid the need for default logic
  - Avoid latch inference

```
reg[1:0] in,out;
reg[3:0] current_state, next_state;
parameter state1 = 4'b0001, state2 = 4'b0010,
           state3 = 4'b0100, state4 = 4'b1000;
case (in) //synopsys full_case
  0: out = 2;
  1: out = 3;
  2: out = 0;
endcase
```

p1

7-52

## full\_case (cont'd)

```
reg [1:0] state,next_state;
//synopsys state vector state
always @ (state or in) begin
  case (state) //synopsys full_case
    0: begin
      out=3;
      next_state =1;
    end
    1: begin
      out=2;
      next_state =2;
    end
    2: begin
      out=1;
      next_state =3;
    end
    3:begin
      out= 0;
      if (in)
        next_state =0;
      else
        next_state=3;
    endcase
  end
always @ (posedge clock)
  state = next_state;
```

p2

p3

7-53

## Directives for Register Inference


- `async_set_reset` : use `//synopsys async_set_reset`

```
module async_set_reset ( reset, set, d, gate, y, t );
input reset, set, gate, d;
output y, t;
// synopsys async_set_reset "reset, set"
reg y, t;
always @ (reset or set)
begin : direct_set_reset
  if(reset)
    y=1'b0; //asynchronous reset
  else if(set)
    y=1'b1; //asynchronous set
end
always @ (gate or reset) // for set (gate or set)
if (reset) //for set : if (set)
  t=1'b0; // for set : t=1'b1
else if (gate)
  t=d;
endmodule
```

7-54

## Directives for Register Inference

- `async_set_reset`

 

7-55

## Directives for Register Inference

- `sync_set_reset` : use `//synopsys sync_set_reset "object_name"`

```
module sync_set_reset ( clk, reset, set, d1, d2, y, t );
input  clk, reset, set, d1, d2;
output y, t;
// synopsys sync_set_reset "reset, set"
reg y, t;
always @ (posedge clk)
begin : synchronous_reset
if (reset)
y=1'b0; // synchronous reset
else
y=d1;
end
always @ (posedge clk)
begin : synchronous_set
if (set)
t=1'b1; // synchronous set
else
t=d2;
end
endmodule
```

7-56

## Directives for Register Inference

- One\_hot
  - No more than one signal is active high
  - use //synopsys one\_hot "object\_name"

```

module one_hot_example
    (reset,set,reset2,set2,y,t);

input reset,set,reset2,set2;
output y,t;
//synopsys async_set_reset "reset,set"
//synopsys async_set_reset "reset2,set2"
//synopsys one_hot "reset,set"
reg y,t;

always @ (reset or set)
begin : direct_set_reset
    if (reset)
        y=1'b0; // asynchronous reset by "reset"
    else if(set)
        y=1'b1; // asynchronous set by "set"
    end
end
    
```

p1

```

always @ (reset2 or set2)
begin : direct_set_reset_too
    if (reset2)
        t=1'b0; // asynchronous reset by "reset2"
    else if(set2)
        t=1'b1; // asynchronous set by "~reset2 set2"
    end
// synopsys translate_off
always @(reset or set)
    if (reset & set)
        $write("ONE_HOT violation for
                'reset','set'.");
//synopsys translate_on
endmodule
    
```

p2

7-57

## Directives for Register Inference

- One\_cold
  - No more than one signal is active low
  - use //synopsys one\_cold "object\_name"

```

module one_cold (reset,set,reset2,set2,y,t);
input reset,set,reset2,set2;
output y,t;
//synopsys async_set_reset "reset,set"
//synopsys async_set_reset "reset2,set2"
//synopsys one_cold "reset,set"
reg y,t;

always @ (reset or set)
begin : direct_set_reset
    if (~reset)
        y=1'b0; // asynchronous reset by "~reset"
    else if(~set)
        y=1'b1; // asynchronous set by "~set"
    end
end
    
```

p1

```

always @ (reset2 or set2)
begin : direct_set_reset_too
    if (~reset2)
        t=1'b0; // asynchronous reset by "~reset2"
    else if(~set2)
        t=1'b1; // asynchronous set by "reset2 ~set2"
    end
// synopsys translate_off
always @(reset or set)
    if (~reset & ~set)
        $write("ONE_COLD violation for
                'reset','set'.");
//synopsys translate_on
endmodule
    
```


p2

7-58
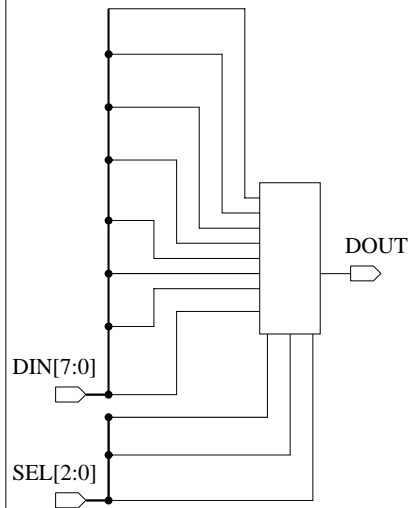
## Multiplexer Inference

```
module mux8to1(DIN,SEL,DOUT):
input [7:0] DIN;
input [2:0] SEL;
output DOUT;
reg DOUT;

//synopsys infer_mux "mux_blk"
always @ (SEL or DIN)
begin: mux_blk
  case (SEL)
    3'b000: DOUT <= DIN[0];
    3'b001: DOUT <= DIN[1];
    3'b010: DOUT <= DIN[2];
    3'b011: DOUT <= DIN[3];
    3'b100: DOUT <= DIN[4];
    3'b101: DOUT <= DIN[5];
    3'b110: DOUT <= DIN[6];
    3'b111: DOUT <= DIN[7];
  endcase
end
endmodule
```



7-59

## Resource Sharing

- Assigning similar operations to a common netlist cells
  - Can reduce hardware
  - May degrade performance
- Possible sharing
  - \*
  - + -
  - > >= < <=
  - sharing within the same always block

7-60

## Control Flow Conflict

- Two operations can be shared only if no execution path exists from the start of the block to the end of the block that reaches both operations

```

always begin
  Z1=A + B;
  if(COND_1)
    Z2= C + D;
  else begin
    Z2= E + F;
    if(COND_2)
      Z3=G + H;
    else
      Z3=I + J;
  end
  end
  if(! COND_1)
    Z4= K + L;
  else
    Z4= M +N;
end
    
```

	A+B	C+D	E+F	G+H	I+J	K+L	M+N
A+B		no	no	no	no	no	no
C+D	no		yes	yes	yes	no	no
E+F	no	yes		no	no	no	no
G+H	no	yes	no		yes	no	no
I+J	no	yes	no	yes		no	no
K+L	no	no	no	no	no		yes
M+N	no	no	no	no	no	yes	


7-61

## Data Flow Conflict

- No sharing if causes a combinational loop

```

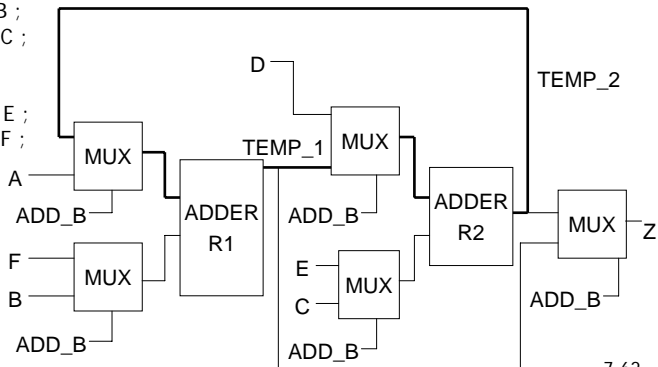always @ (A or B or C or D or E or F or Z or ADD_B)
begin
  if (ADD_B) begin
    Temp_1 = A + B ;
    Z = Temp_1 + C ;
  end
  else begin
    Temp_2 = D + E ;
    Z = Temp_2 + F ;
  end
end
end
    
```



7-62

## Resource Sharing Methods

- Automatic

- HDL compiler identifies the possibility
- Logic optimizer minimizes the area while meeting the timing constraints

```
always @ (A or B or C or ADD_B)
begin
  if (ADD_B)
    Z = B + A;
  else
    Z = A + C;
end
```

- 2 adders with a output mux (sharing)
- 1 adder with 1 input mux (no sharing)

7-63

## Resource Sharing Methods (cont'd)

- Manual

- Synthesizer provides some directives
- Force the sharing of specified operations
- Prevent the sharing of specified operations
- Force specified operations to use a particular type of resource
- Only in a named combinational block

```
module TWO_ADDS_6 (A, B, C, Z, ADD_B);
  input [3:0] A,B,C;
  input ADD_B;
  output [3:0] Z;
  reg[3:0] Z;
  always @ (A or B or C or ADD_B) begin : b1
    /*synopsys resource r0; ops = "A1 A2"; */
    if (ADD_B)
      Z= A + B; //synopsys label A1
    else
      Z= A + C; //synopsys label A2
  end
endmodule
```

p1

- Declare an identifier for an individual resource.  
resource r0;
- Place labels on the operations.  
if (ADD\_B)  
    Z= A + B; //synopsys label A1  
else  
    Z= A + C; //synopsys label A2  
endif;
- Use the ops directive to bind the labeled operations to the resource they share.  
ops = "A1 A2";

p2

7-64


## Explicit Resource Sharing

- |            |            |
|------------|------------|
| ■ Original | ■ Modified |
| if (F)     | if(F)      |
| A=B+C;     | T=C;       |
| else       | else       |
| A=B+20;    | T=20;      |
|            | A=B+T;     |


7-65

## Using Parenthesis

$$A=B+C+D+F$$

 

$$A=(B+C)+(D+F)$$

 

7-66