

Timing Issues in Digital Designs

Prof. Chien-Nan Liu
TEL: 03-4227151 ext:34534
Email: jimmy@ee.ncu.edu.tw

8-1

Outline

- Timing Models in Digital Circuits
- Timing Analysis
- Timing Optimization
- Retiming for Sequential Circuits

8-2

Functionality vs. Performance

- Functionality: system correctly implements specified function
 - Mostly checked by simulation (logic, RTL, behavior)
- Performance: system correctly implements specified function at specified speed
 - Another important consideration in a design
 - Can be checked by simulation or static analysis
- There is always a trade-off between cost (area) and performance
 - Require some estimations at design level

8-3

Delay Model at Logic Level

1. unit delay model
 - Assign a delay of 1 to *each gate*
2. unit fanout delay model
 - Incorporate an *additional* delay for *each fanout*
3. library delay model
 - Use delay data in the library to provide more accurate delay value
 - May use linear or non-linear (tabular) models
 - Rising delay and falling delay are separated
 - [min, typ, max] model may also be used

8-4

Factors that Affect Timing

 


FIGURE 11-9 Factors affecting the timing of a synchronous circuit.


8-5

Linear Delay Model

$$\text{Delay} = D_{\text{slope}} + D_{\text{intrinsic}} + D_{\text{transition}} + D_{\text{wire}}$$

D_s : Slope delay : delay at input A caused by the transition delay at B

 D_w : Wire delay : time from state transition at C to state transition at D




D_I : Intrinsic delay : incurred from cell input to cell output

D_T : Transition delay : output pin loading, output pin drive

8-6

Tabular Delay Model

 - Delay values are obtained by a look-up table
 - Two-dimensional table of delays (m by n)
 - with respect to input slope (m) and total output capacitance (n)
 - Each value in the table is obtained by real measurement



- Can be more precise than linear delay model
 - table size \uparrow \rightarrow accuracy \uparrow

8-7


Timing Models of Flip-Flops

- The delay time of a flip-flop is often referred to the **clock-to-Q** delay
 - Operations can start only when clock signal arrives
- The arrival time of clock signal must also be considered
 - Often be referred to the **clock uncertainty** (clock jitter, clock skew, ...)
- Setup Time:** The length of time that data must stabilize before the clock transition
 - The maximum data path is used to check setup time
- Hold Time:** The length of time that data must remain stable after the active clock transition
 - The minimum data path is used to check hold time


8-8

Setup & Hold Times

- Timing Diagram

 


- Valid Data Transition

 

8-9


Interconnect Delay

- As taught in digital design course, interconnect delays can be ignored compared to gate delays
 - Is it true in deep-submicron process
- Wire delays start to dominate total delay in DSM era
 - Should be considered carefully
- Several RC delay models for a net are available
 - Ex: π model
- However, only rough wire delay model can be used at design phase
 - Basically, wire delay is determined by wire length
 - Lack of physical information about wire length at early stage
 - Not accurate at all, just an experience value

 


8-10

Wiring Delay vs. Feature Size

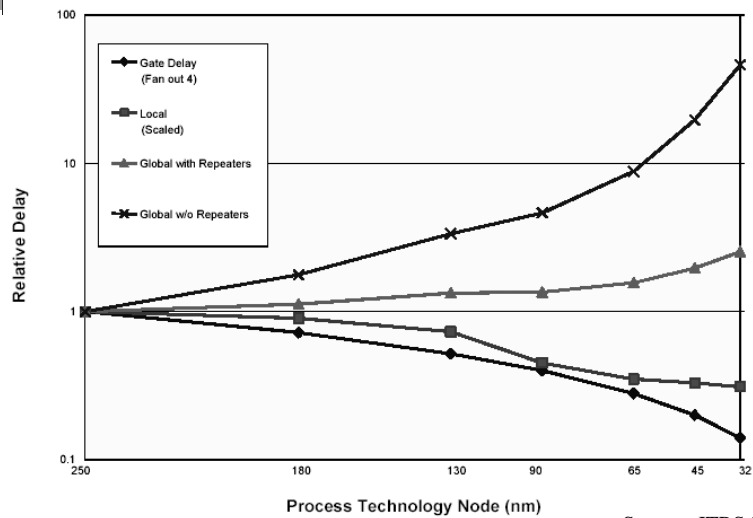

Source : ITRS 2001 8-11

Crosstalk Noise Between Wires

 

- Two neighbor wires may be affected by each other
 - Depending on the types of the two signal transitions
- Crosstalk noise may cause
 - Glitch and logical error
 - Extra propagation delay on wires
- Require complex analysis to predict the effects

8-12


Outline

- Timing Models in Digital Circuits
- Timing Analysis
- Timing Optimization
- Retiming for Sequential Circuits

8-13

What is STA ?

 - STA = static timing analysis
- STA is a method for determining if a circuit meets timing constraints without having to simulate




Reference :Synopsys

8-14


Timing Paths

 - There are 4 types of timing path
 - Input port to data pin of FF (path 1)
 - Clock pin of FF to data pin of FF (path 2)
 - Clock pin of FF to output port (path 3)
 - Input port to output port (path 4)



Timing Constraint
 
$$T_{clock} > t_{clk_to_output} + T_{comb_max} + T_{setup} + T_{skew}$$



Arrival Time and Required Time

- arrival time : calculated from input to output
- required time : calculated from output to input
- slack = required time - arrival time

$A(j)$: arrival time of signal j

$R(k)$: required time for signal k

$S(k)$: slack of signal k


$D(j,k)$: delay of node j from input k

$$A(j) = \max_{k \in FI(j)} [A(k) + D(j,k)]$$

$$r(j,k) = R(j) - D(j,k)$$

$$R(k) = \min_{j \in FO(k)} [r(j,k)]$$


$$S(k) = R(k) - A(k)$$

 

8-17

Delay Graph

 - Replace logic gates with delay blocks
- Add start (S) and end (E) blocks
- Indicate signal flow with directed arcs



8-18


Longest and Shortest Path

- If we visit vertices in precedence order, the following code will need executing only once for each u

Update Successors[u]



```

 1  for each vertex  $v \in Adj[u]$  do
2    if  $A[v] < A[u] + \Delta[u]$  // longest
3      then  $A[v] \leftarrow A[u] + \Delta[u]$ 
4       $LP[v] \leftarrow u$  fi
5    if  $a[v] > a[u] + \delta[u]$  // shortest
6      then  $a[v] \leftarrow a[u] + \delta[u]$ 
7       $SP[v] \leftarrow u$  fi
    
```




8-19

Delay Graph and Topological Sort

  

8-20

Delay Calculation

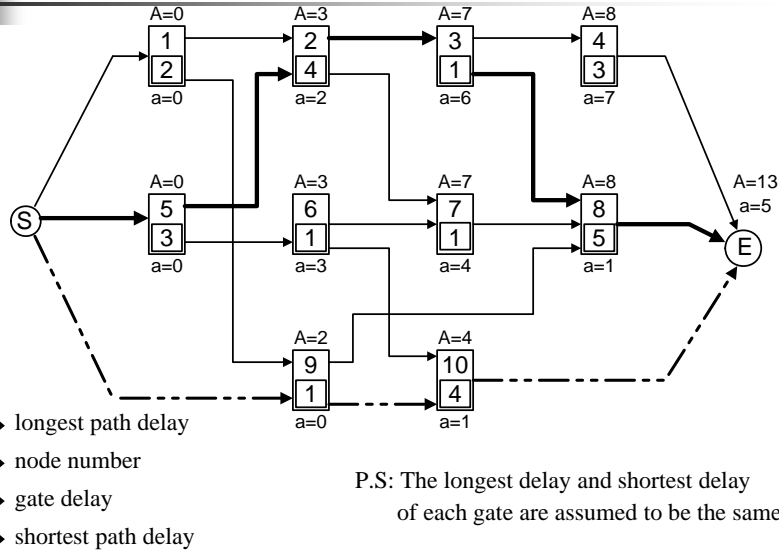

8-21

Timing Report

| Point | Fanout | Incr | Path |
|-----------------------------|--------|--------|---------|
| | | | |
| U19/Z (INB) | | 0.38 | 50.76 r |
| n397 (net) | 8 | 0.00 | 50.76 r |
| data_tri[5]/Z (BTD) | | 0.37 | 51.13 f |
| data[5] (net) | 8 | 0.00 | 51.13 f |
| data[5] (inout) | | 0.00 | 51.13 f |
| data arrival time | | | 51.13 |
| clock clk (rise edge) | | 100.00 | 100.00 |
| clock network delay (ideal) | | 0.00 | 100.00 |
| clock uncertainty | | -0.50 | 99.50 |
| output external delay | | -20.00 | 79.50 |
| data required time | | | 79.50 |
| data required time | | | 79.50 |
| data arrival time | | | -51.13 |
| slack (MET) | | | 28.37 |

Meet timing

8-22


The False Path Problem

- Pattern-independent analysis calculates the delay of logic gates without regard to their function
 - Can result in delays that are unnecessarily conservative
- Some paths may never be sensitized false paths
- Checking for false paths requires the function of the gates to be considered
 - Can approach the complexity of logic simulation or test generation

8-23


Combinational False Paths

 - A false path is a path that is never exercised in operation
- The Classical example :



Longest true path
has delay 30

- A carry bypass adder

 

8-24

Path Sensitization



| VALUE GATE | Controlling value | NonControlling Value |
|---------------|----------------------|-------------------------|
| AND | 0 | 1 |
| NAND | 0 | 1 |
| OR | 1 | 0 |
| NOR | 1 | 0 |
| NOT | 0, 1 | --- |

- Path $P = (I , G1 , G2 , \dots , Gn , O)$ is sensitizable if there is at least one vector which sensitizes the path

8-25

Path Sensitization

 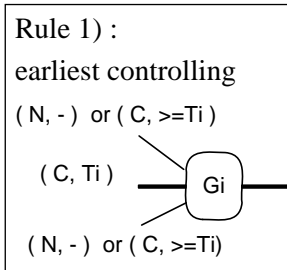Path $P = (I , G1 , G2 , \dots , Gn , O)$ is sensitizable under input vector V , if each gate meets either of the following rules under V .



(stable value, stable time)


N : Non - controlling input , C : Controlling input

T_i = delay of partial path (I , G1 , G2 , ... , Gi)

8-26

Accurate Performance

 
- Actual delay of the circuit: delay of the **Longest Sensitizable Path**
 - The longest sensitizable path can be much shorter than the longest path in a complex circuit
 - Accuracy increases at the expense of computing efficiency



8-27

Statistical Timing Model

 
- Circuit delay elements are statistical in nature
 - Process variation
 - Manufacturing defects (open, short, ...)
 - Power supply noise
 - Interconnect crosstalk



8-28

Where is the Critical Path?

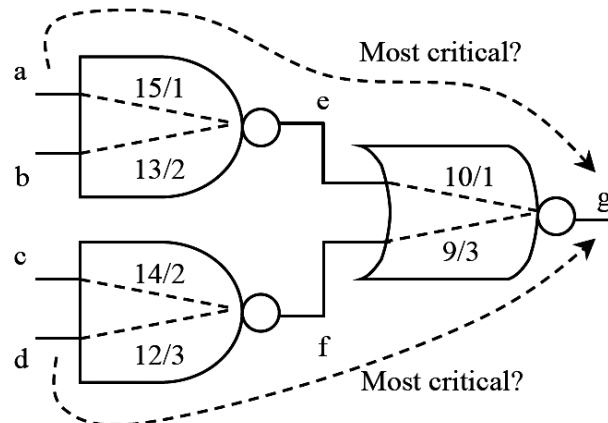
- The most critical path can be different based on which delay model you have in mind



8-29

Statistical Static Timing Analysis

 - The delay of each element is a statistical distribution
 - When calculating the total delay, the "sum" of every gates becomes the "convolution" of their PDF curves
- How critical a path is can be defined as the probability of exceeding the clock period T
- Ex: crt. Prob. = 0.1 for a path P
 - Out of 100 chips, 10 of them have path P 's delay > clock



8-30

Statistical Analysis of s38584


Statistical Analysis

Mean 567.0
Std.dev. 4.29 (0.8%)
 $\mu+3\sigma$ 579.9

Traditional static analysis:

Circuit delay:

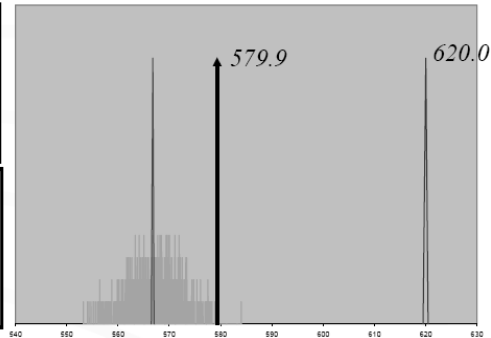cell delay is μ_c : 566.8
cell delay is $\mu_c+3\sigma_c$: 620.0



Delay of traditional worst-case analysis (620.0) is greater than that of the 3σ delay of statistical analysis (579.9)!!

8-31


Outline

- Timing Models in Digital Circuits
- Timing Analysis
- Timing Optimization
- Retiming for Sequential Circuits

8-32

Timing Optimization

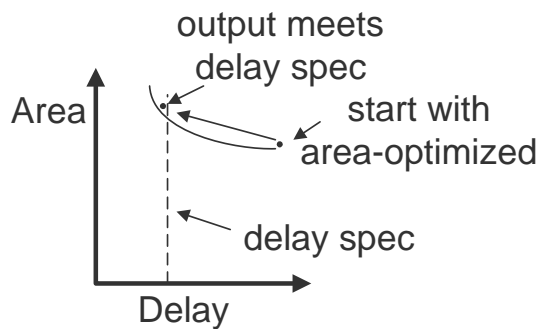- There is always a trade-off between area and delay
- Optimize timing to meet delay spec. with minimum area



8-33

Restructuring Algorithm


While (circuit timing improves) do
 select regions to transform
 collapse the selected region
 resynthesize for better timing
done

- Which regions to restructure ?
- How to resynthesize to minimize delay ?

8-34

Restructuring Regions

 - All nodes with slack within ε of the most critical signal belong to the ε -network
- To improve circuit delay, necessary and sufficient to improve delay at nodes on cut-set of ε -network



8-35

Find the Cutset

- The weight of each node is $W = W_{xt} + \alpha * W_xa$
 - W_{xt} is potential for speedup
 - W_xa is area penalty for duplication of logic
 - α is decided by various area/delay tradeoff
- Apply the maxflow-mincut algorithm to generate the cutset of the ε -network
- ε : Specify the size of the ε -network
 - Large ε might waste area without much reduction in critical delay
 - Small ε might slow down the algorithm
- α : Control the tradeoff between area and speed
 - Large α avoids the duplication of logic
 - $\alpha = 0$ implies a speedup irrespective of the increase in area

8-36


Timing Optimization Techniques (1/8)

- Fanout optimization
 - Buffer insertion
 - Split
- Timing-driven restructuring
 - Critical path collapsing
 - Timing decomposition
- Misc
 - De Morgan
 - Repower
 - Down power
- Most of them will increase area to improve timing
 - Have to make a good trade-off between them

8-37

Timing Optimization Techniques (2/8)

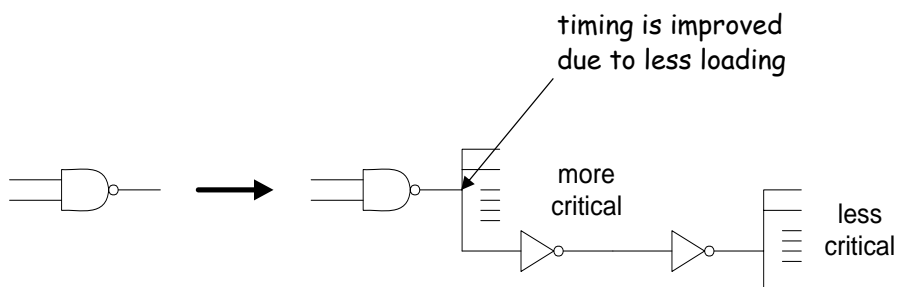
- **Buffer insertion:** divide the fanouts of a gate into critical and non-critical parts and drive the non-critical fanouts with a buffer



8-38

Timing Optimization Techniques (3/8)

 
- **Split:** split the fanouts of a gate into several parts. Each part is driven with a copy of the original gate.



8-39

Timing Optimization Techniques (4/8)

 
- **Critical path collapsing:** reduce the depth of logic networks



8-40

Timing Optimization Techniques (5/8)

 
- Timing decomposition:** restructuring the logic networks to minimize the arrival time



8-41

Timing Optimization Techniques (6/8)

 
- De Morgan:** replace a gate with its dual, and reverse the polarity of inputs and output
 - NAND gate is typically faster than NOR gate



8-42

Timing Optimization Techniques (7/8)

 
- **Repower:** replace a gate with one of the other gate in its logic class with higher driving capability



8-43

Timing Optimization Techniques (8/8)

 - **Down power:** reducing gate size of a non-critical fanout in the critical path



8-44



Outline

- Timing Models in Digital Circuits
- Timing Analysis
- Timing Optimization
- Retiming for Sequential Circuits

8-45

Retiming

  
- Exploit the ability to move registers in a circuit
 - To minimize the cycle time
 - To minimize the the number of registers for a given cycle time



8-46

Moving Registers

- Combinational logic are not modified

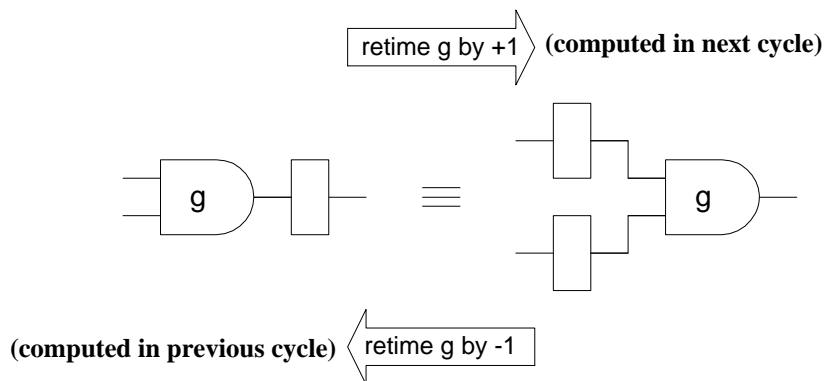

8-47

Formulation

- Directed graph:
 - Nodes - combinational logic
 - Edges - connections (possibly latched) between logic
- Weights
 - Nodes - combinational logic propagation delay
 - Edges - number of registers
- Path delay $d(P)$: sum of node delays along a path
- Path weight $w(P)$: sum of edge weights along a path
- Clock period: $\Phi(G) = \max\{d(p) \mid w(p) = 0\}$

8-48

Some Definitions

- $\mathcal{W}(u, v)$ is defined as the minimum number of registers on any path from vertex u to vertex v
- The critical path p is a path from u to v such that $\mathcal{W}(p) = \mathcal{W}(u, v)$
- $D(u, v)$ is defined as the maximum total propagation delay on any critical path from u to v

8-49

Synchronous Circuits


A synchronous circuit must satisfy following rules:

- D1: The propagation delay $d(v)$ is non-negative for each vertex v
 - Infeasible in real cases
- W1: The register count $\mathcal{W}(e)$ is non-negative for each edge e
 - Infeasible in real cases
- W2: In any directed cycle, there is some edge with positive register count
 - No combinational loops

8-50


Retiming: Formulation

 - Assign an integer-valued labeling r to each vertex
- $w_r(u, v) = w(u, v) + r(v) - r(u)$
- $w_r(p) = w(p) + r(v) - r(u)$
- Corollary: For any cycle p , $w_r(p) = w(p)$
- Legal retiming needs only being checked against condition W1: non-negative edge weight
- Corollary: Let G be a synchronous circuit and r be a retiming on G . Then the retimed graph G_r satisfies condition W2



8-51

Relocating Registers

 


8-52

Retiming and Resynthesis

- Migrate all registers to the periphery of a sub-network
 - Peripheral retiming
- Optimize the sub-network with any combinational technique
 - Resynthesis
- Replace registers back in the sub-network
 - Retiming
- This procedure may further improve the timing across the registers

8-53


Examples of Resynthesis

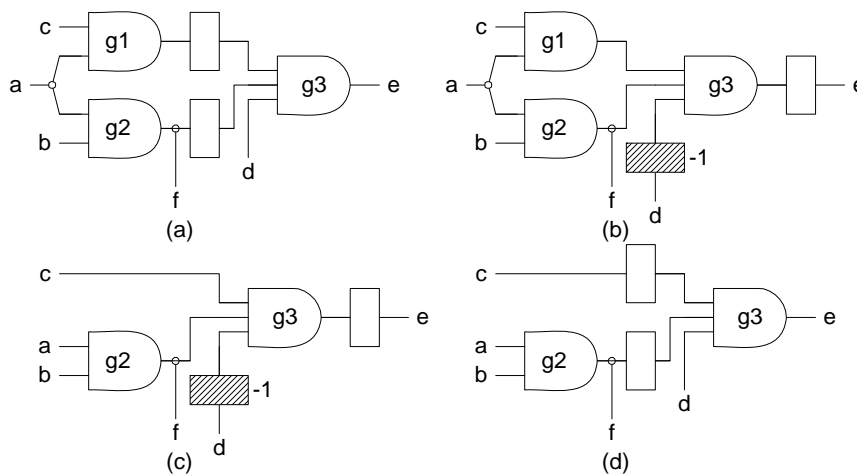

8-54

Peripheral Retiming

 - A peripheral retiming is a retiming such that
 - $r(v)=0$ where v is an I/O pin
 - $w(u,v)+r(v)-r(u)=0$ where $e(u,v)$ in an internal edge
- Move all registers to the peripheral edges
- Leave a purely combinational logic block between two set of registers
- Example:



8-55

Conditions for Peripheral Retiming


- No two paths between any input i and any output j have different edge weights
- Exist α_i and β_j , $1 \leq i \leq m$, $1 \leq j \leq n$ such that $W_{i,j} = \alpha_i + \beta_j$ (m : no. of inputs; n : no. of outputs)
- $W_{i,j} = \sum_{path\ i_j \rightarrow o_j} w(e)$ if all paths between input i and output j have the same weight
- Complexity $O(e \cdot \min(m,n))$

8-56

Examples of Peripheral Retiming

 
- Example 1:

$$W_{1,1}=2, W_{2,1}=3, \\ \Rightarrow \alpha_1=1, \alpha_2=2, \beta_1=1$$



 - Example 2:

$$W_{1,1}=0, W_{1,2}=0, W_{2,1}=0, W_{2,2}=1 \\ \Rightarrow \text{no solution}$$




8-57

Legal Resynthesis Operations (1/2)


- Any that do not create a path with negative weight
- Resynthesis could create pseudo-dependency between any input and output

- Example:

 

8-58

Legal Resynthesis Operations (2/2)

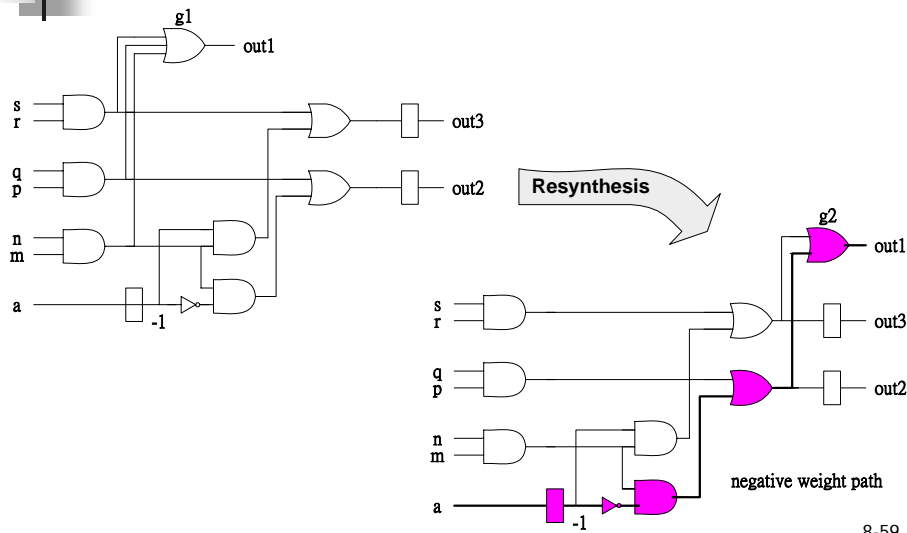

Effects of Retiming and Resynthesis

- Area optimization:
 - No significant improvement
 - Limitation on existing combinational optimization techniques
 - Some circuits (pipelined datapaths) have inherently no potential for further optimization using retiming and resynthesis techniques
- Performance optimization of pipelined circuits:
 - Significant improvements for pipelined arithmetic circuits

8-60